

# Humidity Temperature Controlled House

Team 8

Zhen Yun Li  
Thomas Kong  
Jason Raggio

# Overview

- Design Purpose
- Equipment List
- Sensors
- How the System Works
- Circuit Diagram
- Program Code
- Cost
- Future Improvements
- Conclusion

# Design Purpose

- Create a comfortable, controlled environment
- Help people with medical conditions which require certain temperatures and humidity levels
- Control temperature and humidity of different rooms in one house separately

# Equipment List

- Foam
- Basic Stamp Version 2
- Board of Education
- Light Emitting Diode (LED)
- Two buttons
- Humidity/Temperature Sensor
- Three water pumps
- IRF 510 Transistors
- IN4001 Diodes
- High Resistance Wire
- Servo Motor
- PCV Piping
- 12 VDC Fan
- 24 Gauge Bus Wire- Uninsulated tinned-copper

# Sensor


- Sensirion Temp/Humidity Sensor (SHT11)
- The features include:
  - ✓ A temp. range from  $-40^{\circ}\text{C}$  to  $+123.8^{\circ}\text{C}$
  - ✓ Temp. accuracy  $\pm 0.5^{\circ}\text{C}$  at  $25^{\circ}\text{C}$
  - ✓ Humidity range from 0 to 100% RH
  - ✓ Absolute RH accuracy of  $\pm 3.5\%$  RH
  - ✓ Low Power Consumption (typically  $30\mu\text{W}$ )

# How the System Works - I

- The system is placed in one of the four rooms
- A fan is mounted onto a wall venting outside of the house
- A section of the PVC tubing is attached to a servomotor which will turn the tubing in specific positions
- Tubing is routed through the other rooms which will connect back to the room with the system
- By rotating the servomotor, the system will draw air from each room (separately) via the fan and sample air


# How the System Works - II

## Diagram

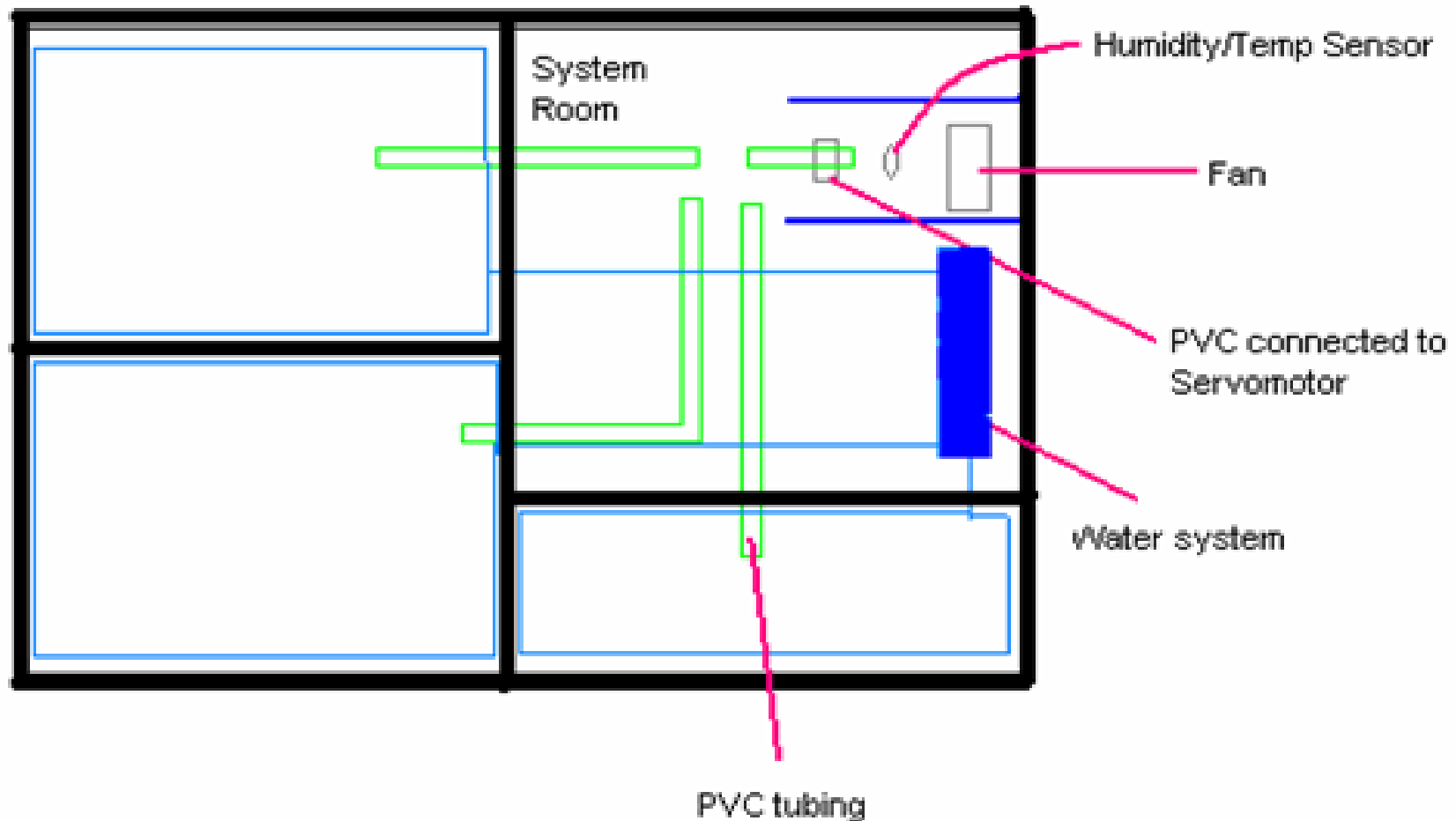


# Circuit Diagram - I


## Water Pump 1

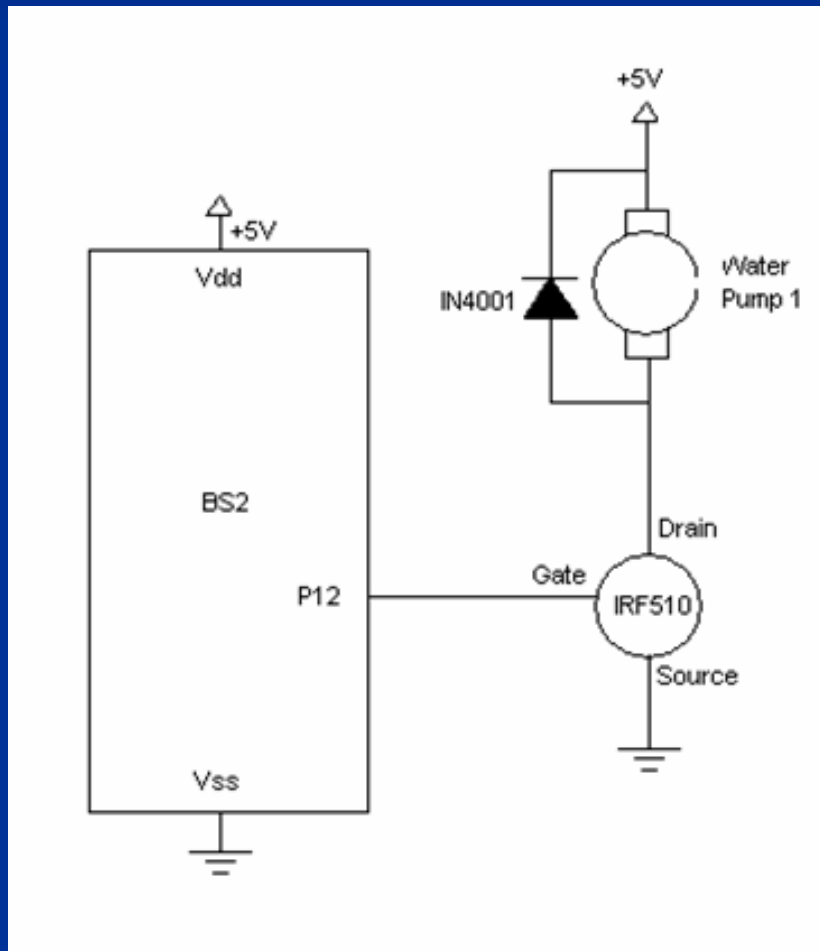

## Water Pump 2

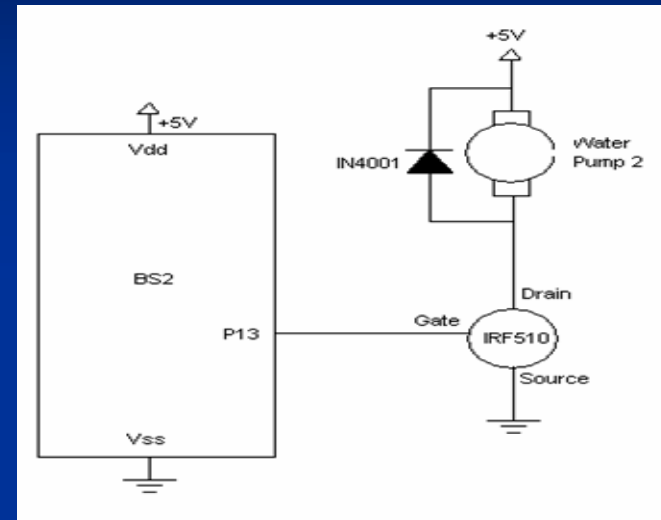


## Water Pump 3

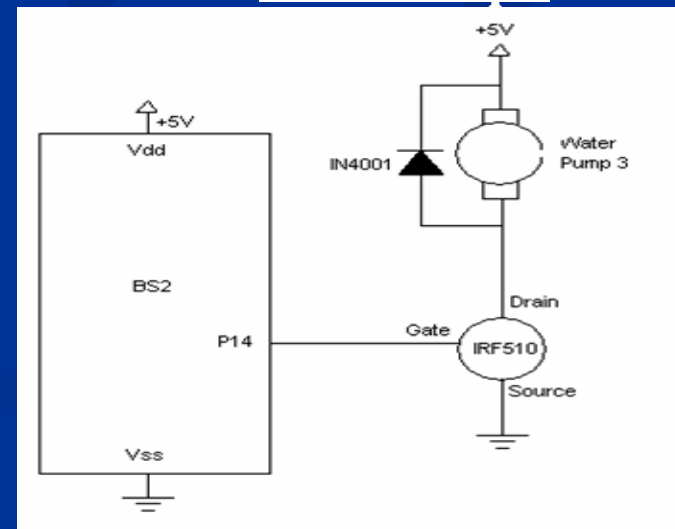




# Circuit Diagram - II

Servomotor


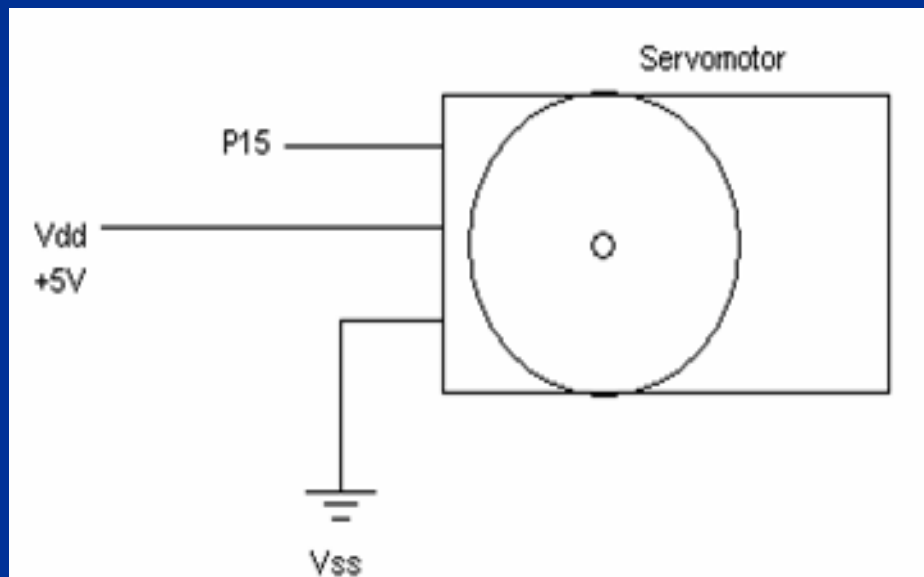


Fan

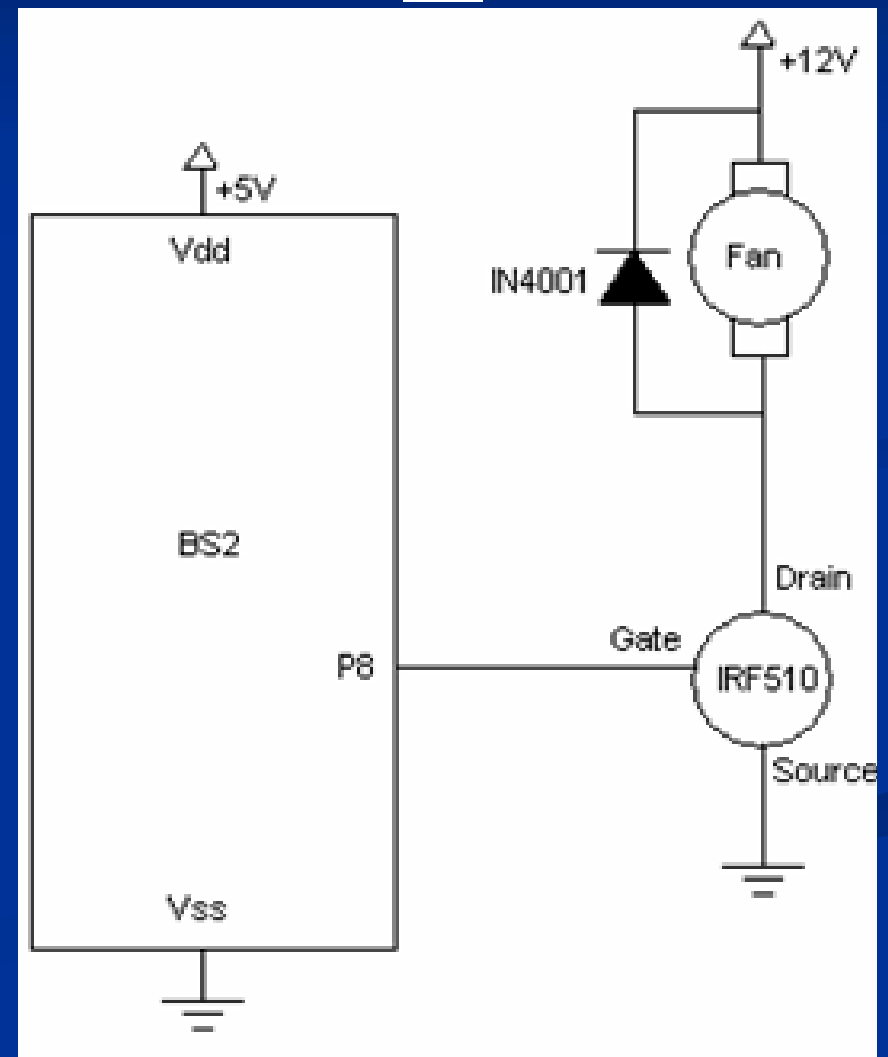


# Circuit Diagram - III

## Sensirion SHT 11 Temp/Humidity Sensor

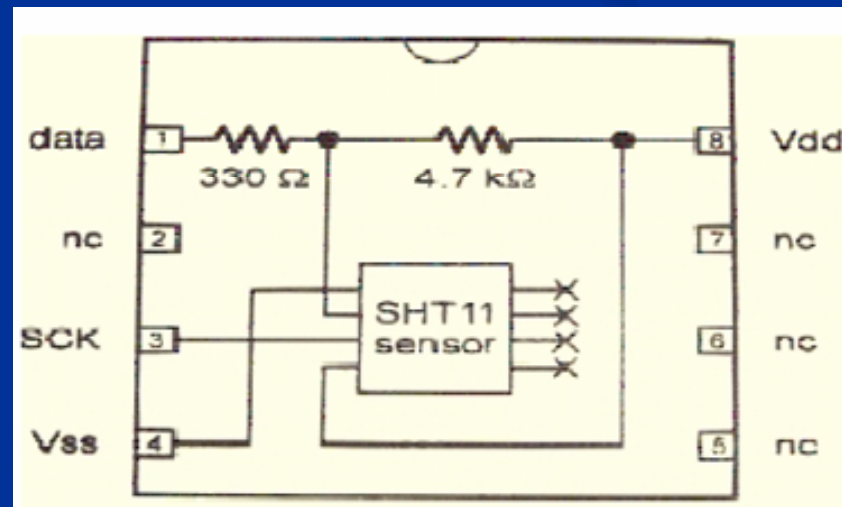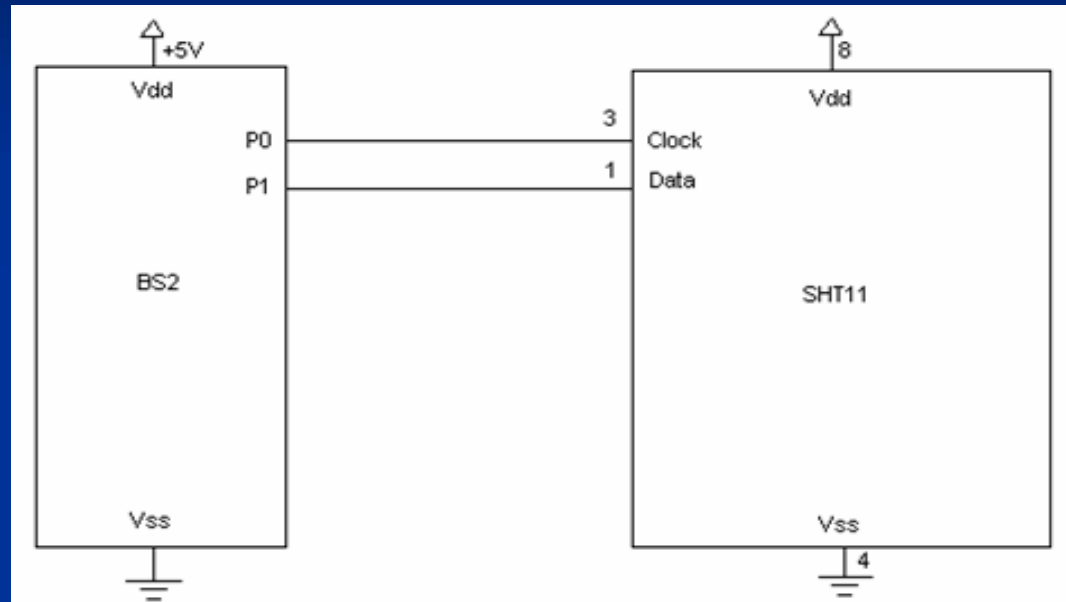

# Circuit Diagram - IV


## Emergency and Reset Buttons

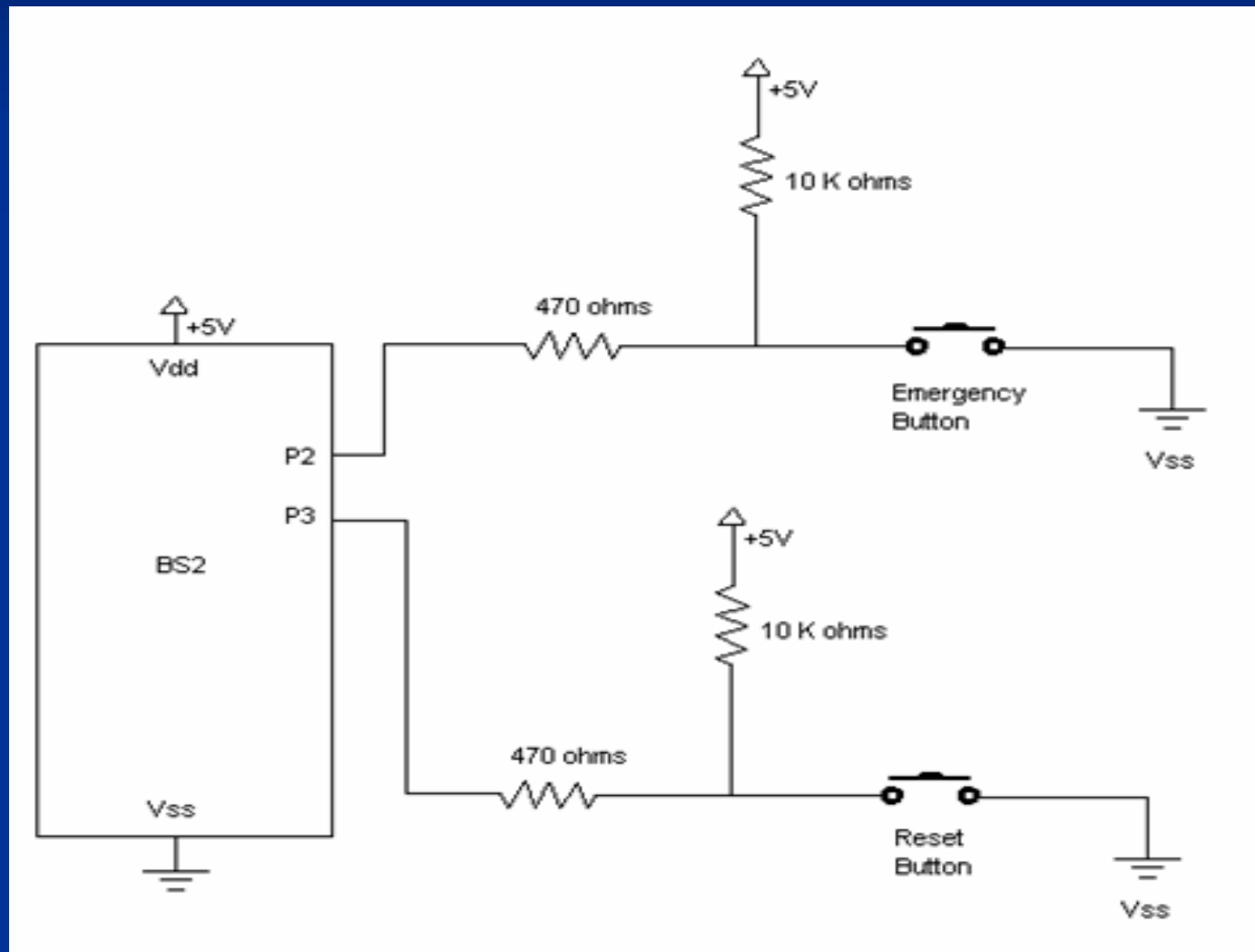

# Circuit Diagram - V

## Heating

### Room 1

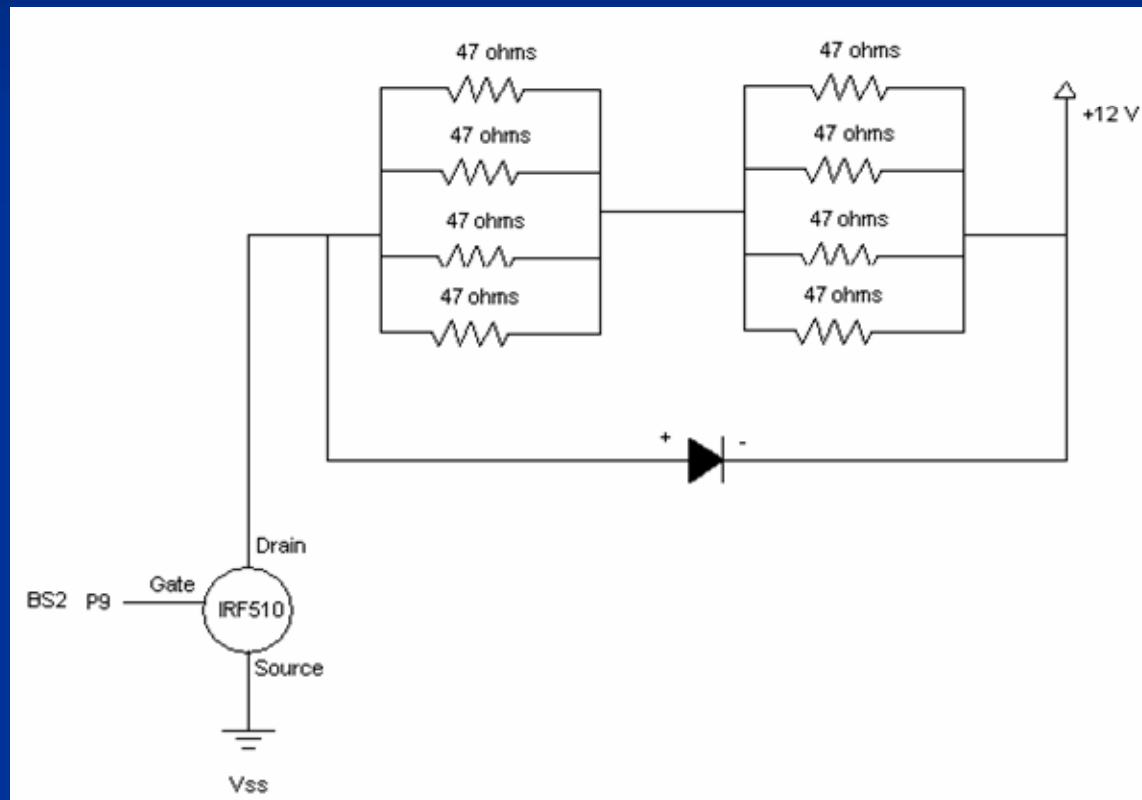

Heater for room 2 and 3 are similar except that Pins 10 and 11 were used on the BS2

# Program Code

# Cost

BS2, Board of Education, etc.	\$130.00
Plexiglass (30" x 36")	\$11.92
1/2" PVC tubing 20 ft.	\$2.80
IN4001 Diode x 7	\$4.49
IRF-510 MOSFET Transistor x 7	\$15.13
Foam	\$15.62
Tape	\$2.38
L-fittings for PVC x 5	\$1.03
Fan x 2	\$23.88
Water Pump x 2	\$25.00
Sensirion SHT11 Temp/Humidity Sensor	\$32.59
24 Gauge Bus Wire	\$2.16
Total	\$267.00

# Future Improvements

- Creating better connections at joints in ducting system
- Making the system more efficient (ie: one water pump)
- Humidifier/spray nozzles
- Incorporate other various systems such as:
  - Carbon Monoxide detector system
  - Smoke/fire detector system
  - Home Security system
  - Cooling system
  - Dehumidifier

# Conclusion

- Prototype was successful
- Can be applied elsewhere (ie: tropical plants)