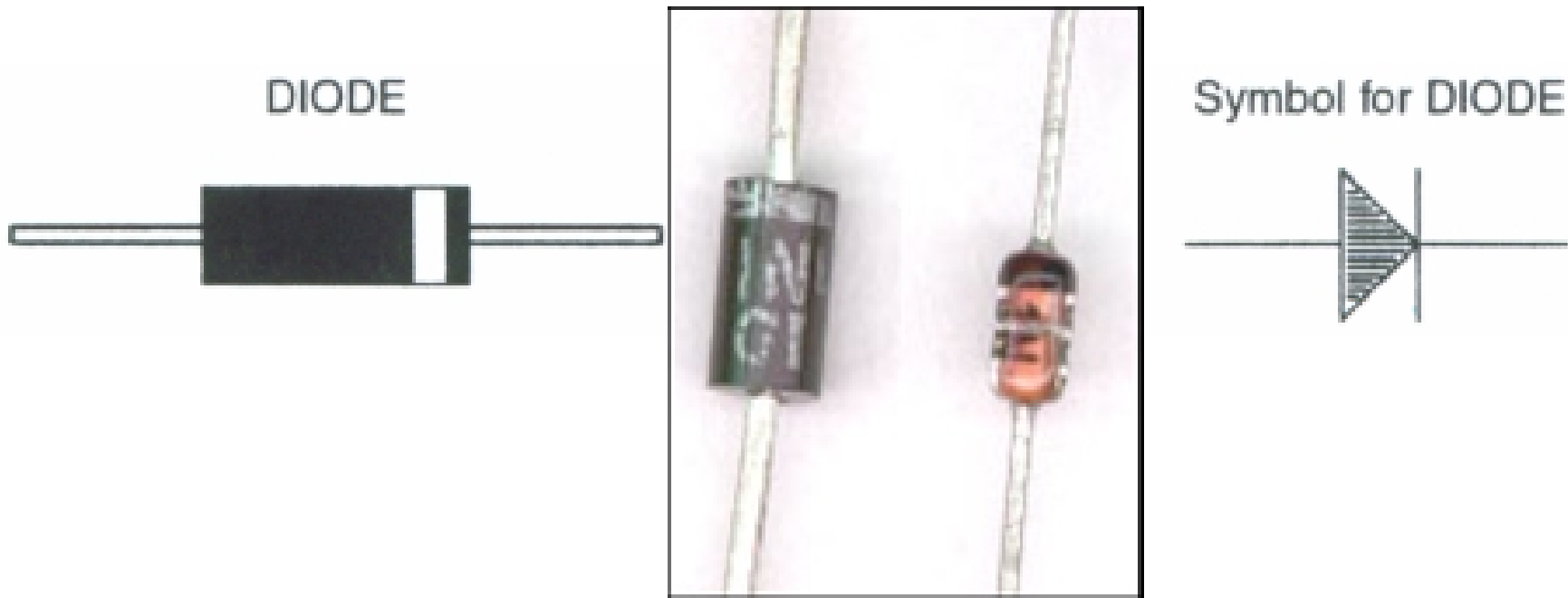



# Lecture 3

# Diode




A diode is an semiconductor component that, in general, will pass current in only one direction

# Water Analogy of Diodes

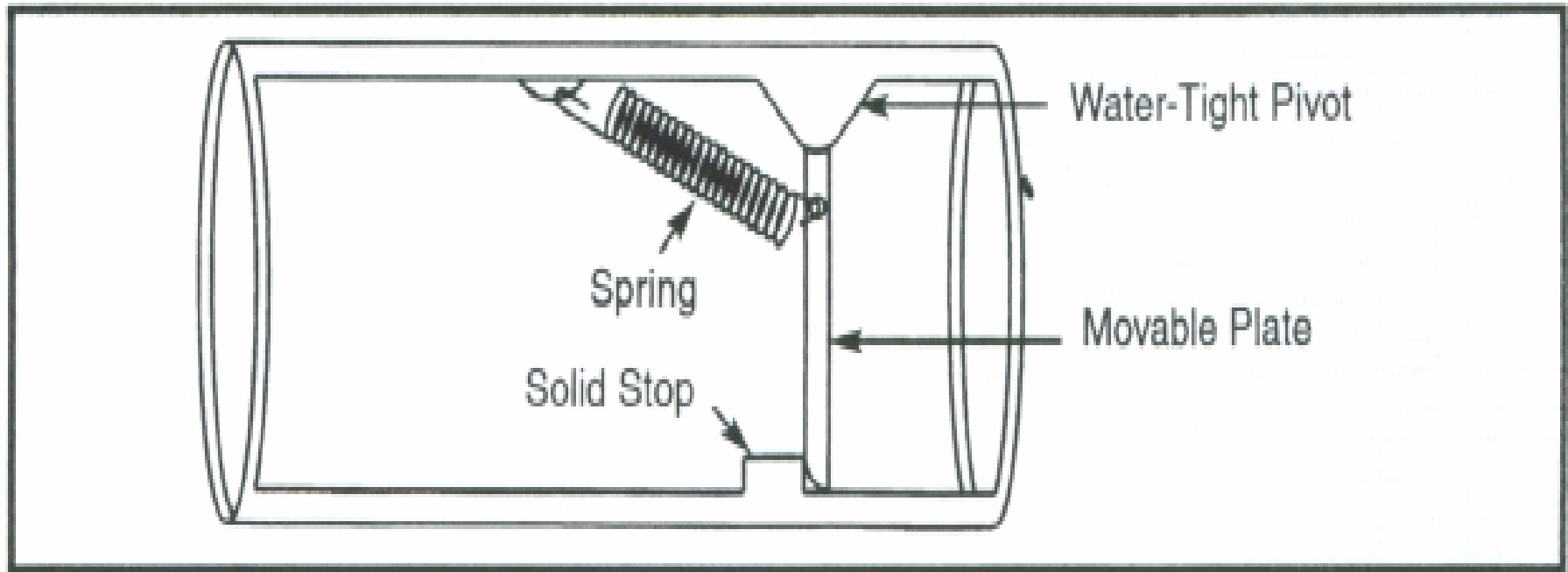


# Diode: How it Works

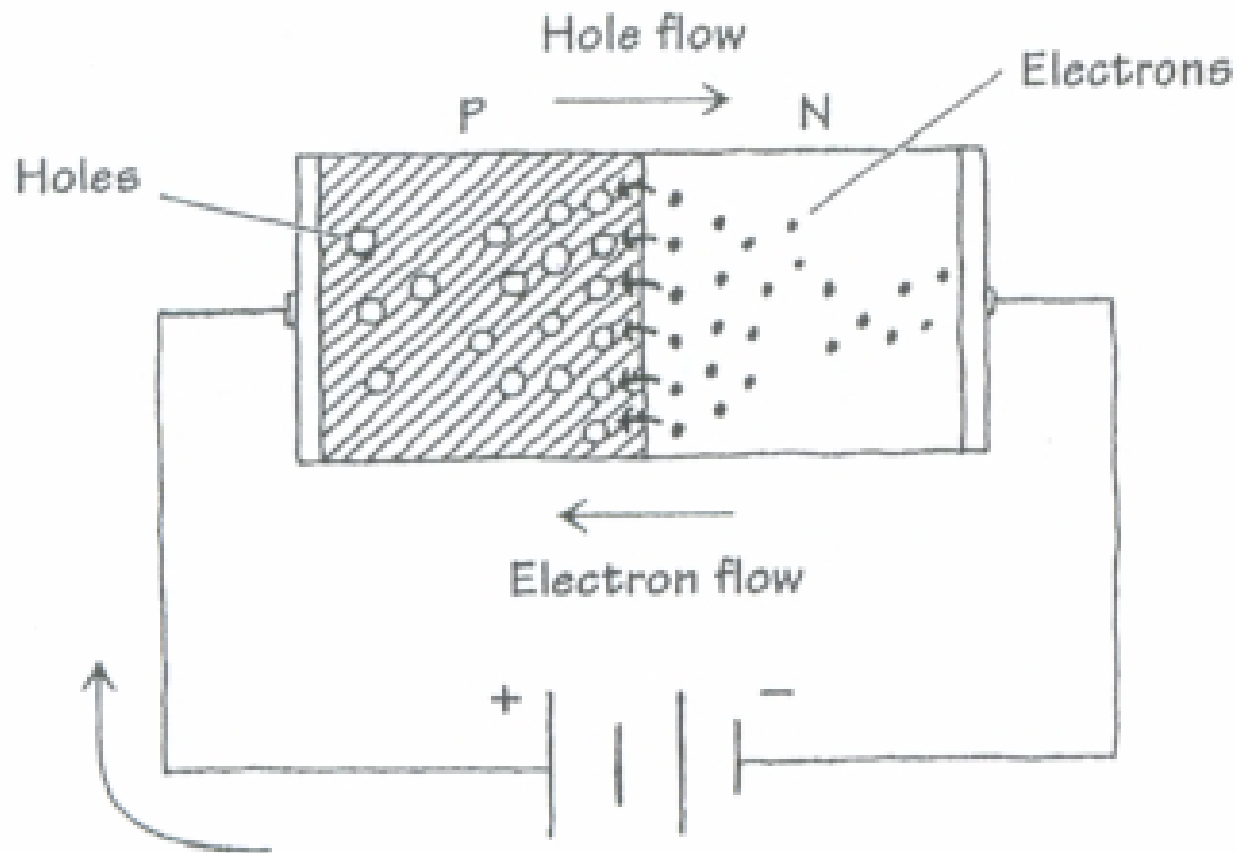



**Forward-biased (“open door”)**

# Diode: How it Works

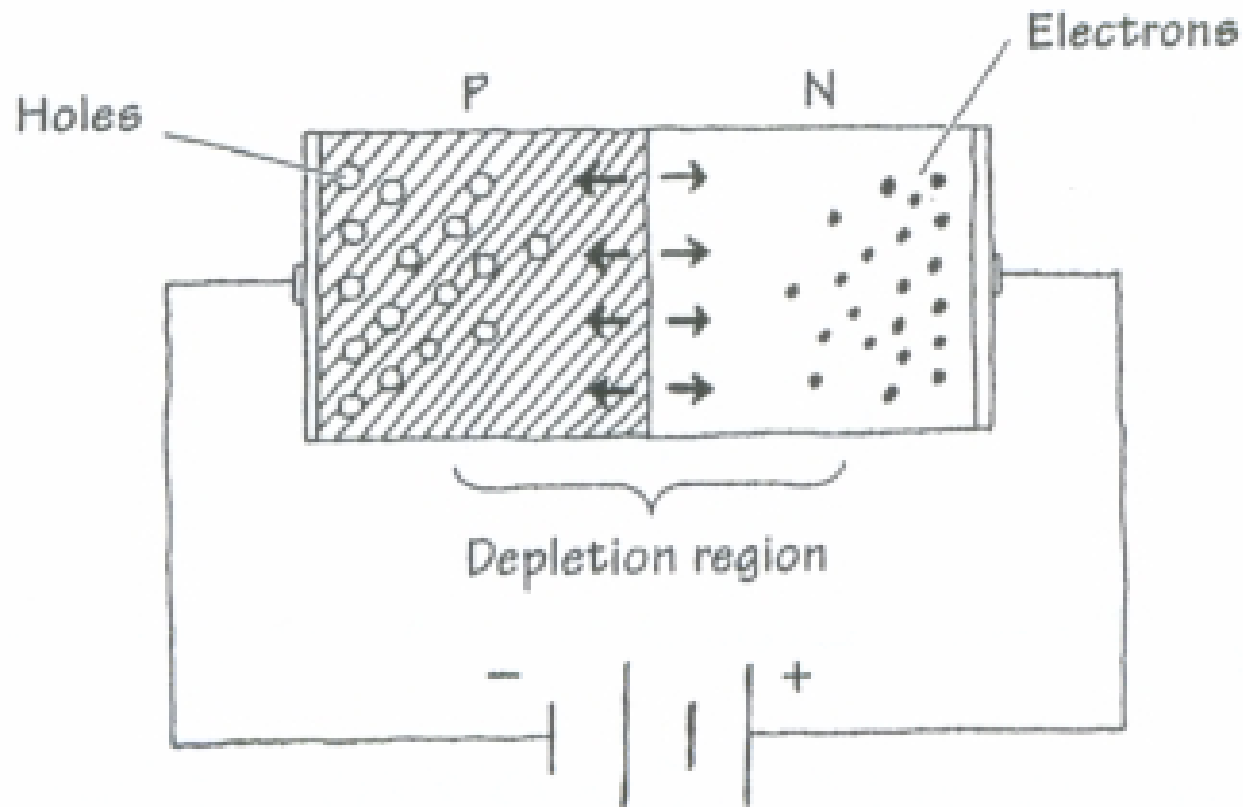


**Reverse-biased (“closed door”)**

# Diode Applications 1

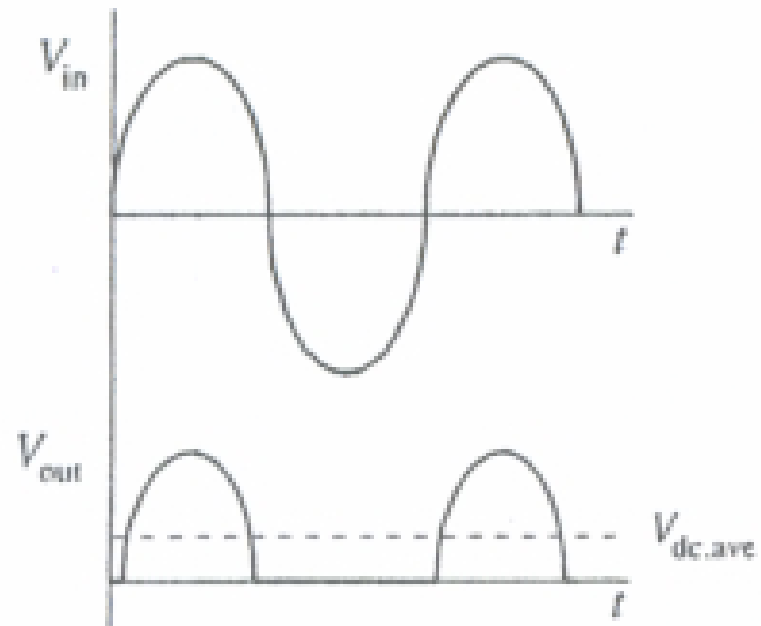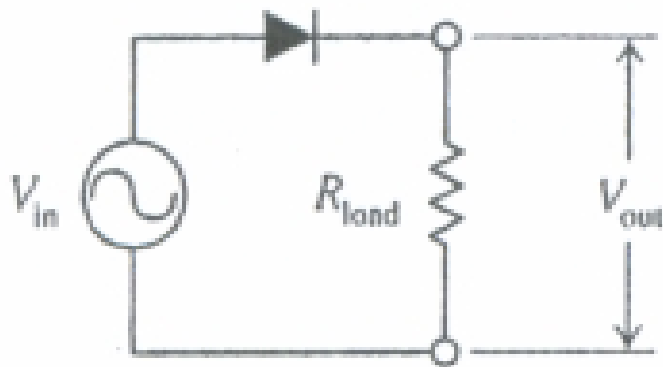


## Half-Wave Rectifier

# Diode Applications 2

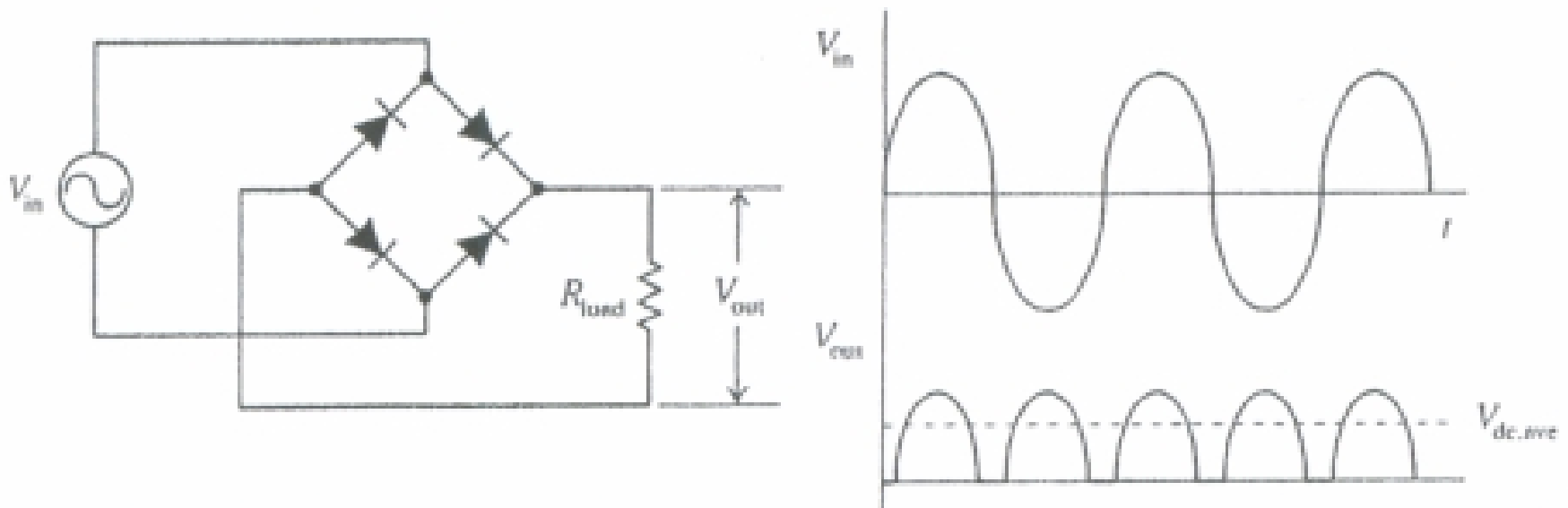

## Full-Wave Bridge Rectifier

# Diode Applications 3

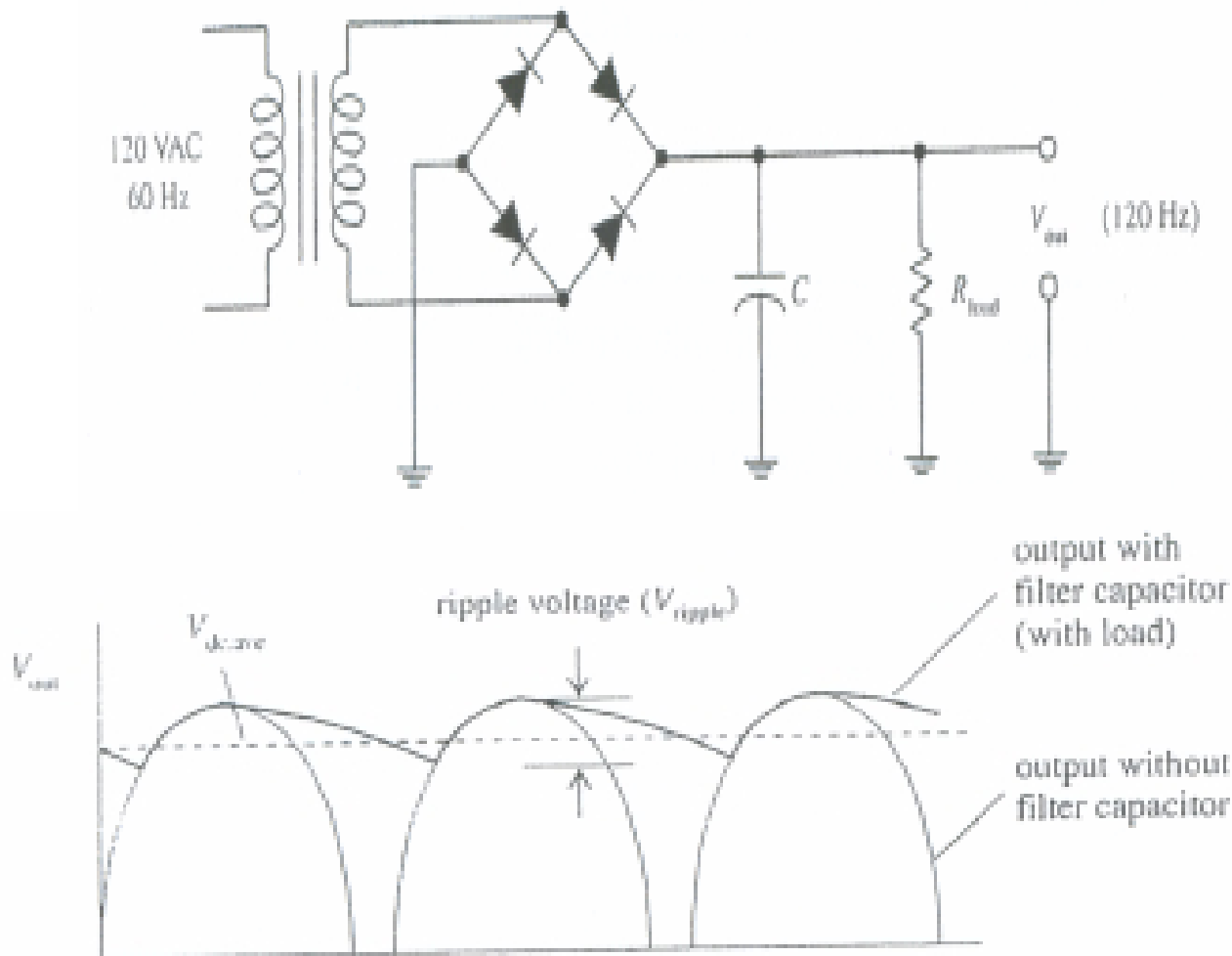


## Basic AC-DC Power Supply




# Diode Applications 4

DC application

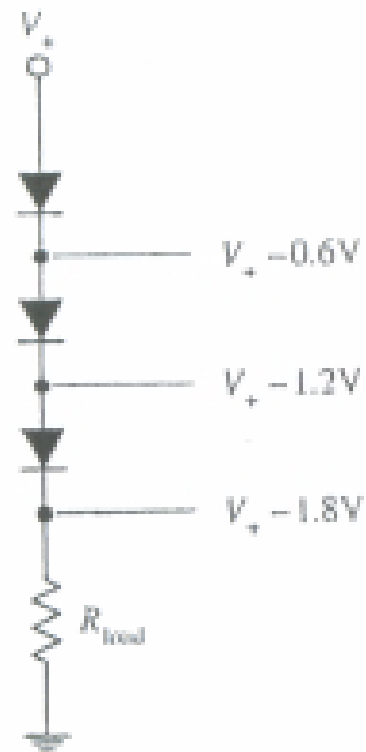


AC application

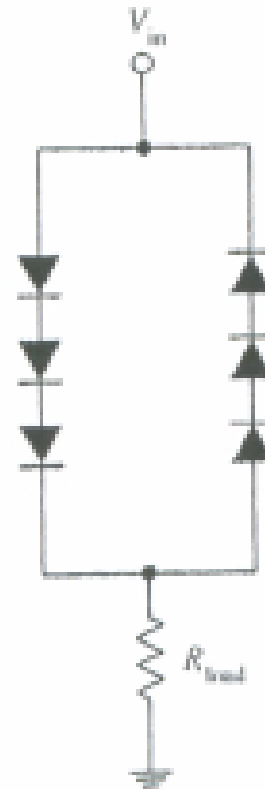


**Voltage Dropper**

# Zener Diode

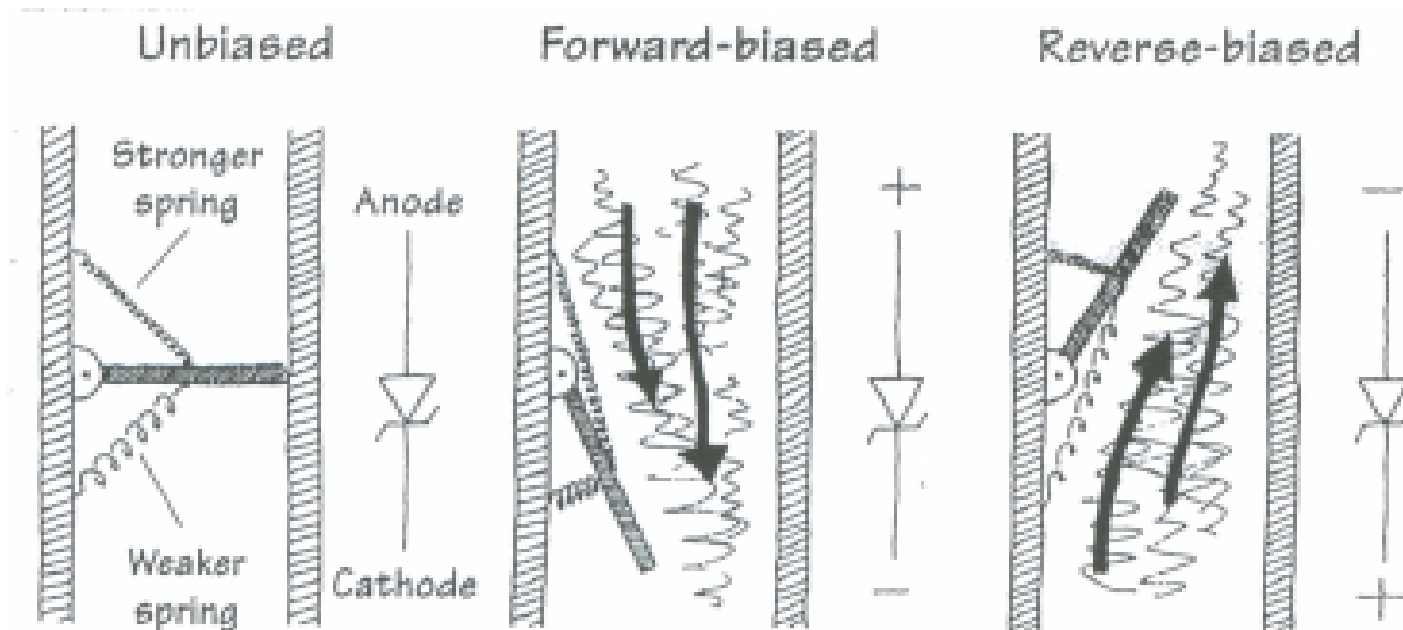**Acts as a pn-junction diode but it also has the ability to conduct in the reverse-biased direction when a specific breakdown voltage is reached**



# LED

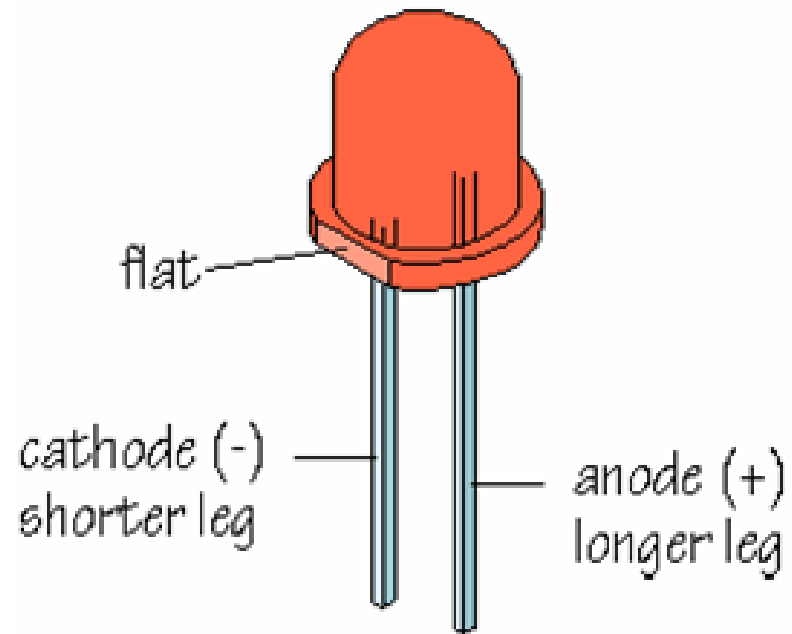


Light-emitting diode


Semiconductor

Has polarity


# LEDs

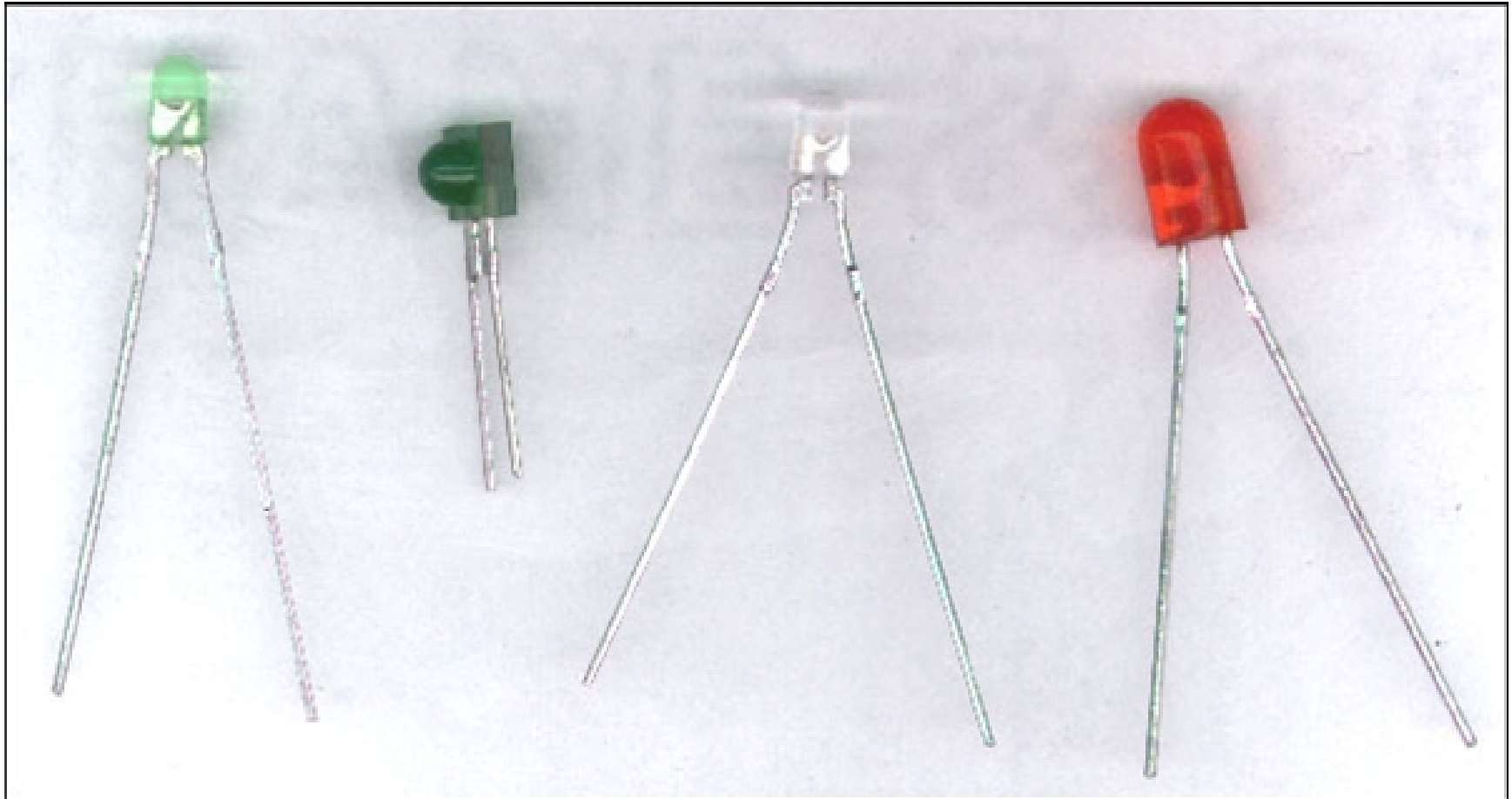


# LED: How It Works

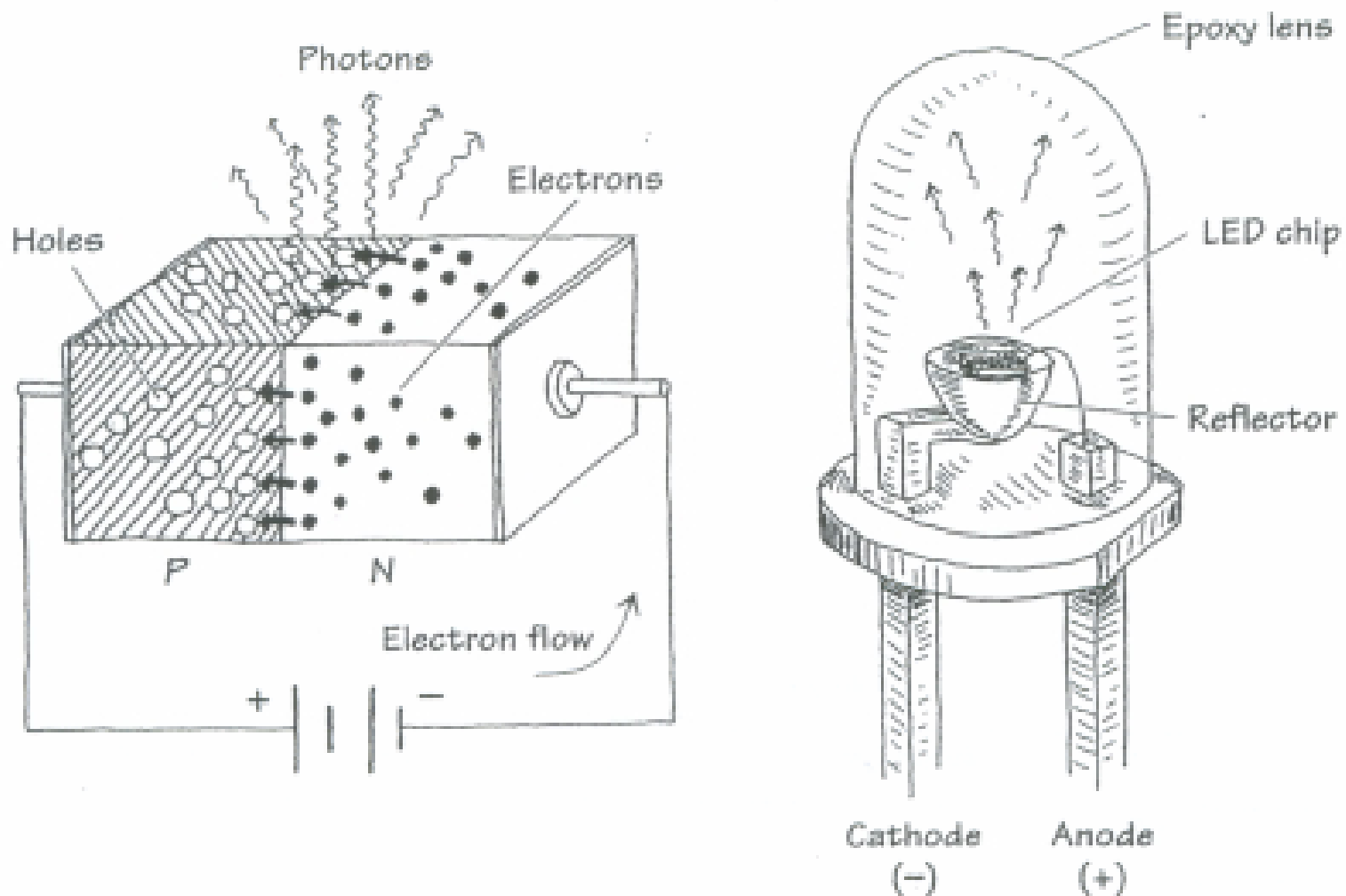

# Kinds of LEDs 1

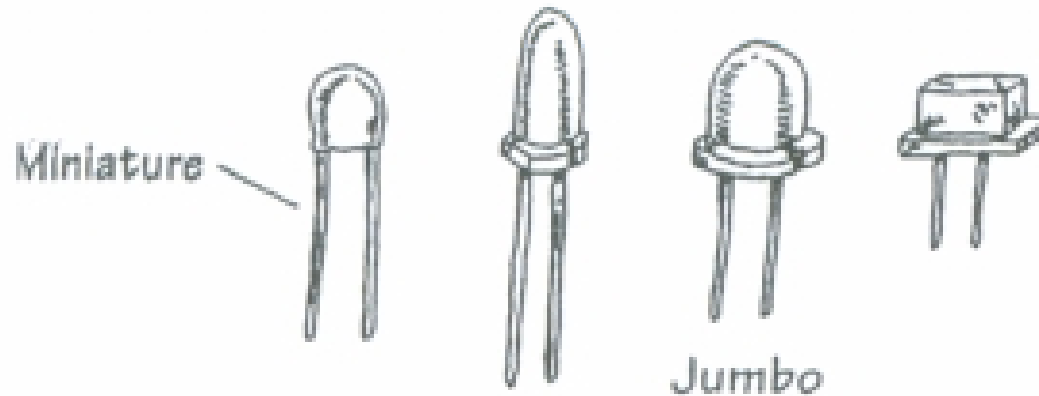


## Visible-Light LEDs


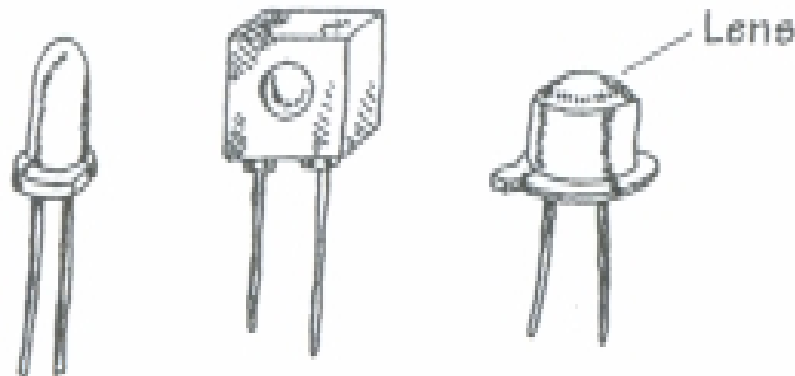


## Infrared LEDs

# Kinds of LEDs 2

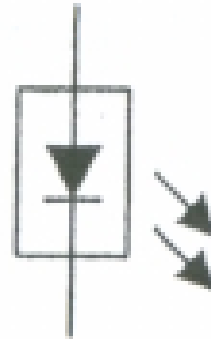


## Blinking LEDs

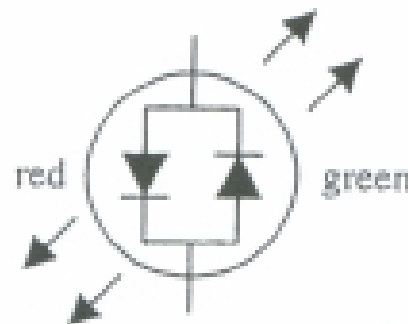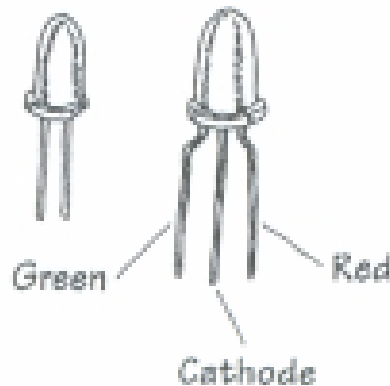

## Tricolor LEDs


# How to Connect LED

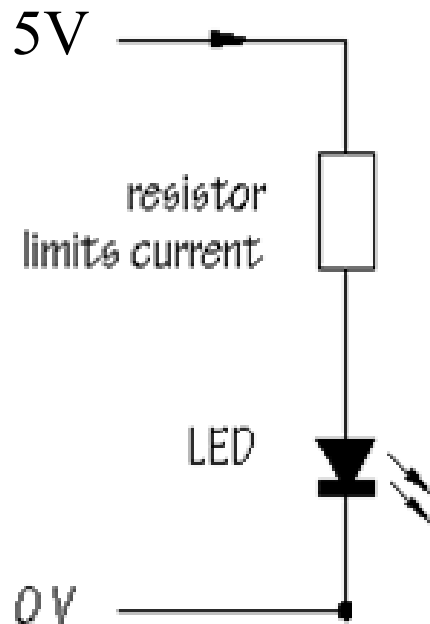


- Requires 1.5~2.5V and 10 mA
- To prevent overloading, use resistor ( $470\Omega$ )



# Connect LED to BS2

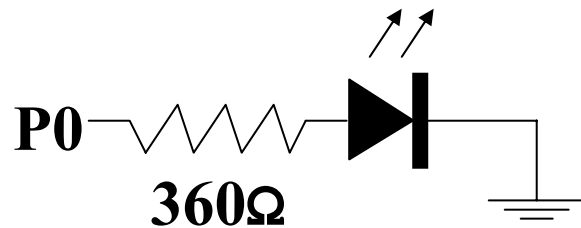


LED is on when P0 is high

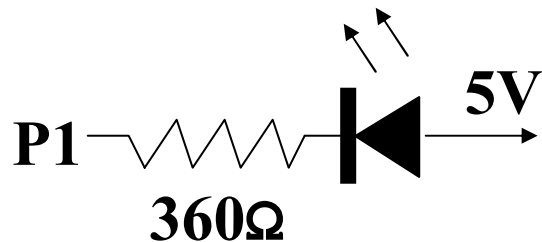

LED is on when P1 is low

# Connect Multiple LEDs to BS2

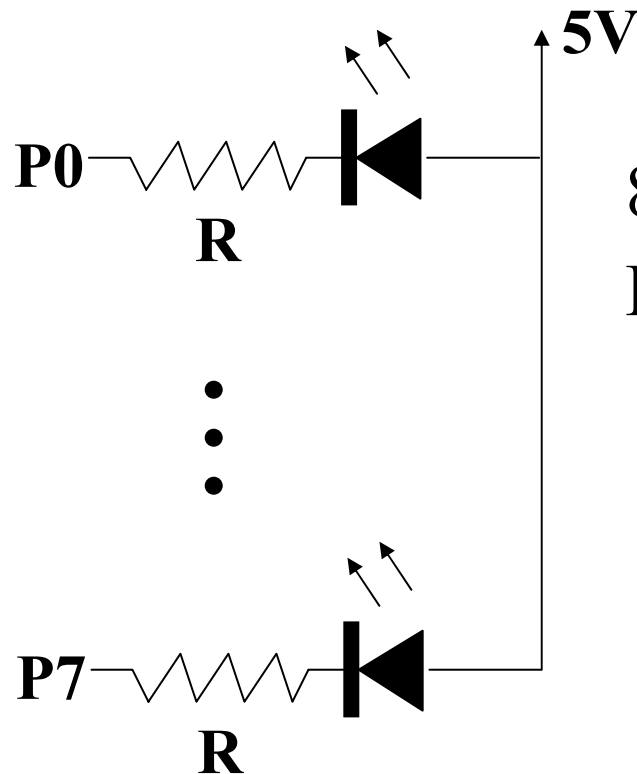

8 LEDs are connected to BS2

Each I/O/pin (P0-P7) is allowed to sink 6.25mA


$$R = \frac{V}{I} = \frac{3.6}{6.25 \times 10^{-3}} = 576\Omega$$

# 7 Segment LEDs



- 7 Light-emitting diodes in one
- Display any single-digit number (0–9)

# 7 Segment LED Circuit

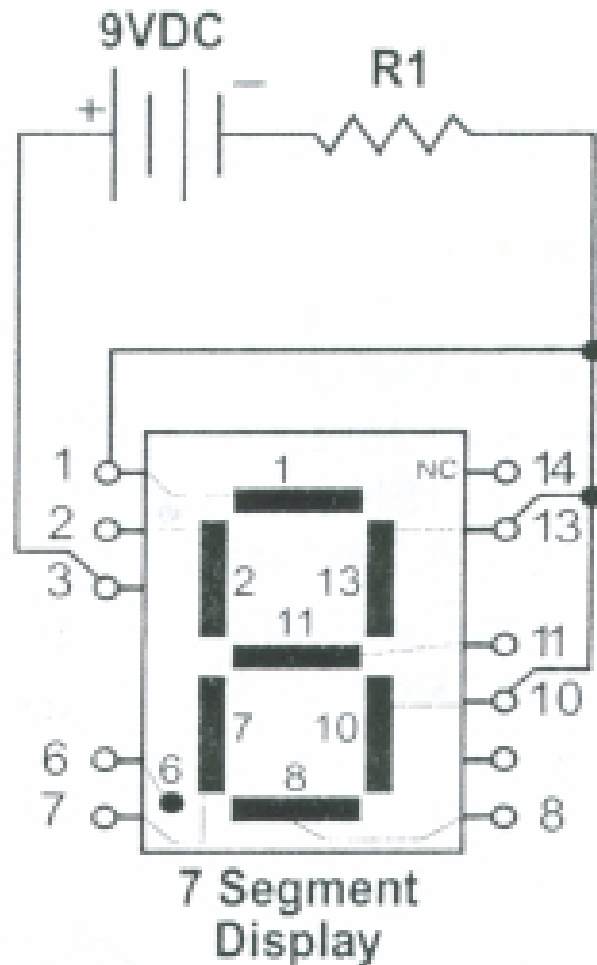

Number	Segments
0	1, 2, 7, 8, 10, 13
1	10, 13
2	1, 7, 8, 11, 13
3	1, 8, 10, 11, 13
4	2, 10, 11, 13
5	1, 2, 8, 10, 11
6	1, 2, 7, 8, 10, 11
7	1, 13, 10
8	1, 2, 7, 8, 10, 11, 13
9	1, 2, 10, 11, 13
Decimal Point	6 and 9

# LED Experiments

Experiments	Chapters
What's micro controller	1
Basic A and D	
Earth measurements	
Robotics	
StampWorks	1, 2, 3, and 4
Others	

# Lecture 4

# Button/Switch




Symbol

# Switches 1

## SPST switches (Single Pole, Single Throw )



Throw switch

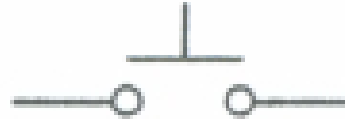

Normally open  
push-button




Normally closed  
push-button

## SPDT switches



Throw switch

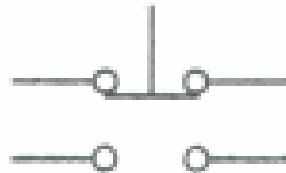

Normally open/closed  
push-button



# Switches 2

## DPST switches




Throw switch



Normally open  
push-button

## DPDT switches

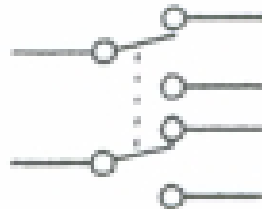



Throw switch





Normally open/closed  
push-button

# Switches 3


## SP(n)T switches

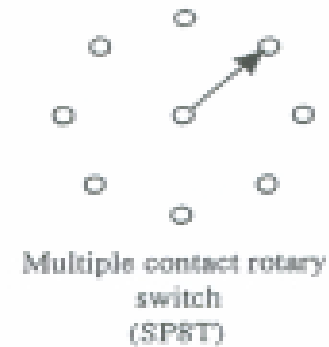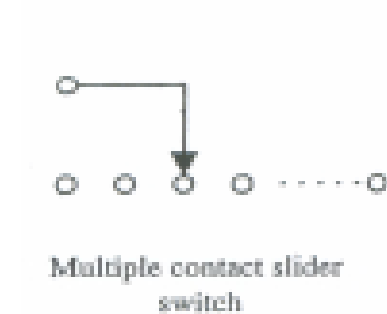

## (n)P(m)T switches

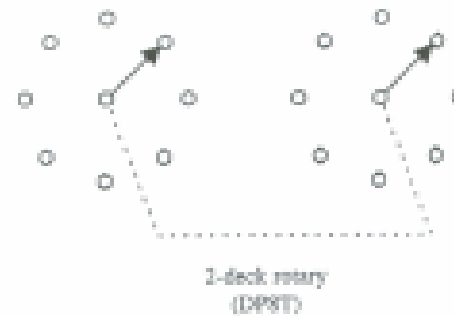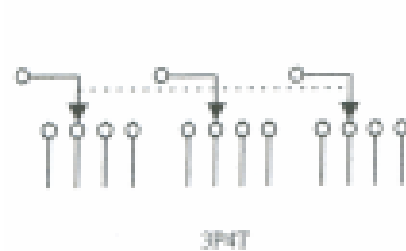


# Button Connection 1 (Wrong)

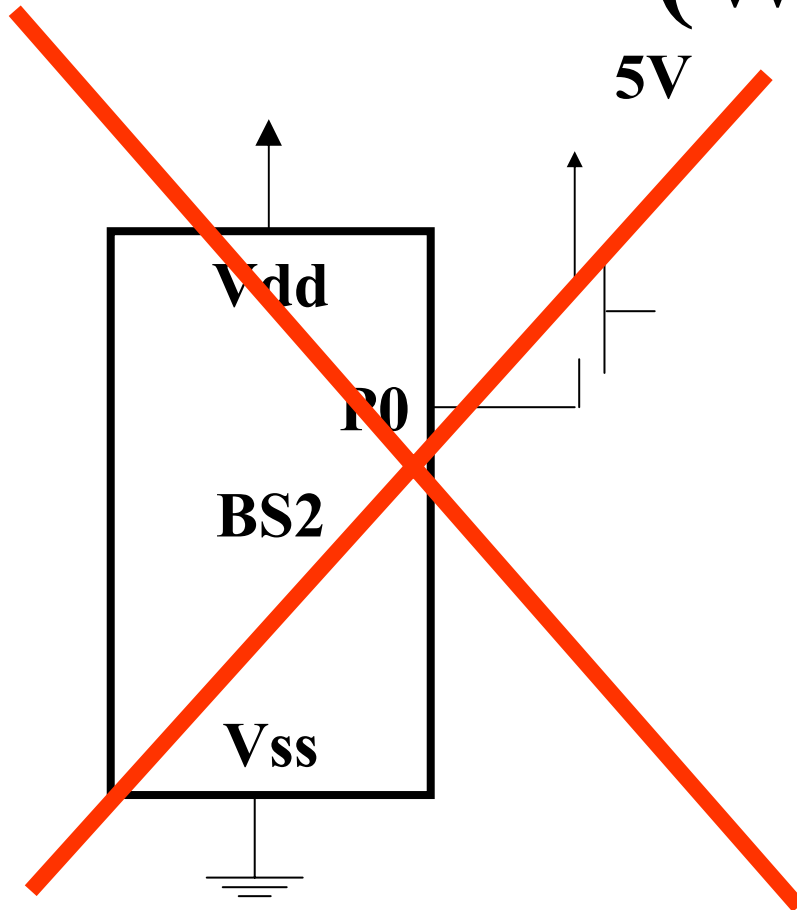

BS2 will get damaged when P0 is pulled high since the current limit through pin is violated

$$I = \frac{V}{R} = \frac{5}{0} = \infty$$


# Button Connection 2 (Wrong)

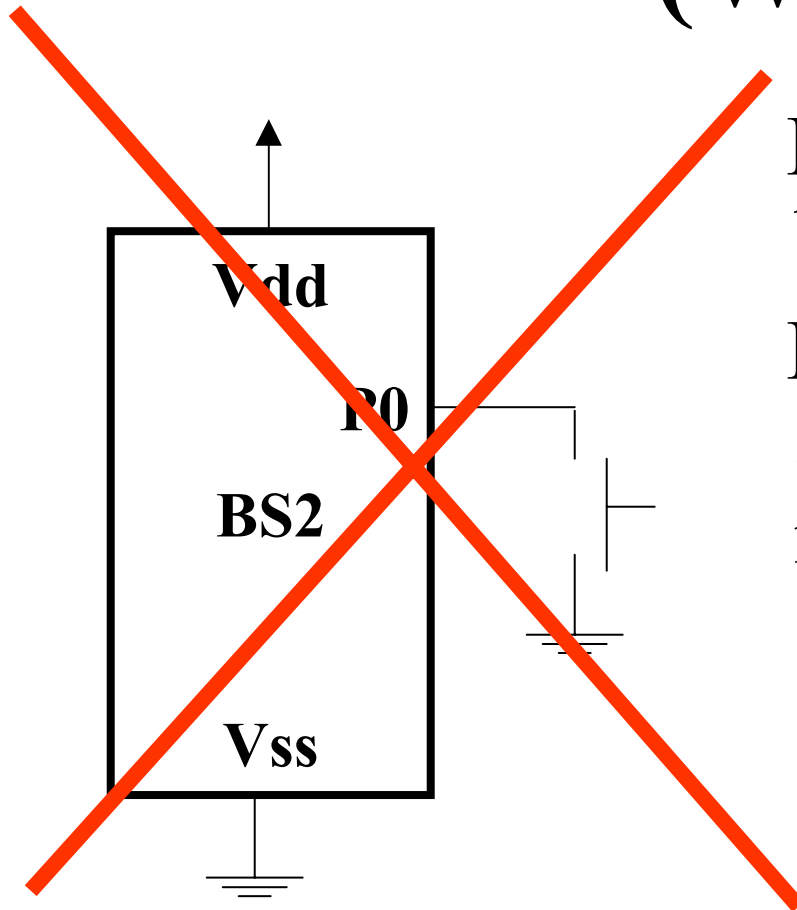

P0 is pulled low when the button is pressed

But P0 is not connected to anywhere when the button is not pressed then P0 could be either high or low so called a floating input condition


# Button Connection 3 (Wrong)

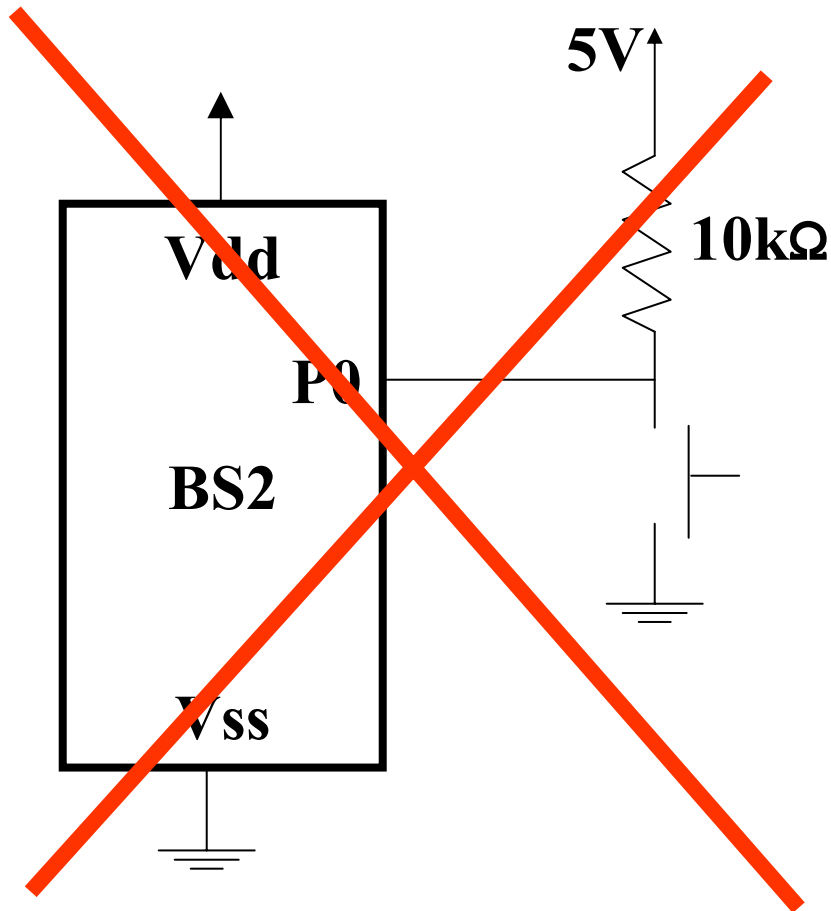

- Button is not pressed  
P0 is pulled high
- Button is pressed  
P0 is pulled low
- By mistake, P0 is used  
as a output when the  
button is pressed  
then ...

# Button Connection 1


## (Pull up resistor)

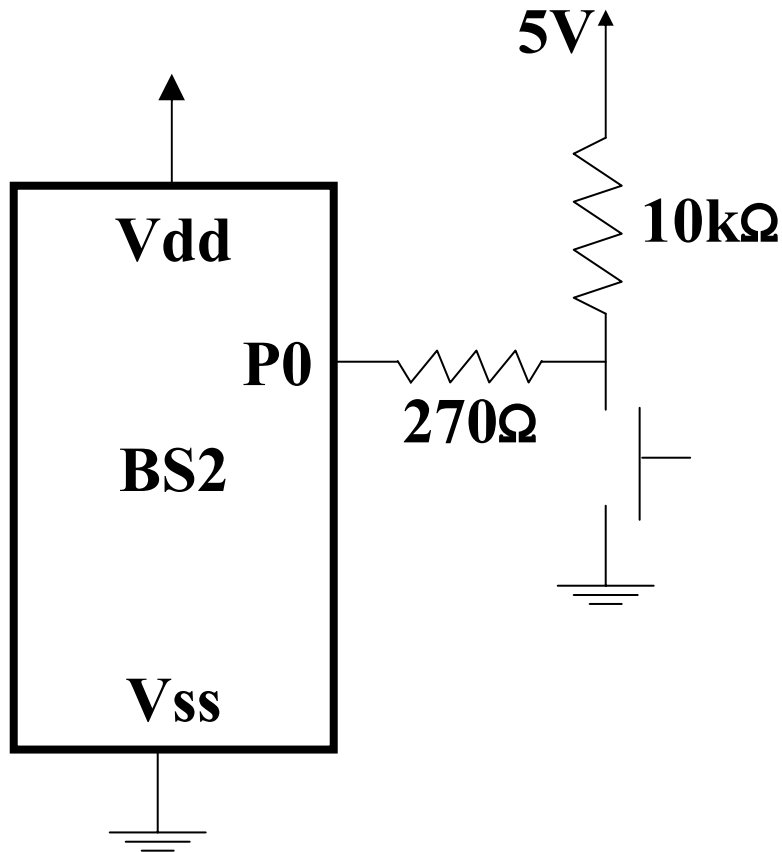

- Button is not pressed  
P0 is pulled high
- Button is pressed  
P0 is pulled low
- 270Ω is for protecting I/O pin
- Preferred


# Button Connection 2

## (Pull down resistor)

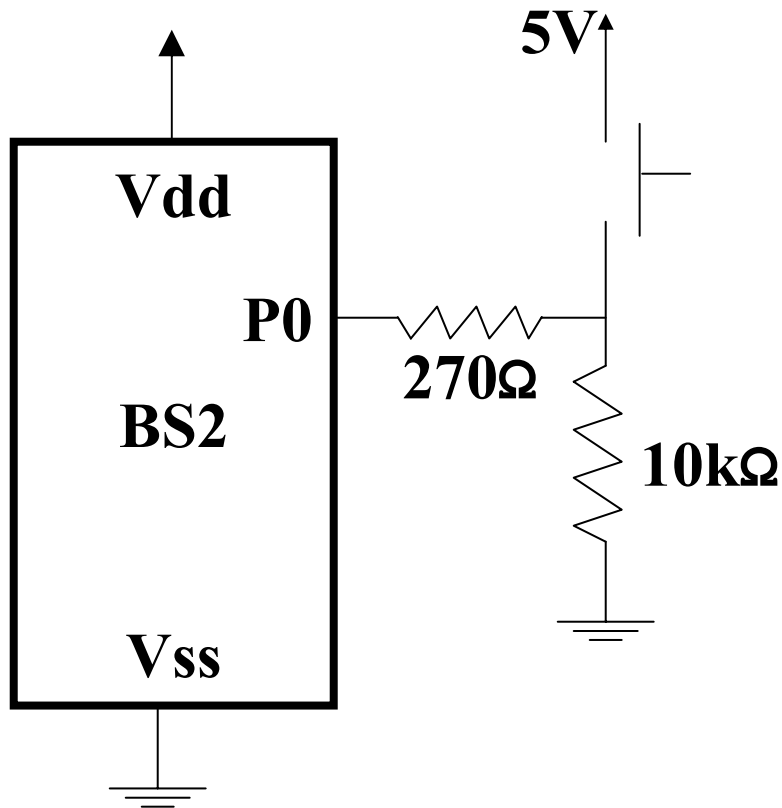

- Button is not pressed  
P0 is pulled low
- Button is pressed  
P0 is pulled high
- 270Ω is for protecting I/O pin


# Limit Switch

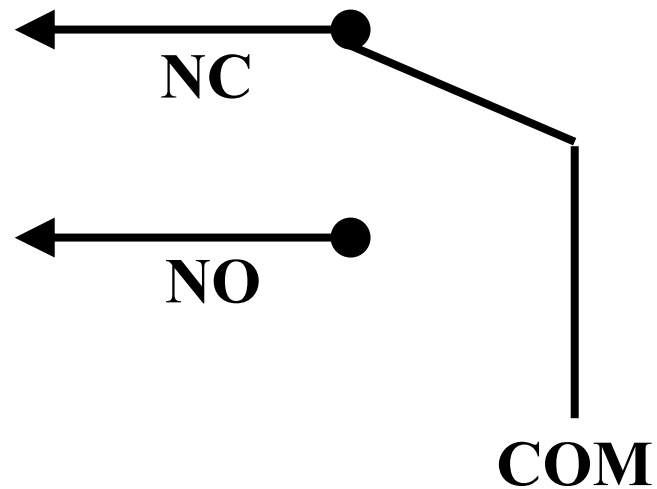

SPDT limit switch



# Limit Switch

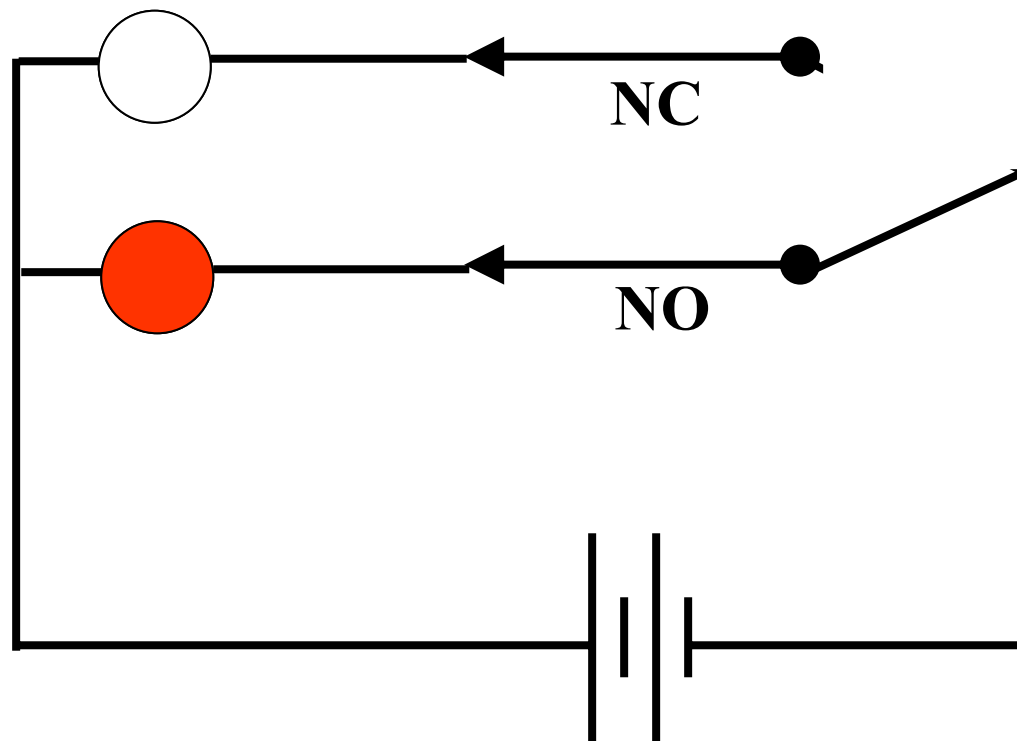

# Button Experiments

Experiments	Chapters
What's micro controller	2
Basic A and D	2
Earth measurements	
Robotics	
StampWorks	6, 8, 9, and 10
Others	

# Simple Project

**Problem 2:** Recently, at a local primary school a young student was left behind on the school premises at the end of the school day. The student was rescued after his parents' frantic efforts to locate him. Following this incident, the school hired a safety consultant to recommend solutions to prevent recurrence of such incidents. The safety consultant has suggested that the school implement the following solution to keep real-time count of individuals on school's premises.

# **Simple Project -Cont.**

**Individuals will enter and exit the school from two separate gates. A pressure sensitive pad at the entrance gate will register entrance by an individual whenever it is depressed. Another pressure sensitive pad at the exit gate will register exit by an individual whenever it is depressed. A microcontroller will continuously monitor the two pressure pads. You are to develop a prototype real-time people counting system. Use two buttons to mimic the pressure pads and write a program that will provide real-time people count. What are some of the drawbacks of the above solution? How can this solution be further improved?**