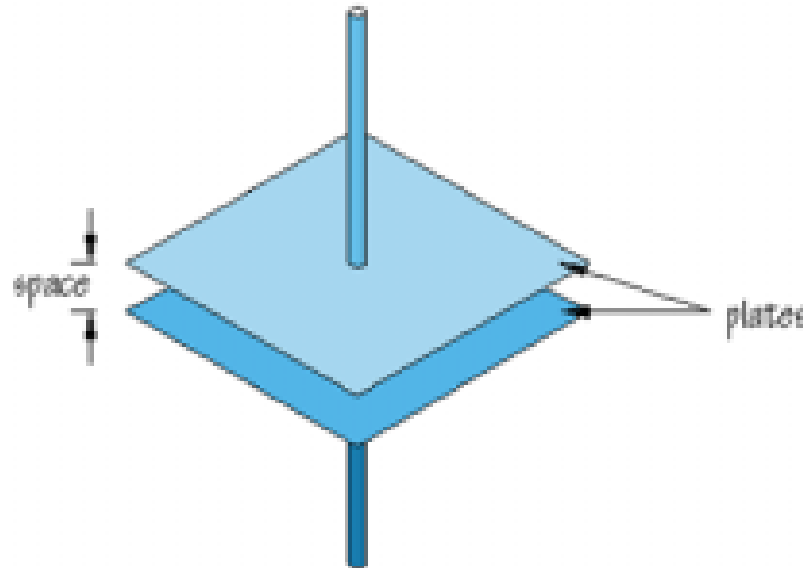


# Lecture 5

# Capacitors 1

- Store electric charge
- Consists of two **plates** of a conducting material separated by a space filled by an insulator
- Measured in units called **farads, F**




# Capacitors 2



Mylar


Ceramic

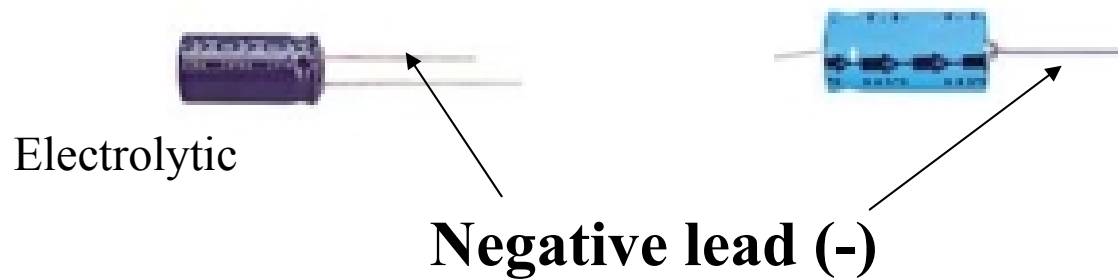

Electrolytic

Negative lead (-)

# Capacitor Symbols

 

**Fixed  
capacitor**




**Polarized  
capacitor**



**Variable  
capacitor**

# How to Read Capacitor Value

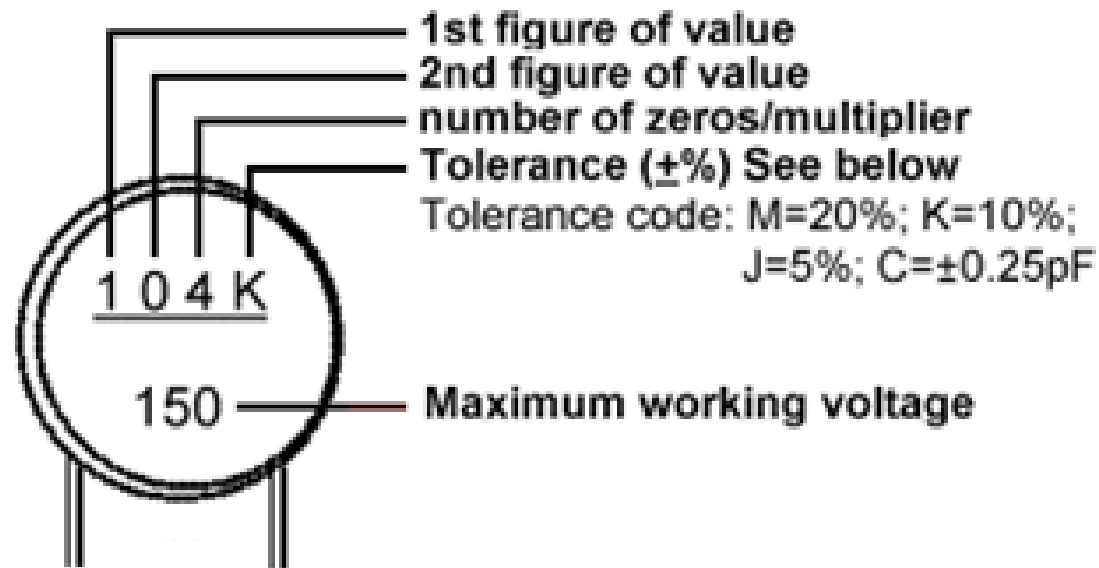

- The first two figures give us 10, the third figure gives us 0000, and the letter 10%. We normally express this as  $0.1\mu\text{F}$ .

# Example: Capacitor Value 1

Ceramic




Label represents  
a tolerance


Label says: 103M

Actual value:  $0.01\mu\text{F} \pm 20\%$

# Example: Capacitor Value 2

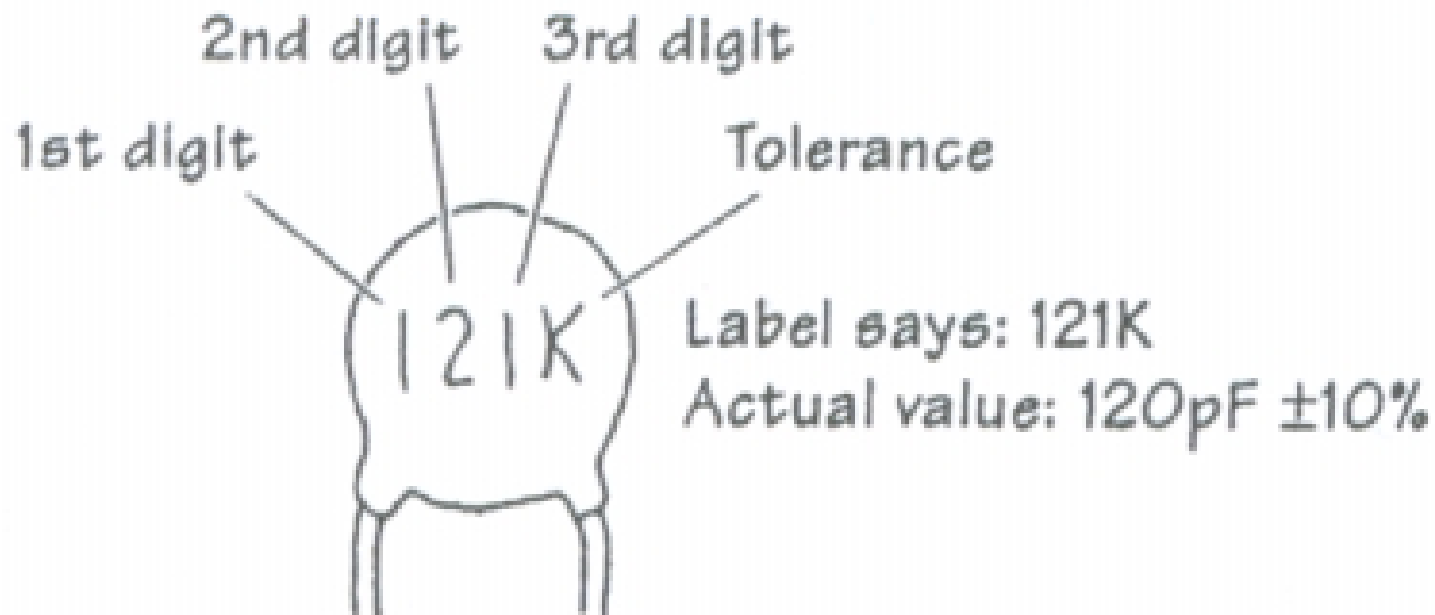

## Example: Capacitor Value 3

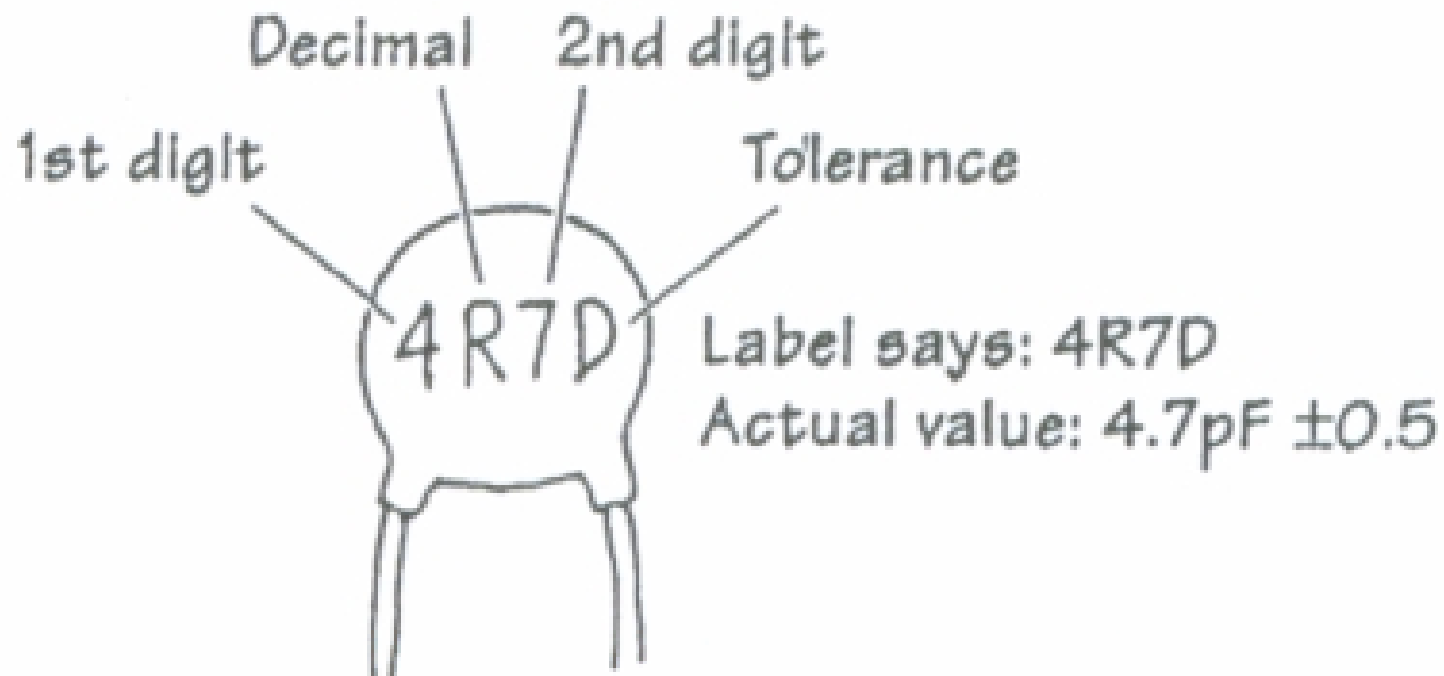



# Example: Capacitor Value 4


European Marking



Label says: 68p  
Actual value: 68pF

# Lecture 6

# Photoresistors

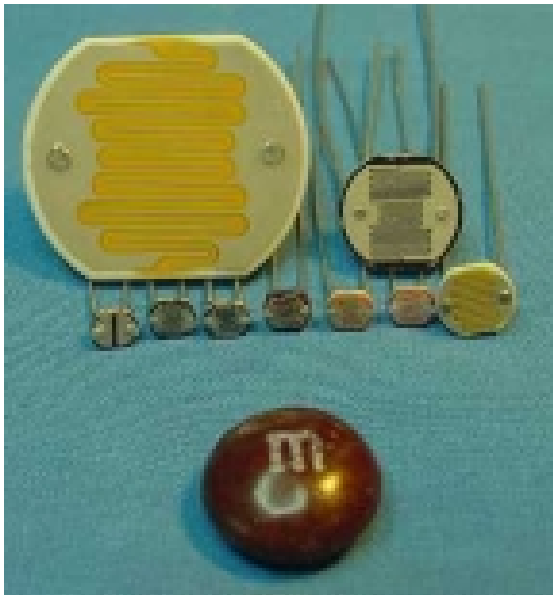


- Light sensitive resistors
- Resistance decreases when light intensity increases




Symbol





# Photoresistor: How It Works

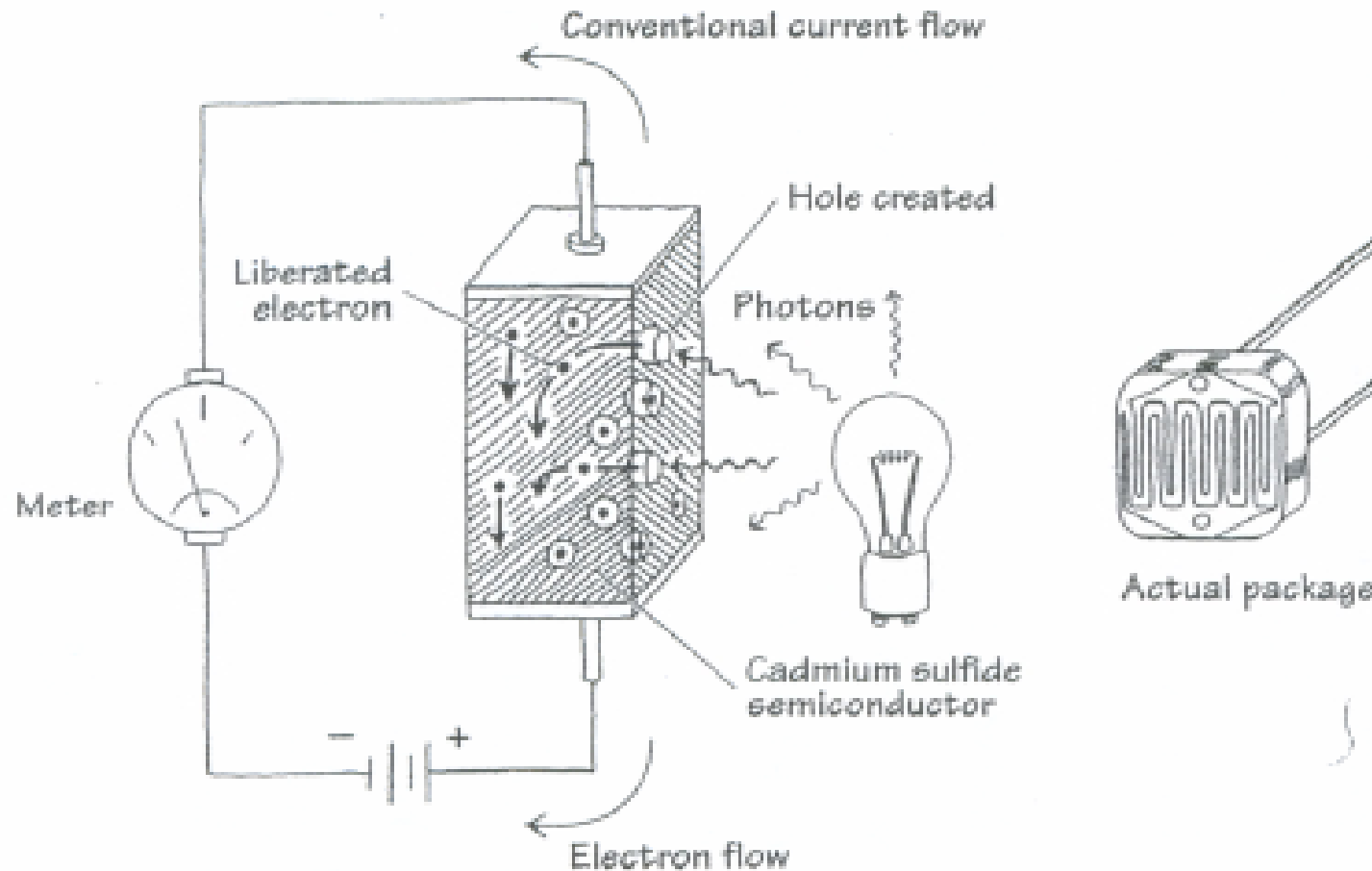


# Simple Light Meter

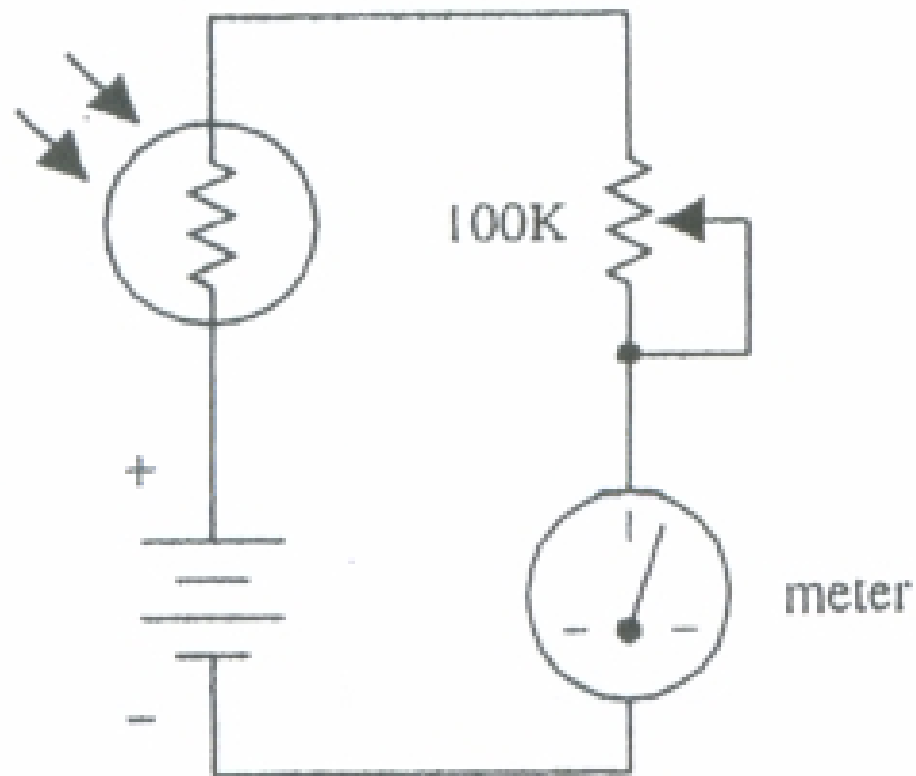


# Light Sensitive Voltage Divider

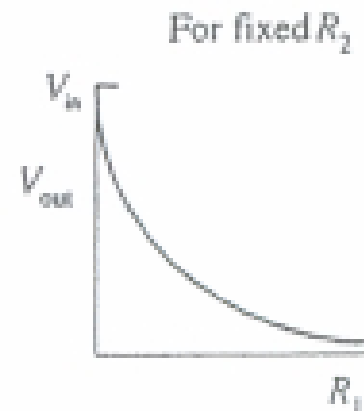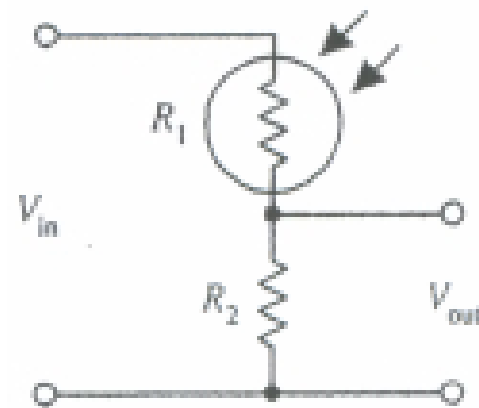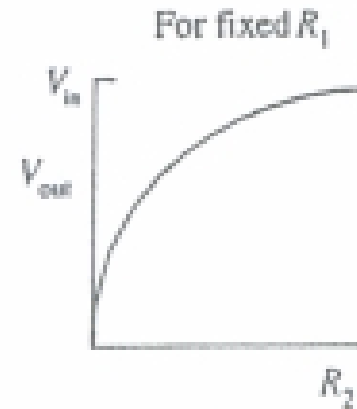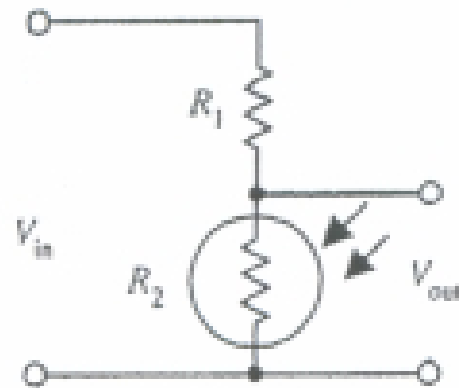

# Light Activated Relay

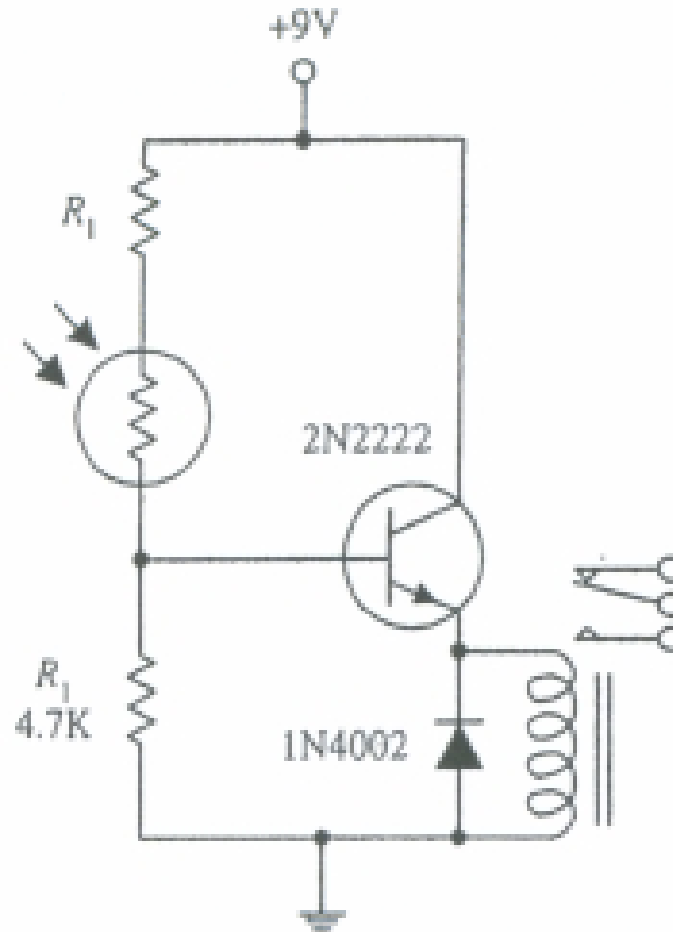


# Photoresistor with BS2

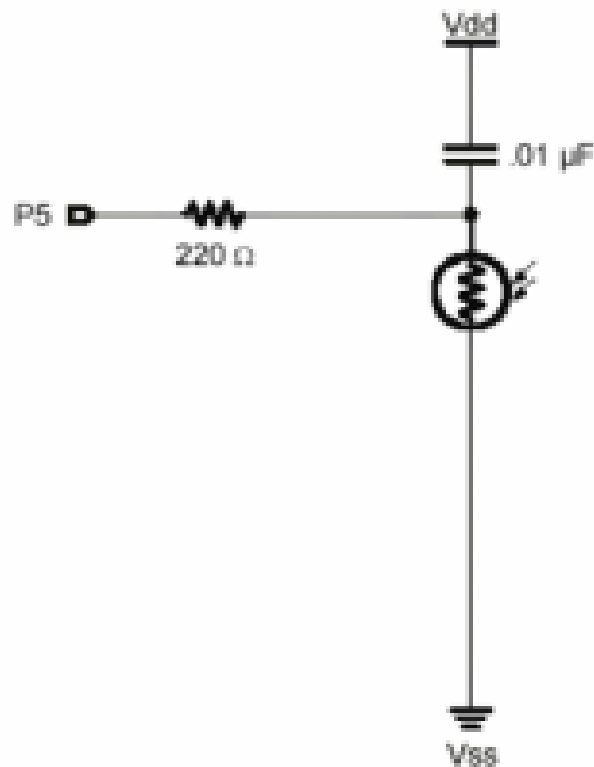

- Usually connect with a capacitor
- Use RCTime command to find out light intensity




# RC Circuit

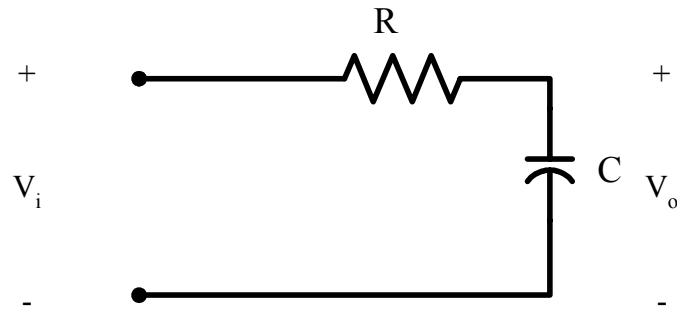


$$\frac{V_o(s)}{V_i(s)} = \frac{1}{RCs + 1}$$

**RC is time constant,  $\tau$**

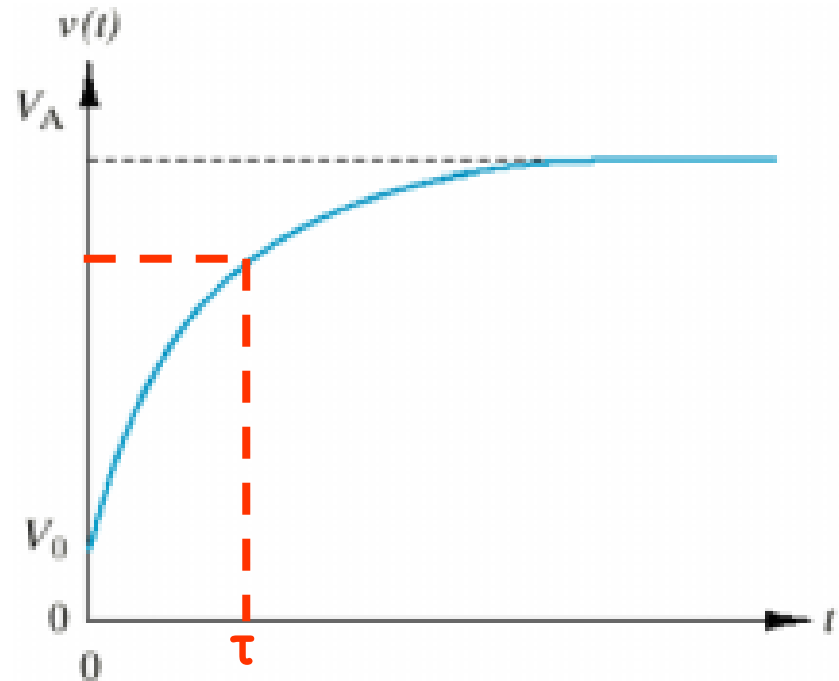**63.2% of the voltage output  
in steady state ( $V_A$ )**




# Rctime with BS2

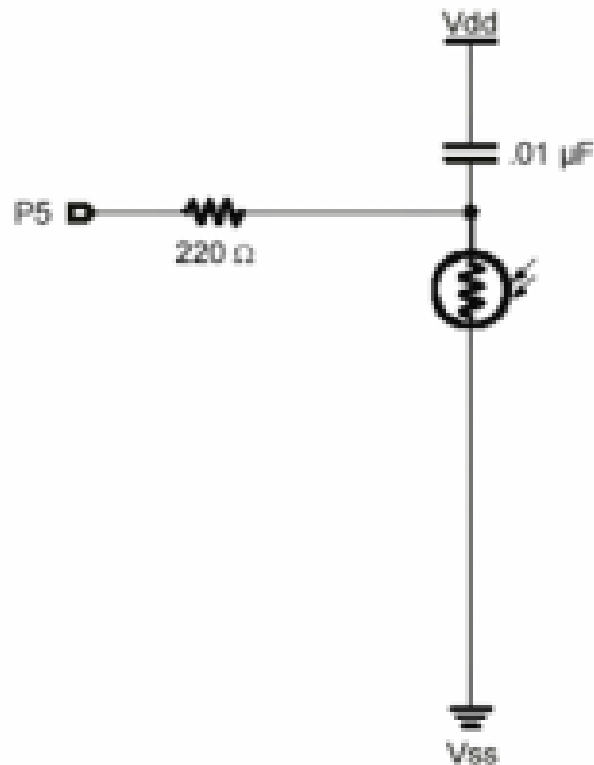


- Software version of analog to digital converter
- Pbasic rctime command
  - Rctime Pin#, state, variable
- Example code
  - High 5
  - Pause 3
  - Rctime 5,1, tau

# Photodiode

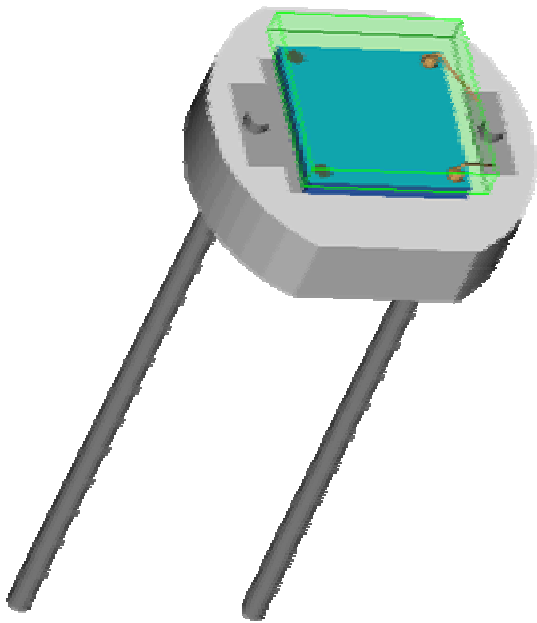


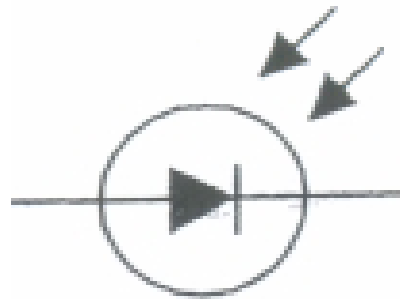- Transforms light energy to electric current
- Very linear
- More sensitive than photoresistor




**Symbol**

# Photodiode: How It Works

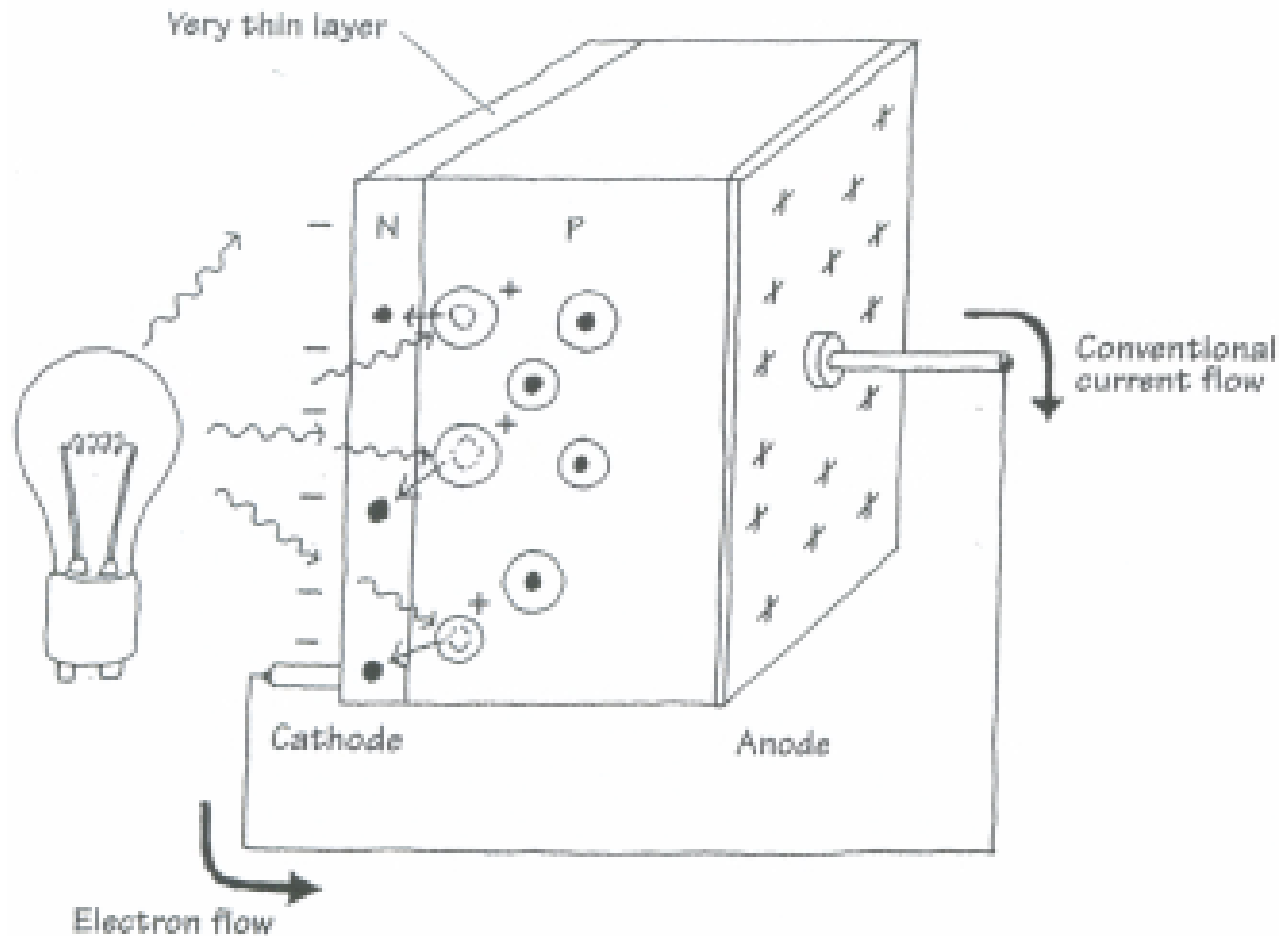


# Photodiode Applications


**Photovoltaic Current Source**

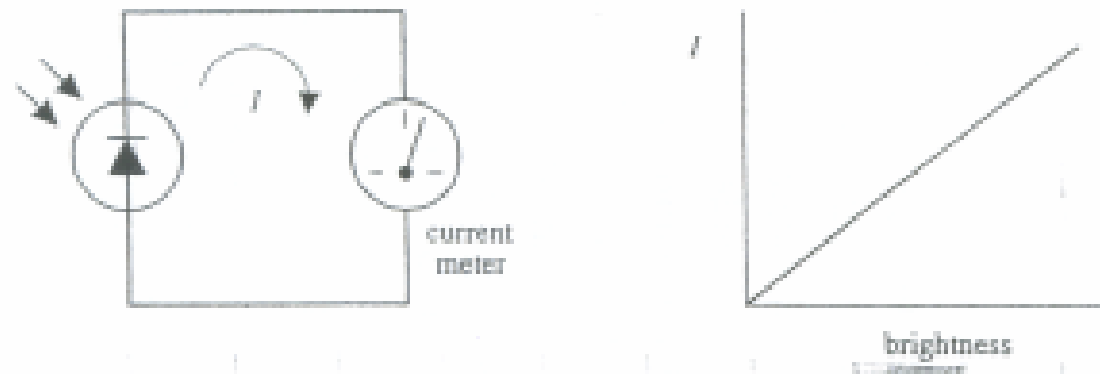

**Photoconductive Operation**

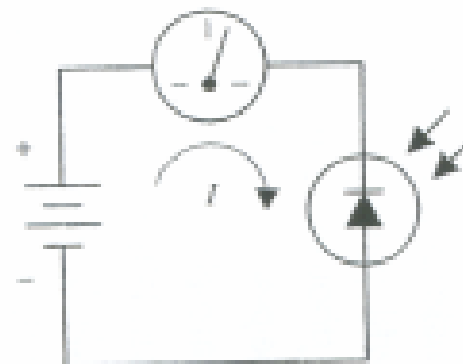


# Photodiode with BS2

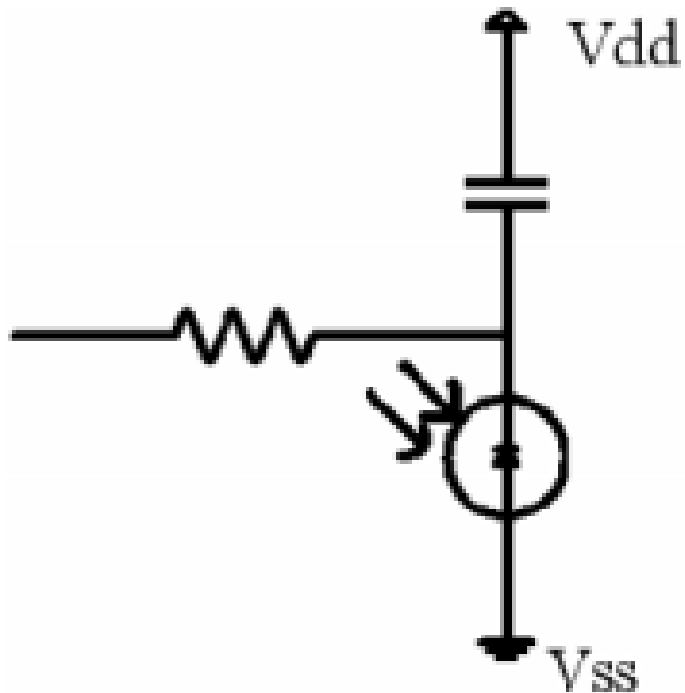


- Polarity: cathode connects to the ground
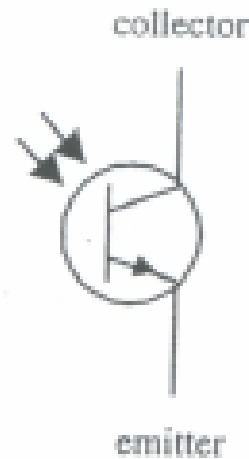
# Phototransistor

- The base lead of a BJT is replaced by a light sensitive surface




**Phototransistor**

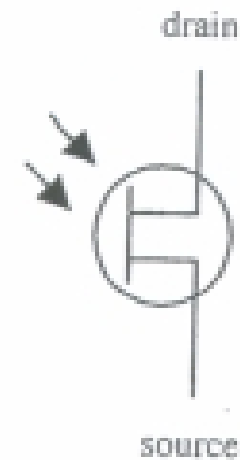

**Photo FET**


# Phototransistor: How It Works

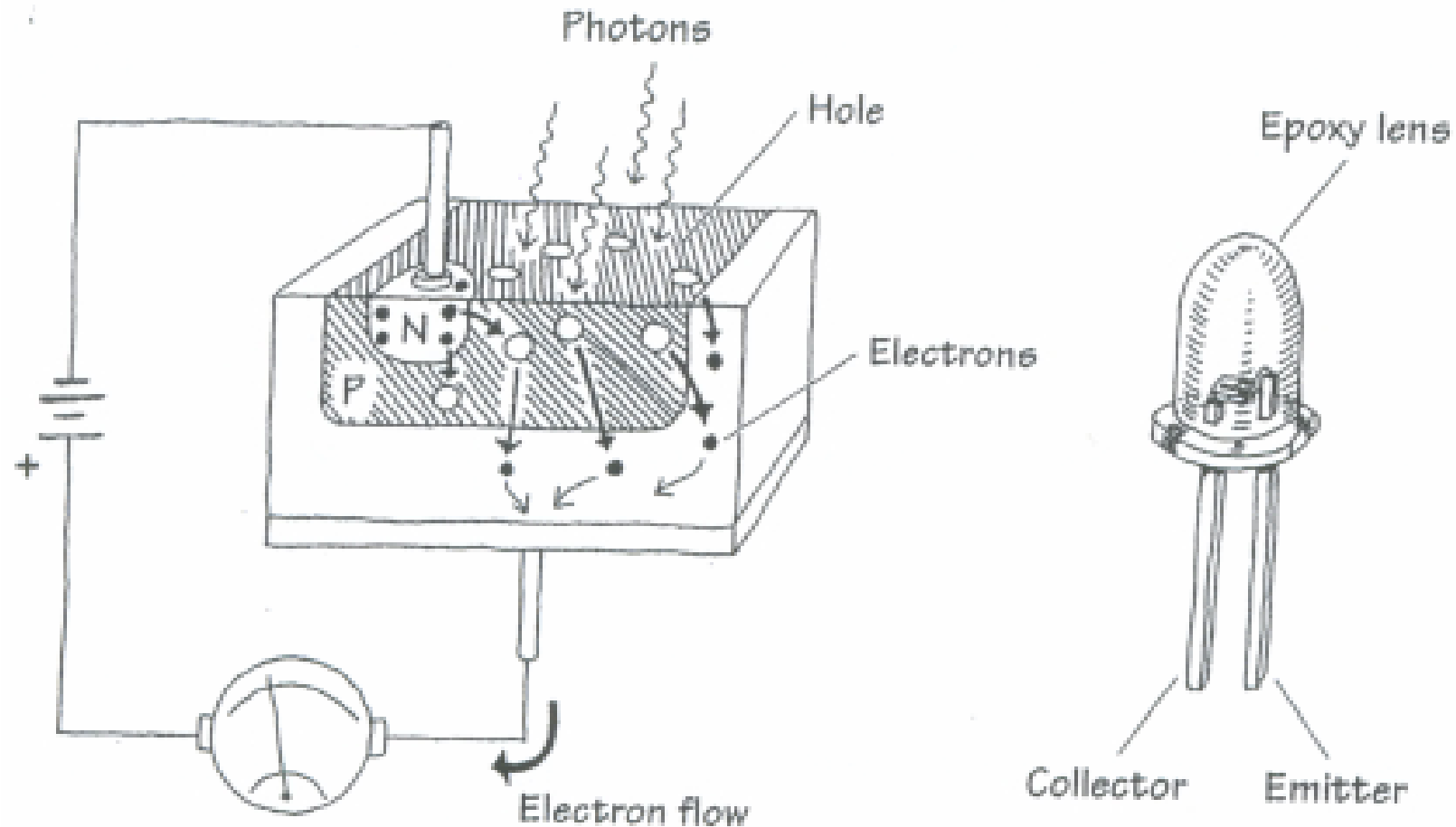




# Phototransistor Applications


LIGHT ACTIVATED

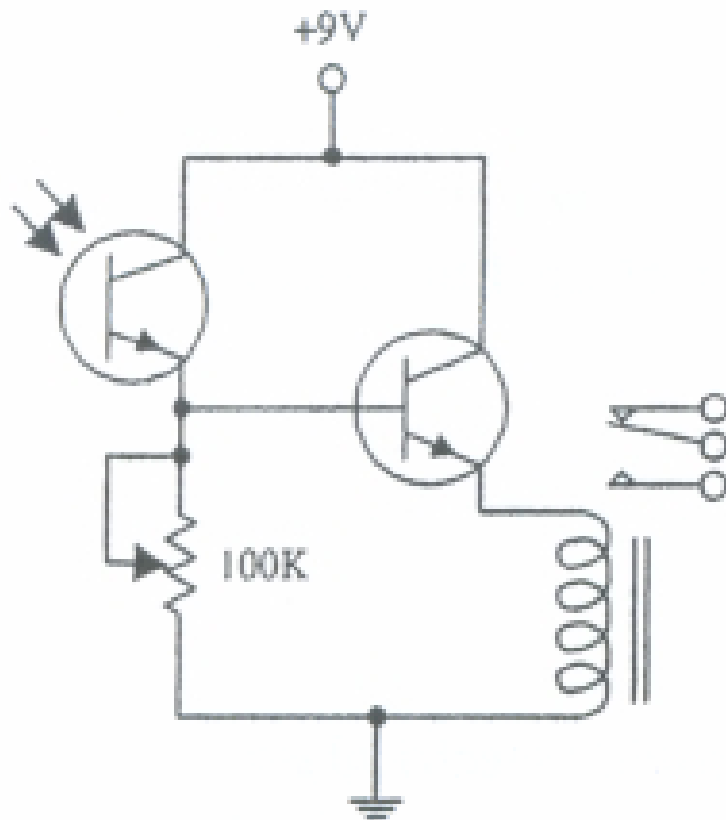


DARK ACTIVATED

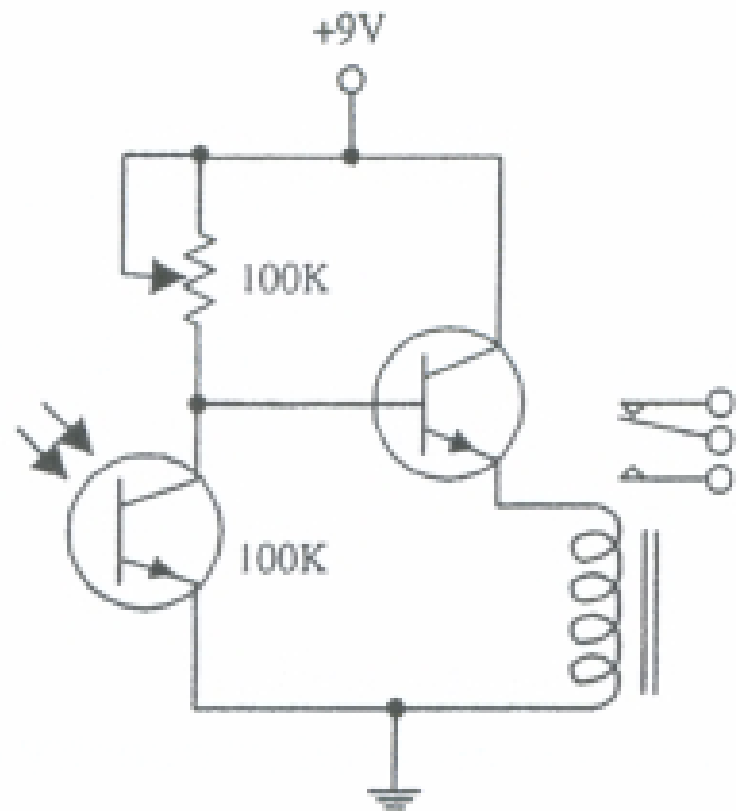

# Tachometer

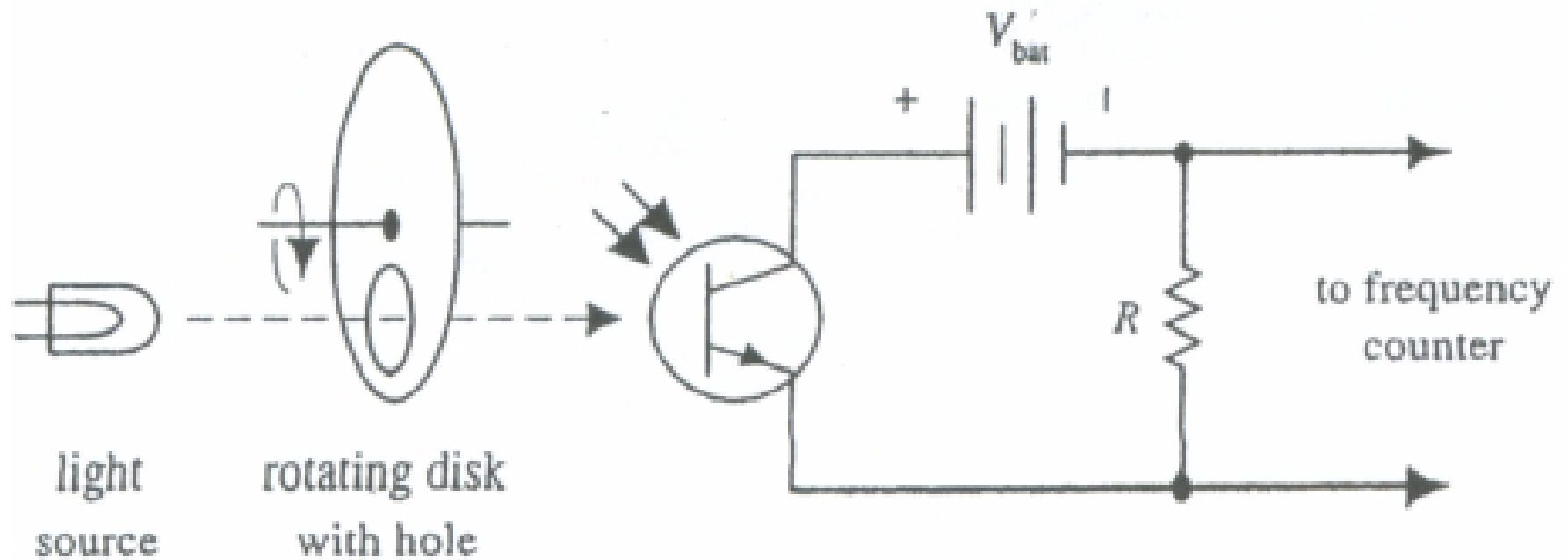


# Optoisolators 1

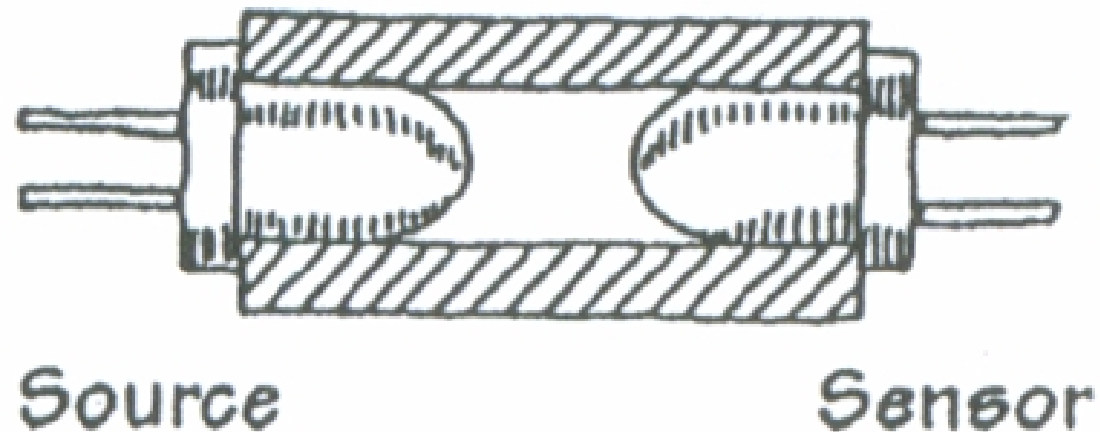


**Closed Pair**

# Optoisolators 2

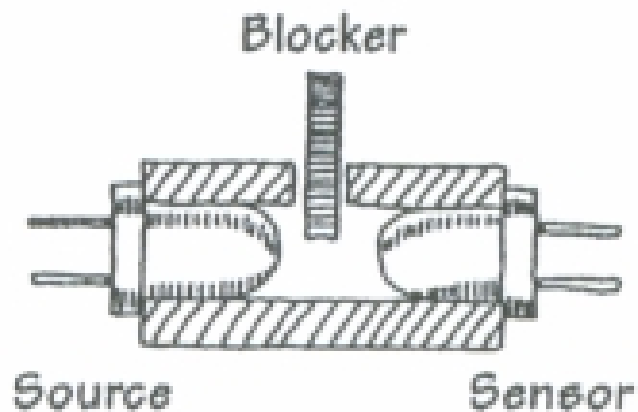


**Slotted Pair**

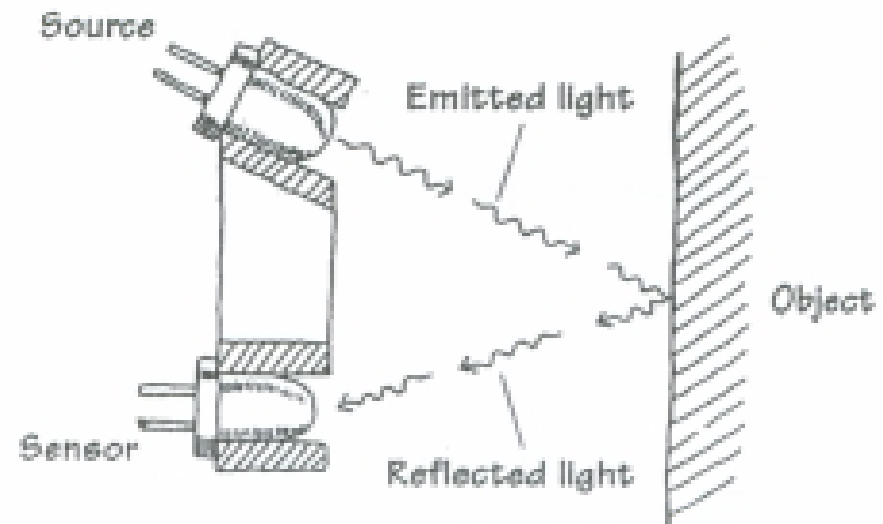

**Reflective Pair**

# Optoisolators 3

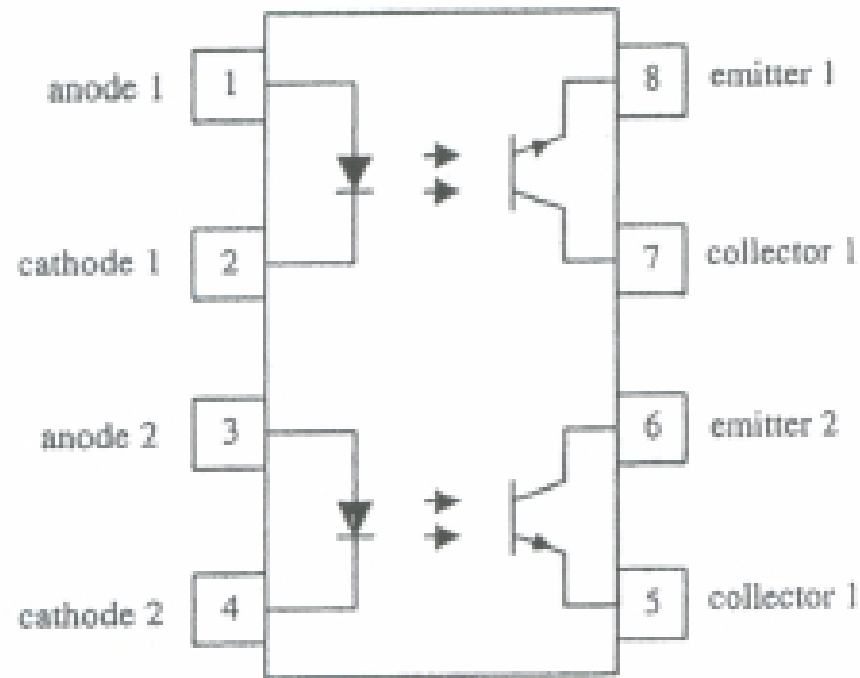


## Integrated Optoisolators

# Optoelectronic Sensors Experiments

Experiments	Chapters
What's micro controller	
Basic A and D	8
Earth measurements	4 (except DS1620)
Robotics	
StampWorks	5, 7, and 19
Others	

# Lecture 7

# Rctime with BS2

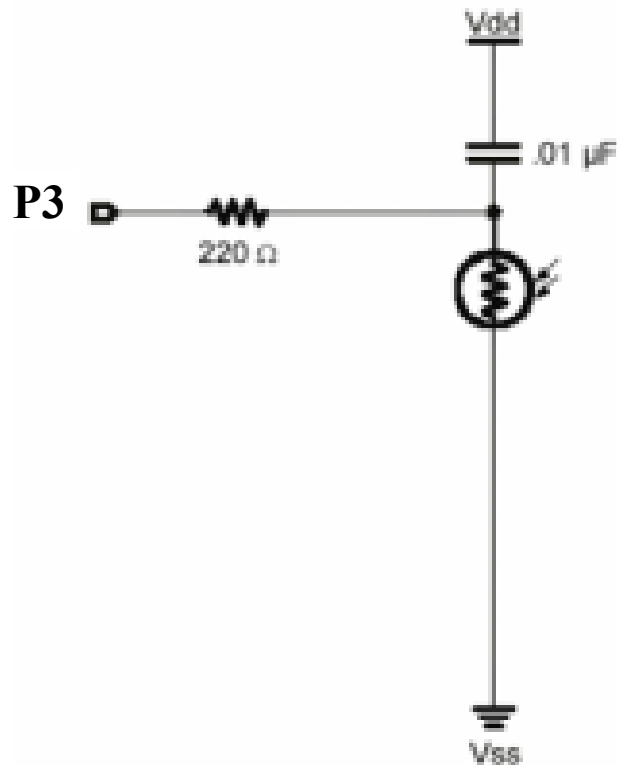


- Software version of analog to digital converter
- Pbasic rctime command
  - High 3
  - Pause 3
  - Rctime 3,1, tau




# Analog to Digital Conversion

- Process of converting an analog signal to a digital number
- Three step procedure
  - Sampling (sample and hold)
  - Quantization
  - Coding


# Sampling

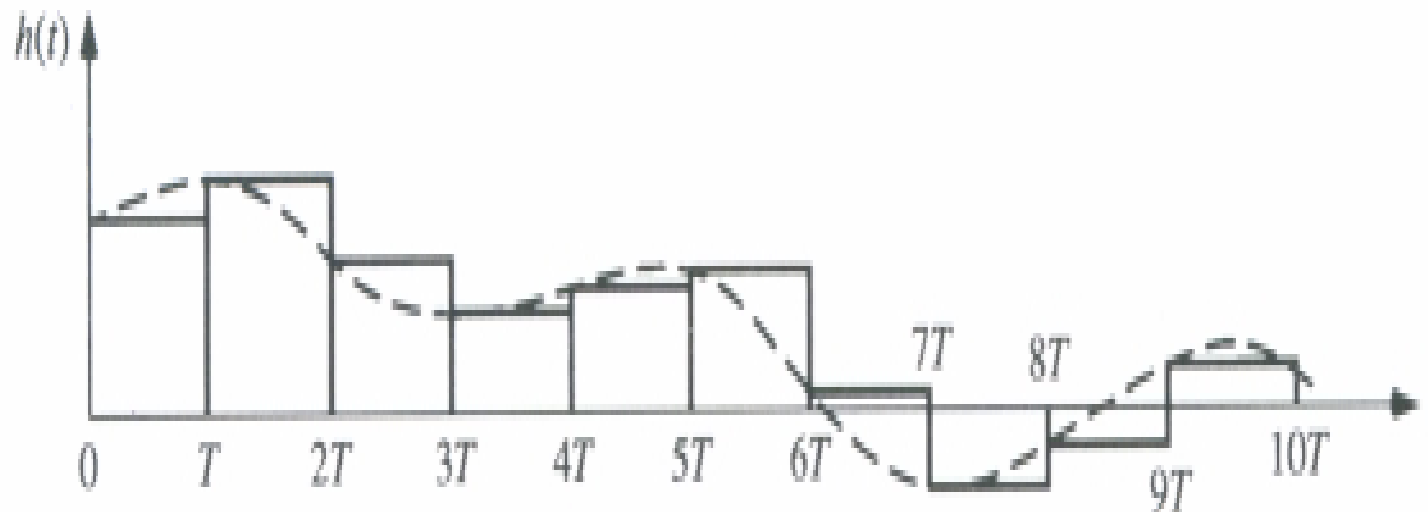

# Quantization and Coding

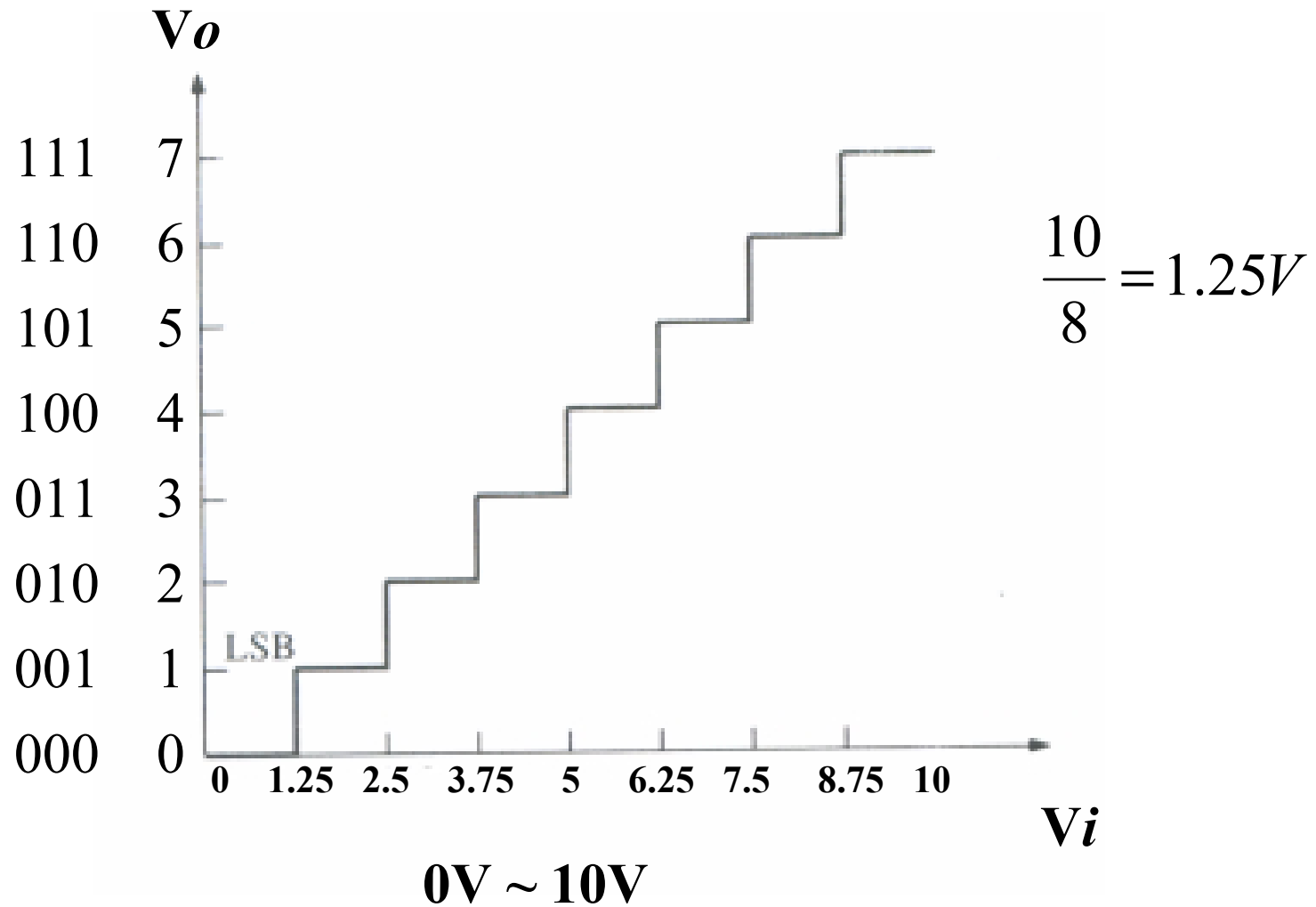


# ADC

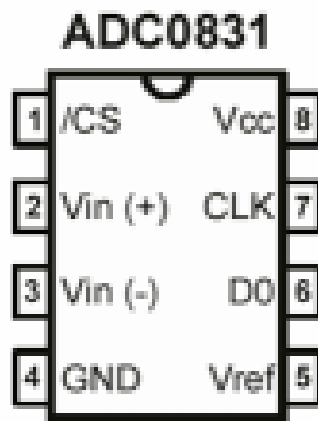

- Analog to digital converter
- 8-bit successive analog to digital converter
- 0V to 5V input range
- Single 5V power supply


# ADC Pin Description

Identifier

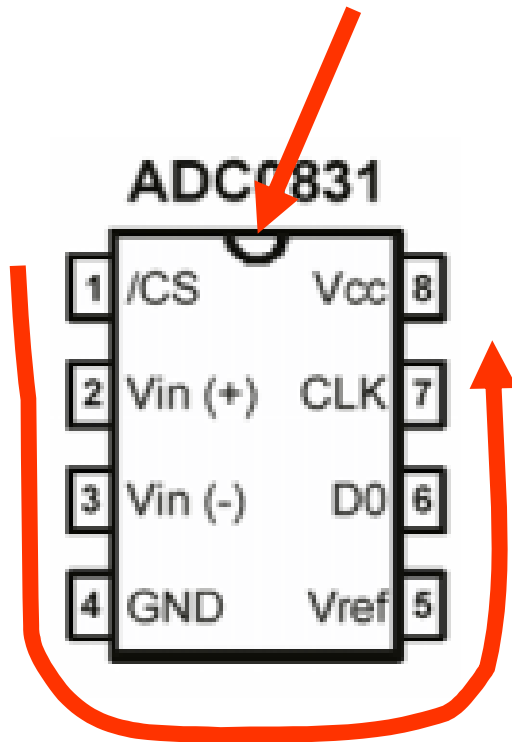


Pin	Description
Pin 1	ADC is ready to do conversion when it is low
Pin 2	0 to 5V analog input need to be digitized
Pin 3	Zero offset adjustment
Pin 4	Ground
Pin 5	Span adjustment
Pin 6	8 bit ADC output
Pin 7	Clock signal from BS2
Pin 8	Regulated 5V (Power supply)

# ADC with BS2-1

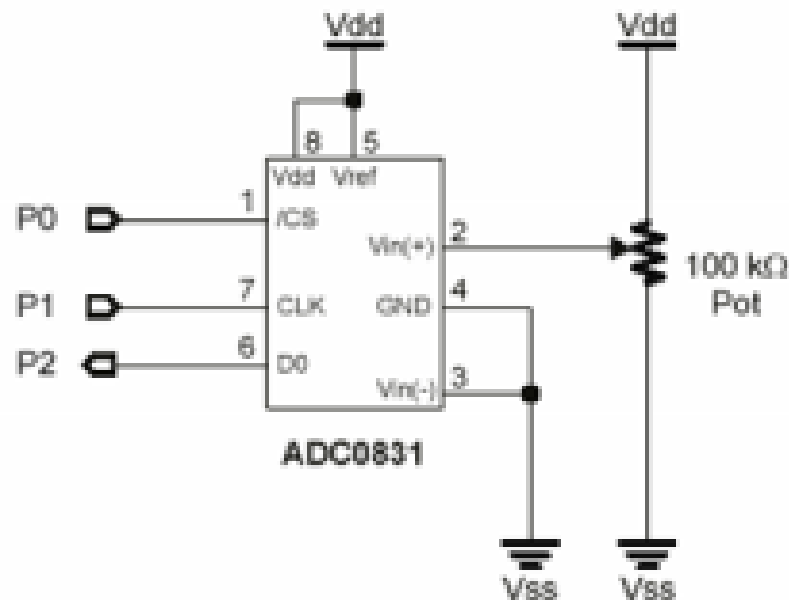

- 0V to 5V analog input using a potentiometer
- Output is from 0 to 255 – 8 bit resolution

# Sample Code for ADC 1

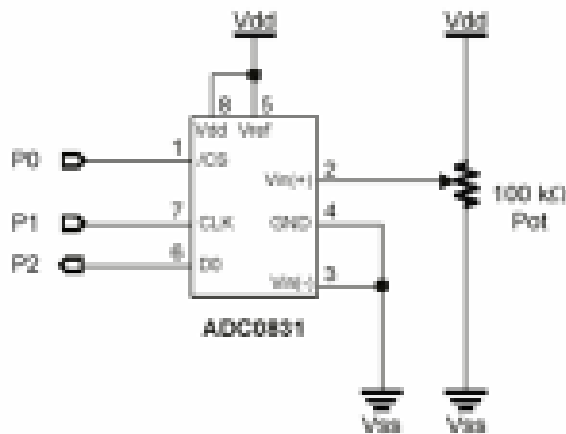

adcbits var byte

High 0

Low 0

Low 1

Pulsout 1,210

Shiftin 2, 1,MSBPOST, [adcbits\8]

**Serial  
communication**

Shiftin Data\_pin, Clock\_pin, mode, [variable\bits]

# Sample Code for ADC 2

Q var word

Debug window shows;

R var word

Q = 13 / 5  **Quotient** → Q = 2


R = 13 // 5  **Remainder** → R = 3

Debug ? Q

Debug ? R



# ADC with BS2-2

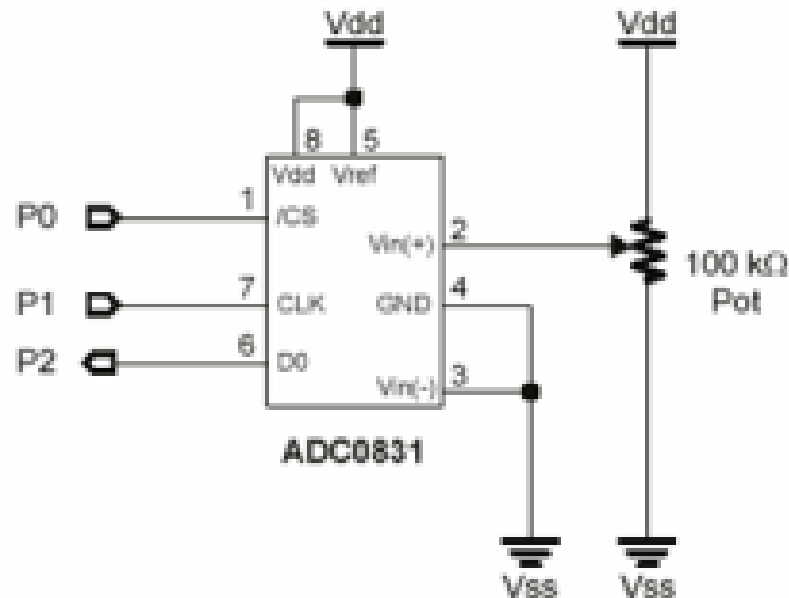


- 2V to 5V limited analog input using a potentiometer
- Output is from 102 to 255
  - 8 bits resolution

$$\frac{2V}{5V} \times 255 = 102$$

$$\frac{5V}{5V} \times 255 = 255$$

# ADC with BS2-3

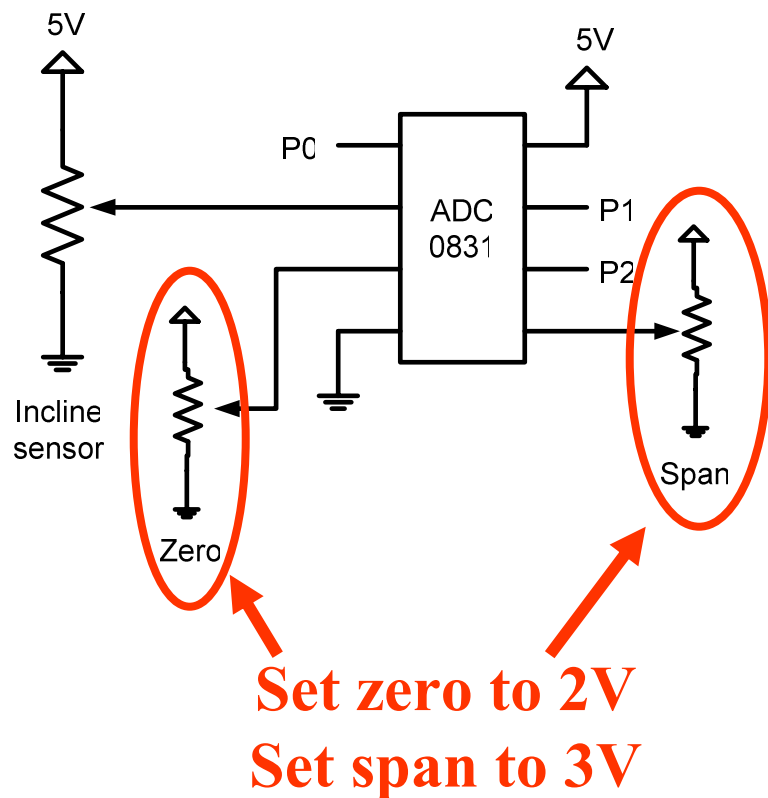


- Using two potentiometers zero and span can be adjusted to get full 8 bit resolution

$$\frac{(2-2)V}{3V} \times 255 = 0$$

$$\frac{(5-2)V}{3V} \times 255 = 255$$

# ADC with BS2-4

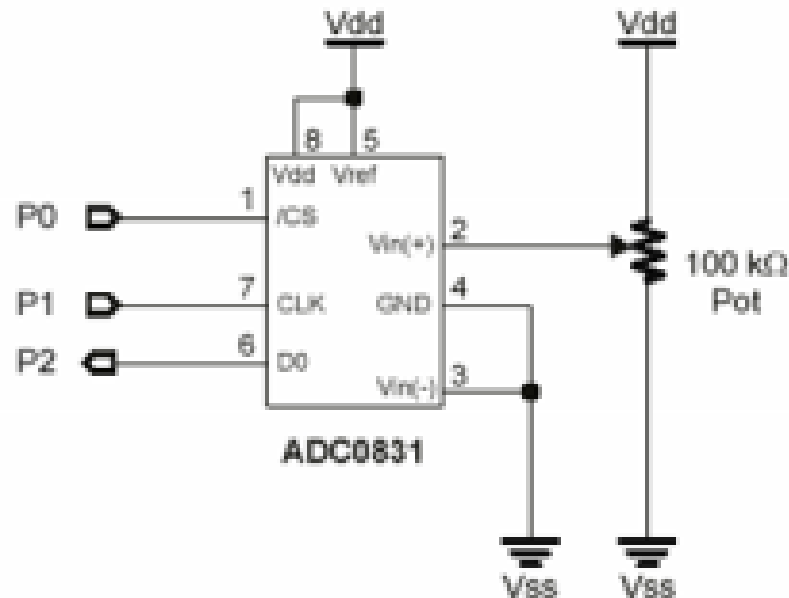


- 0V to 4V limited analog input using a potentiometer
- Output is from 0 to 204
  - 8 bits resolution

$$\frac{0V}{5V} \times 255 = 0$$

$$\frac{4V}{5V} \times 255 = 204$$

# ADC with BS2-5

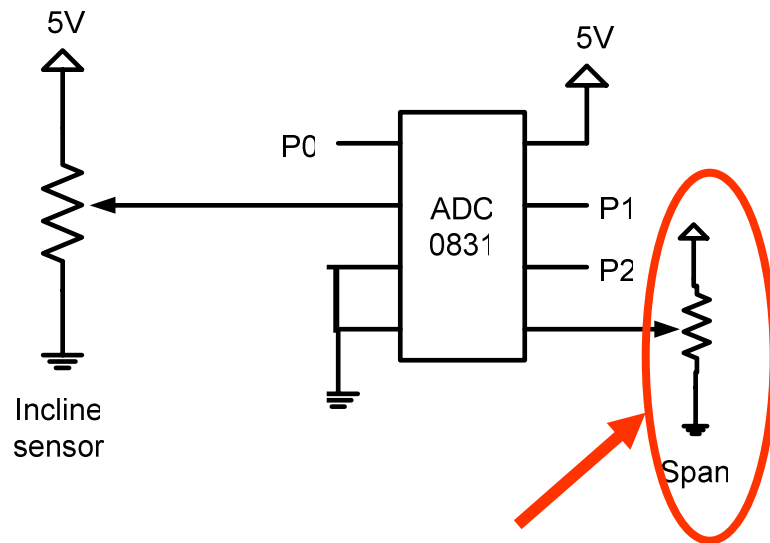


**Set to 4V**

- Using another potentiometer to span can be adjusted to get full 8 bit resolution

$$\frac{0V}{4V} \times 255 = 0$$

$$\frac{4V}{4V} \times 255 = 255$$

# ADC with BS2-6

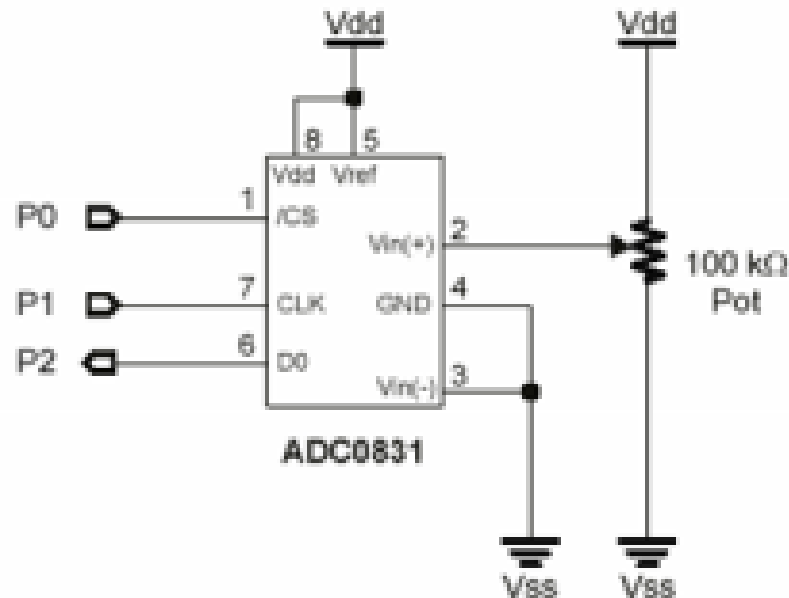


- 2V to 4V limited analog input using a potentiometer
- Output is from 102 to 204
  - 8 bits resolution

$$\frac{2V}{5V} \times 255 = 102$$

$$\frac{4V}{5V} \times 255 = 204$$

# ADC with BS2-7

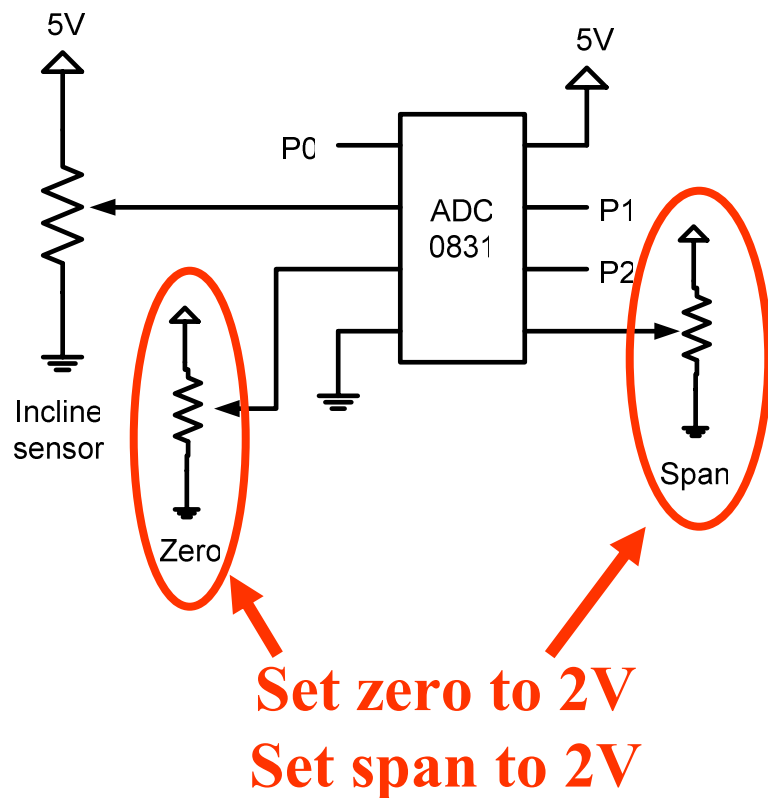

- Using 2 potentiometers zero and span can be adjusted to get full 8 bit resolution

$$\frac{(2-2)V}{(4-2)V} \times 255 = 0$$

$$\frac{(4-2)V}{(4-2)V} \times 255 = 255$$

# ADC0831 Experiments

Experiments	Chapters
What's micro controller	
Basic A and D	1, 3
Earth measurements	
Robotics	
StampWorks	27
Others	

# Lecture 8



# Servo Motor

- DC motors with feedback position control
- As long as the coded signal exists on the input line, the servo will maintain the angular position of the shaft
- As the coded signal changes, the angular position of the shaft changes




# Servo Motor: How It Work?

- Consists of some control circuit and a potentiometer
- This potentiometer allows the control circuitry to monitor the current angle of the servo motor
- If the shaft is at the correct angle, then the motor shuts off
- If the circuit finds that the angle is not correct, it will turn the motor in the correct direction until the angle is corrected




# Servo Motor Wiring

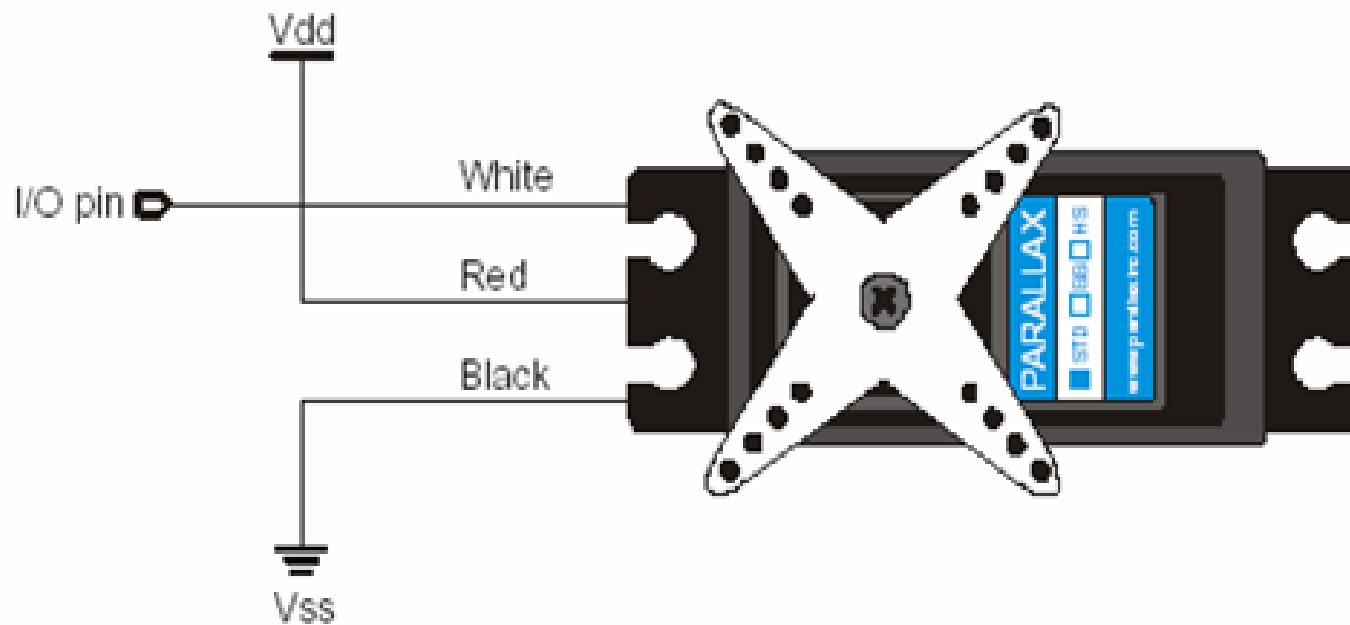

# Servo Motor with BS2



Only when you use  
AA battery pack

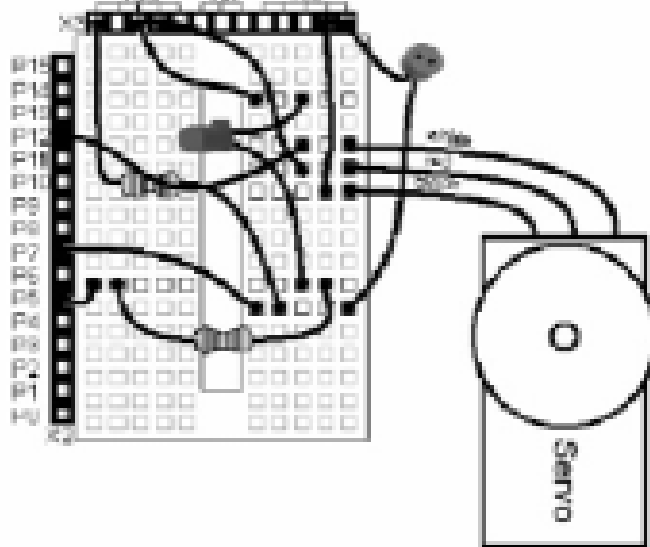

2 servo motors only

Need another capacitor for additional servo motors

# Sample Code

X var byte

Output 12

Here:

For X = 1 to 100

Pulsout 12, 500

Pause 10

Next

Pause 500

For X = 1 to 100

Pulsout 12, 1000

Pause 10

Next

Pause 500

Goto Here


Pulsout Pin #, Duration  
12 is pin number of BS2  
500 means 1milisecond



# PWM

- Pulse-Width-Modulation
- An efficient method to deliver controlled amount of power to loads such as motors
- Use square voltage pulses
- Modulation
  - Process of controlling the duty cycle of square wave
- Pulse-width-modulator
  - The circuit used to achieve modulation tasks


# PWM - Duty Cycle

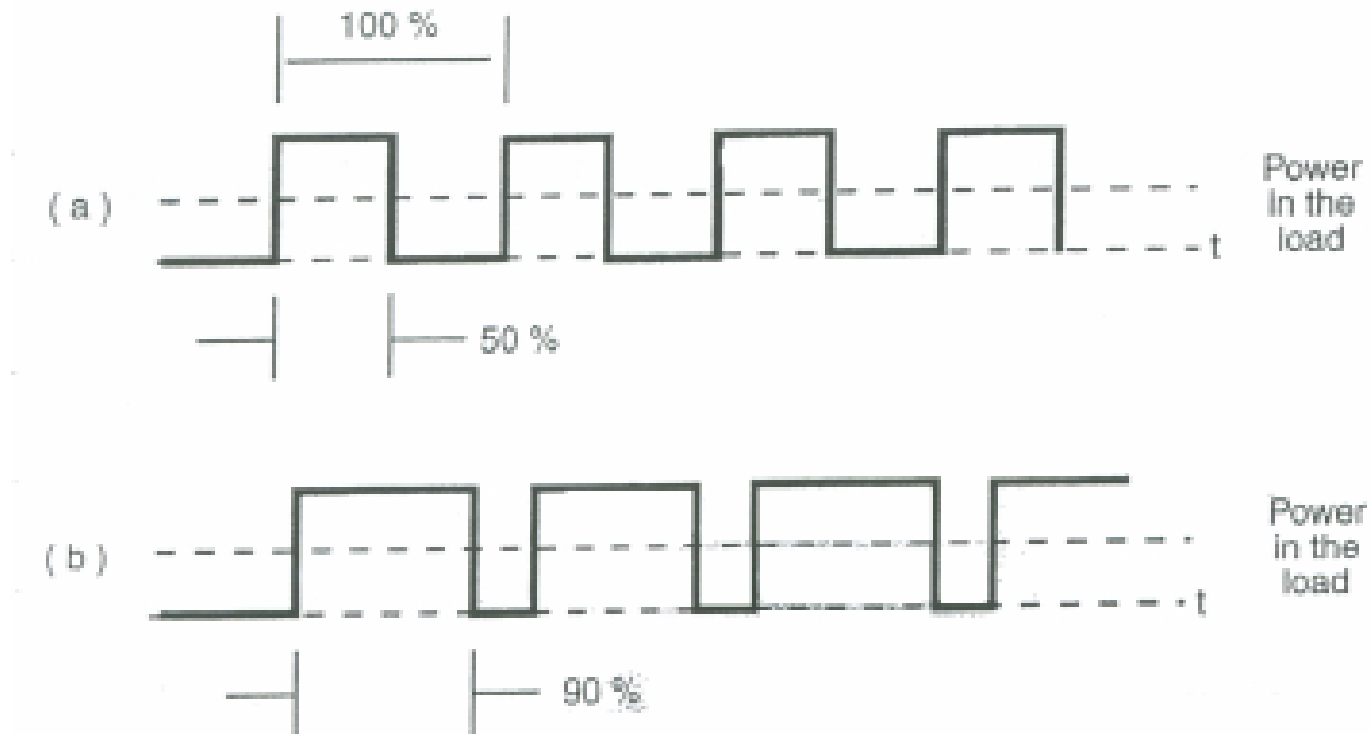

The power depends on the pulse width

**Amount of power delivered to load depending on duration of each pulse**

# The Basic PWM Control

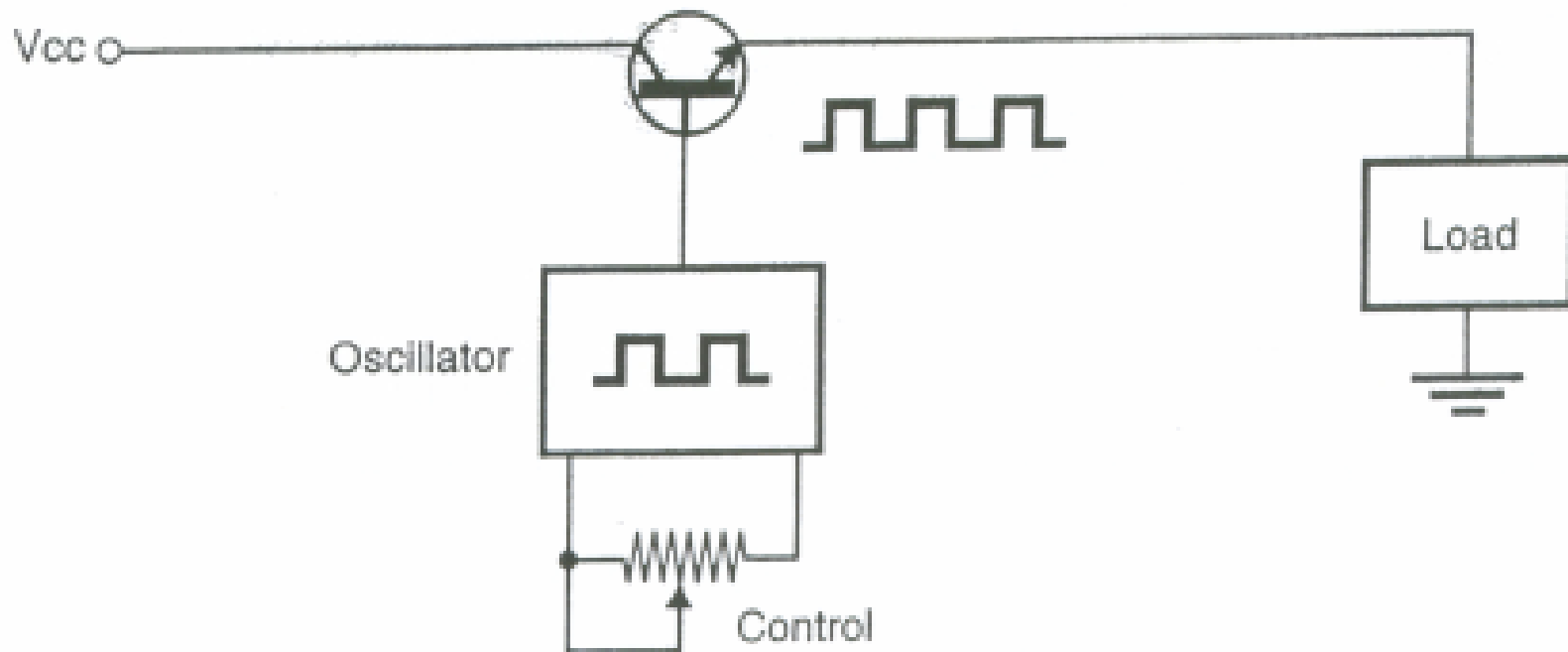




# Stepper Motor

- Do not spin freely with just power
- Driven by the interaction (attraction and repulsion) of magnetic fields
- With proper sequence of the on-off pattern of the magnetic fields, the stepper turns (when it's not, the stepper sits and quivers).



# Stepper Motor with BS2

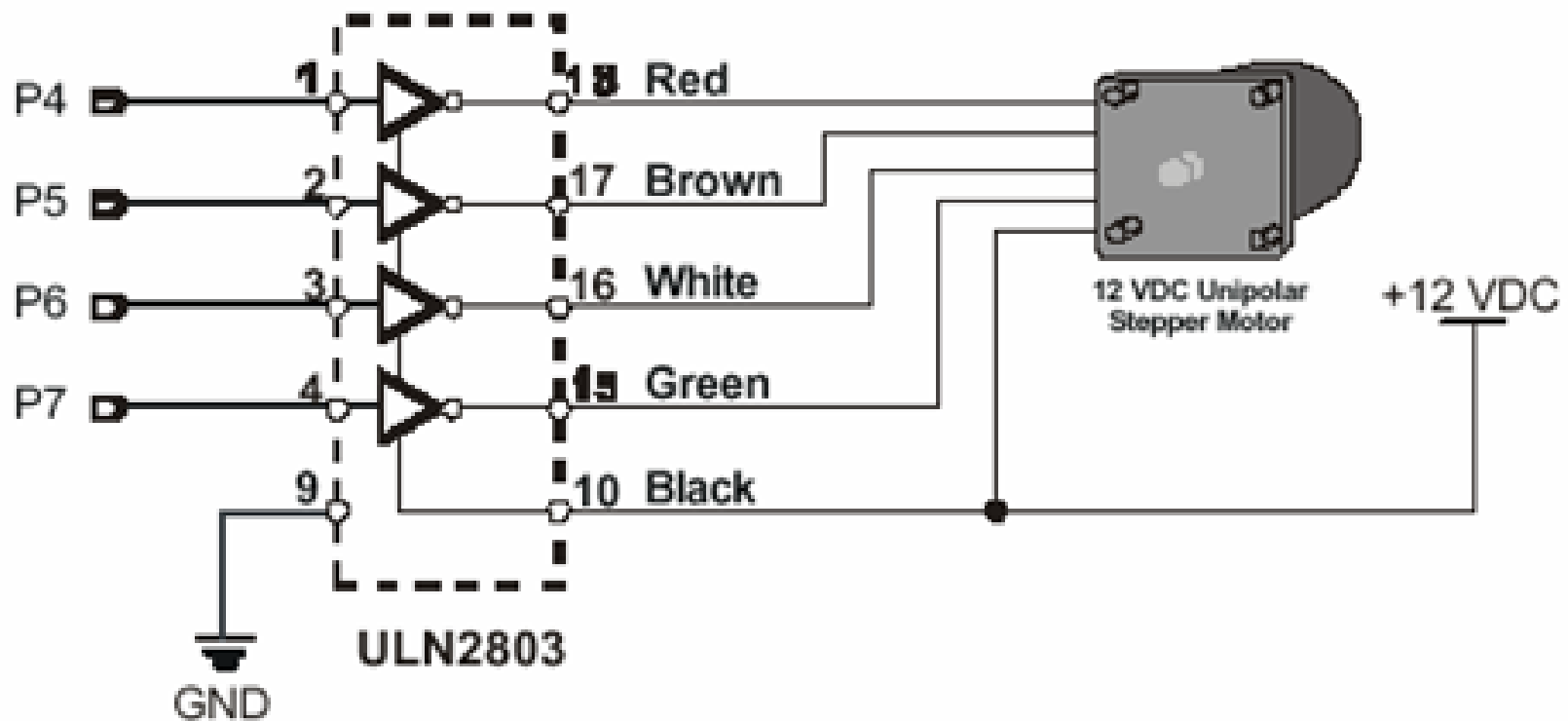

**ULN 2803 high-current transistor driver**

# Motor Experiments

Experiments	Chapters
What's micro controller	3 and 4
Basic A and D	
Earth measurements	
Robotics	
StampWorks	25 and 26
Others	