

Lecture 9

Pulse Generation


- Pulsout
 - Software version of pulse generation
 - Pulsout pin, Period
 - Pin: specified I/O pin from 0 to 15
 - Period: 2 μ sec per each unit
- 555 Timer
 - Hardware version of pulse generation
 - BS2 can do other works
 - Microcontroller is not necessary

555 Timer


- **Highly stable devices for generating accurate time delay or oscillation**
- **Not programmable**
- **Controlled by resistors and capacitors**
- **Applications**
 - **Pulse generation**
 - **PWM**
 - **Time delay generation**




555 Timer Block Diagram

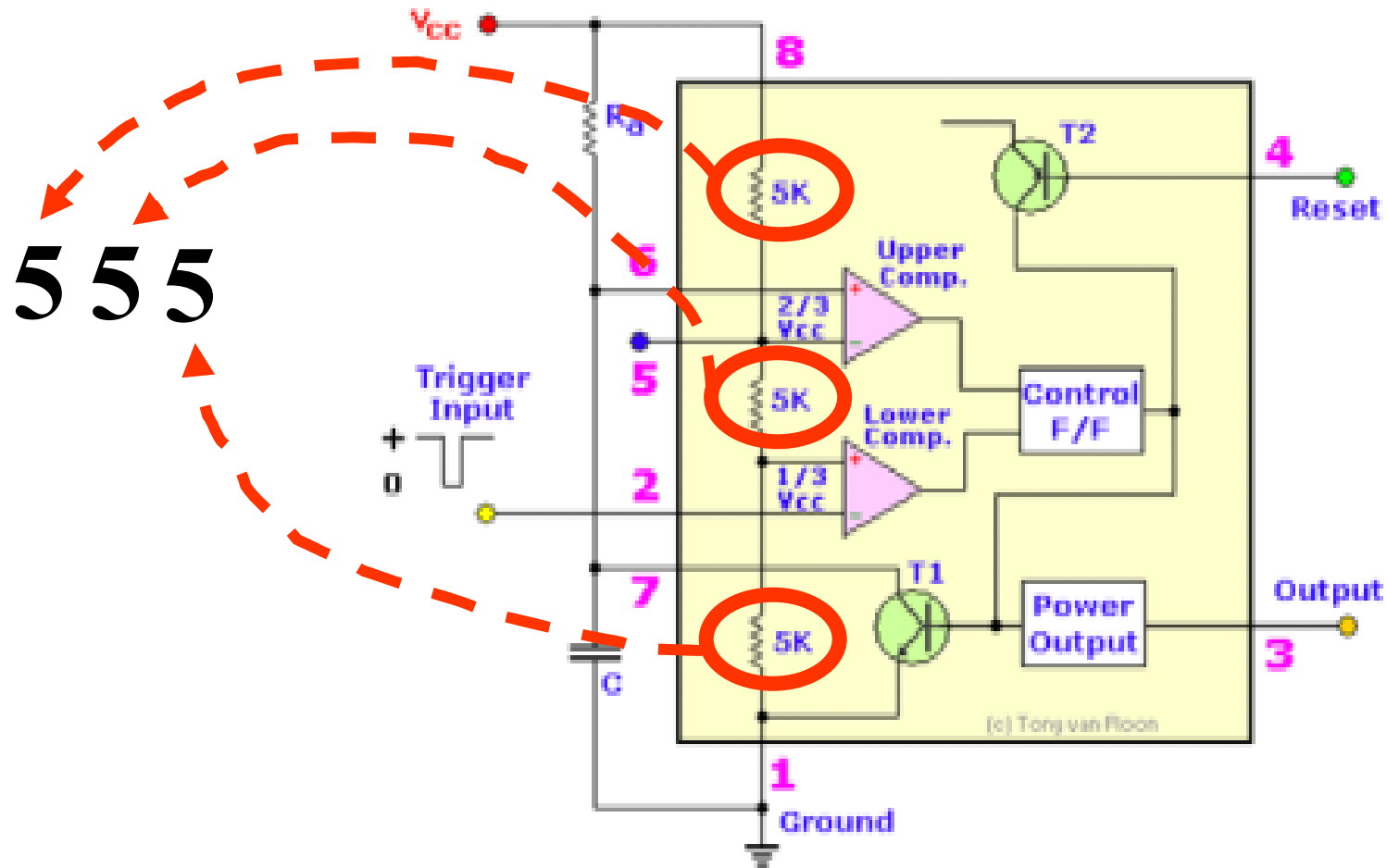


Connection Diagram

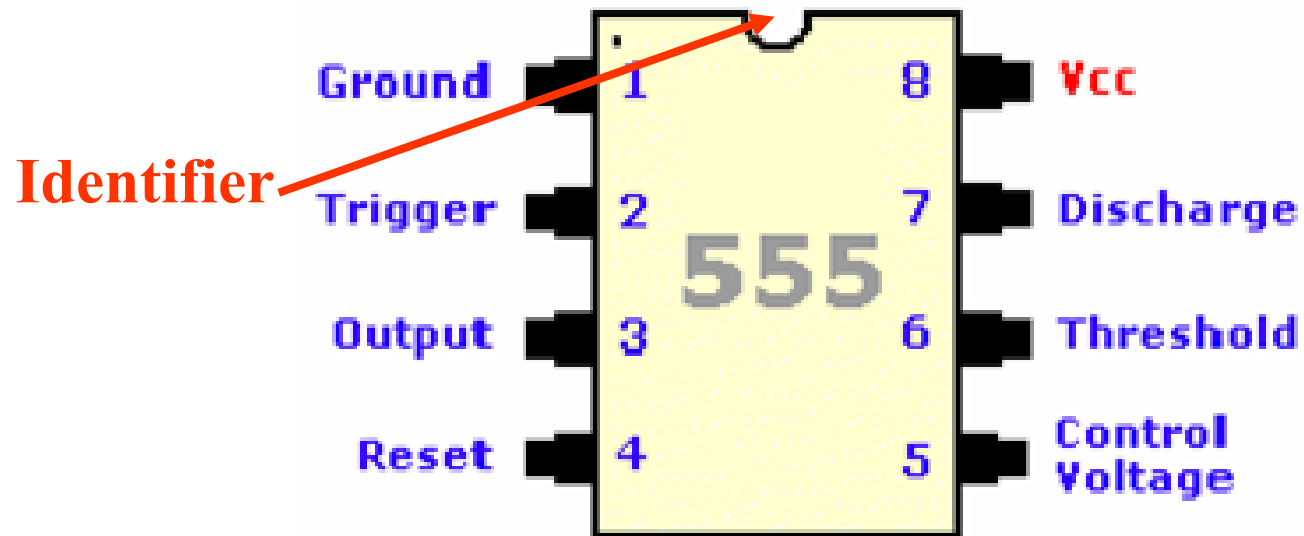


555 Timer without BS2

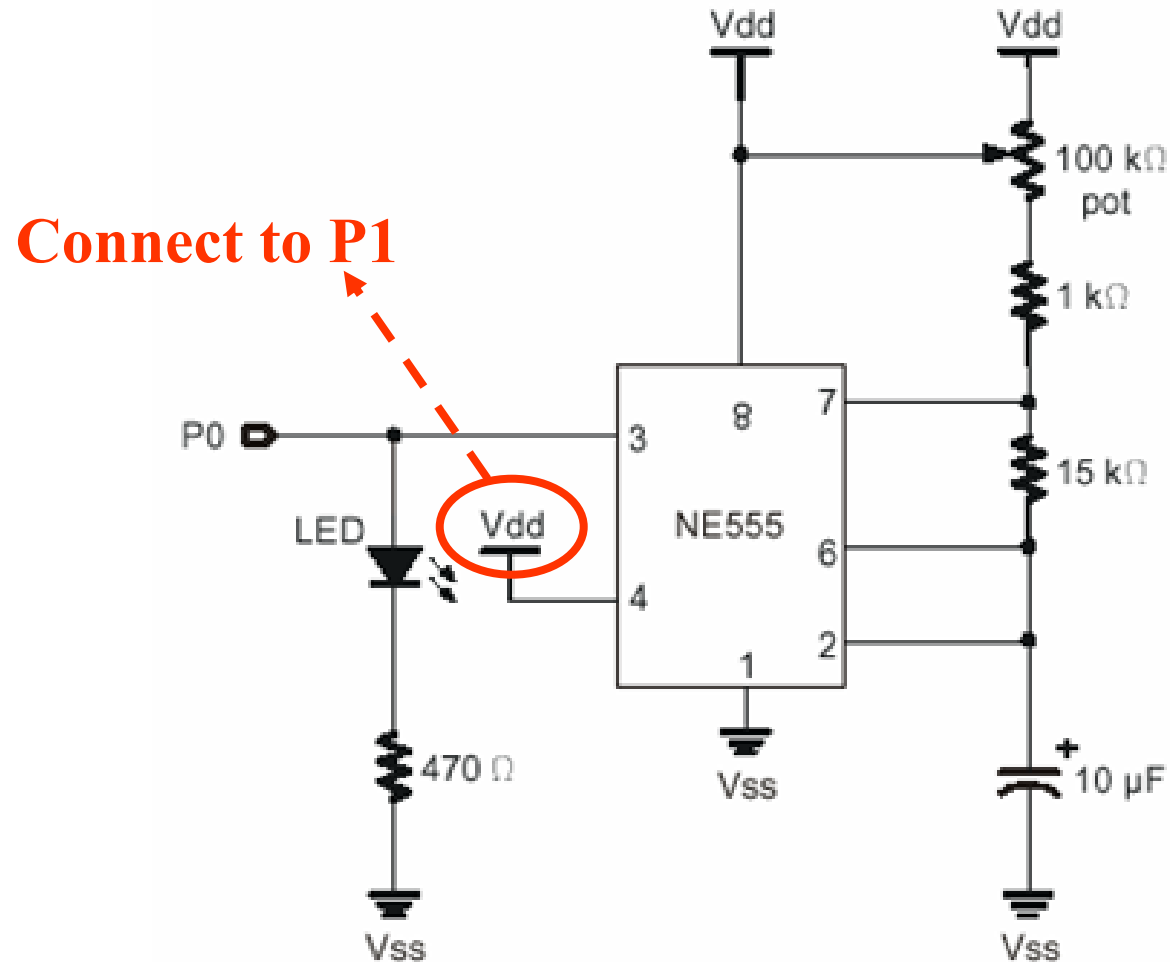

555 Timer with BS2

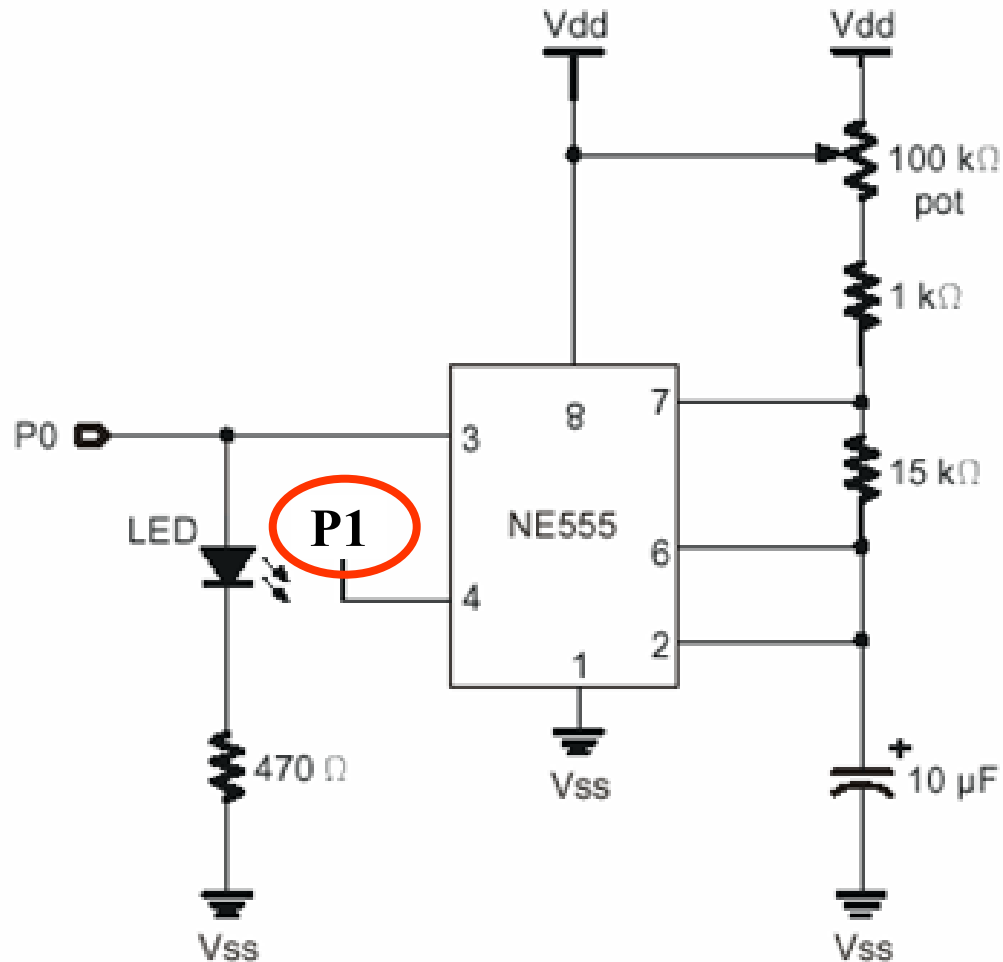

Astable Operation 1

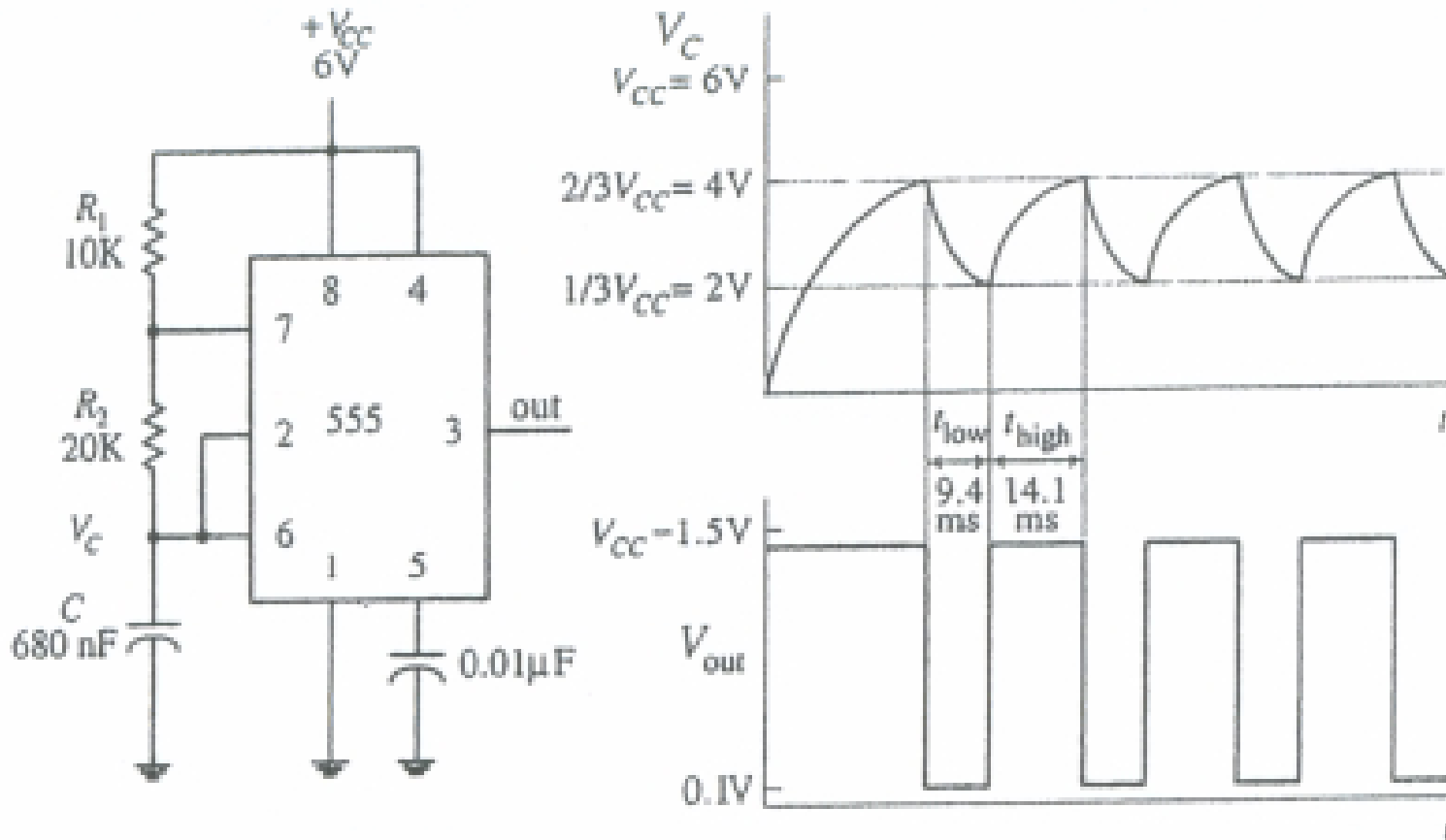



Calculation of Duty Cycle

$$t_{low} = 0.693 R_2 C$$


$$t_{high} = 0.693 (R_1 + R_2) C$$

$$\text{Duty cycle} = \frac{t_{high}}{t_{high} + t_{low}}$$

$$f = \frac{1}{t_{high} + t_{low}}$$

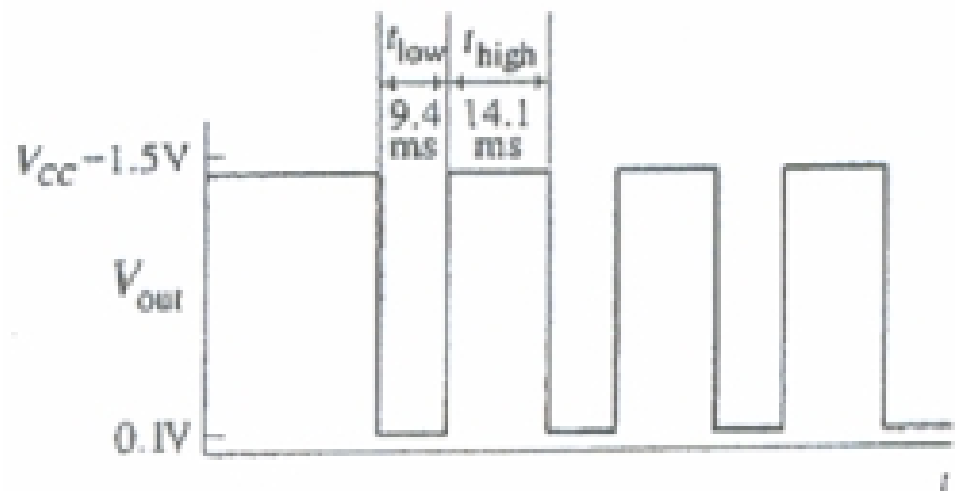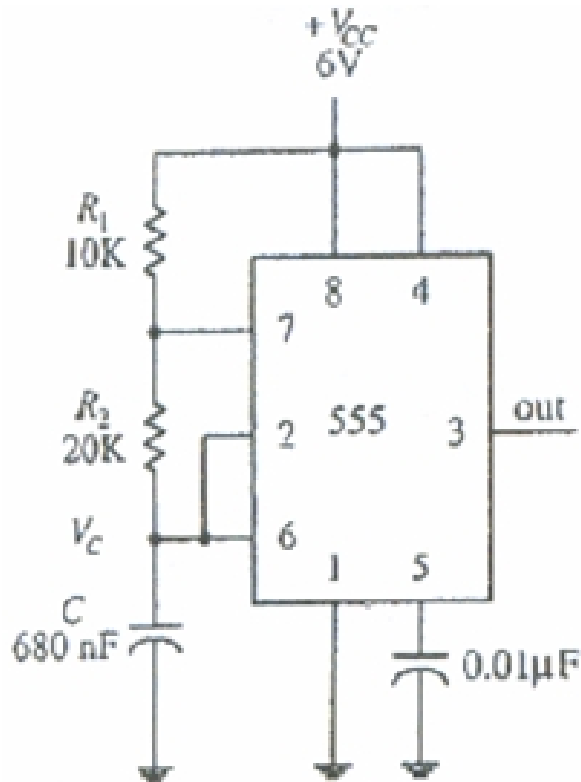

Calculation of Duty Cycle

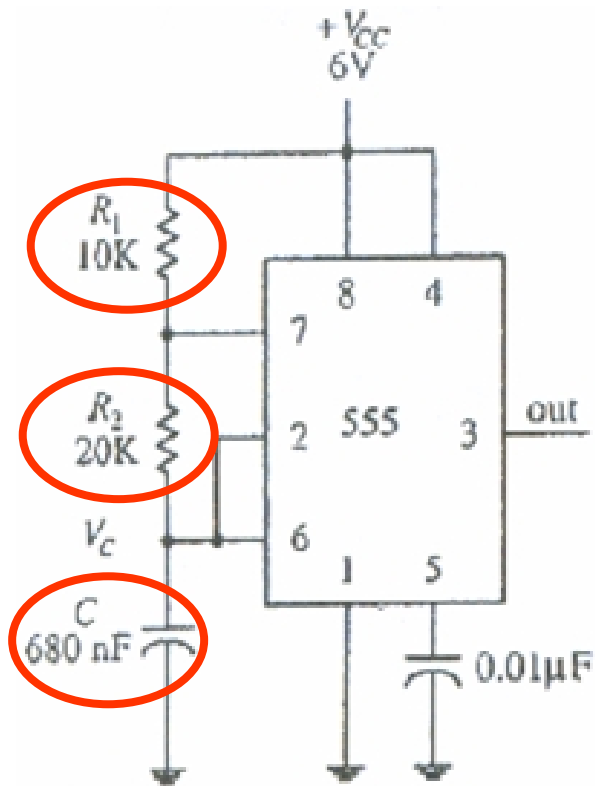

$$t_{low} = 0.693(20K)(680nF) = 9.6ms$$


$$t_{high} = 0.693(10K + 20K)(680nF) = 14.1ms$$

$$Duty\ cycle = \frac{14.1ms}{14.1ms + 9.6ms} = 0.6$$

$$f = \frac{1}{14.1ms + 9.6ms} = 42Hz$$

Astable Operation 2

Frequency vs. C , R_1 and R_2

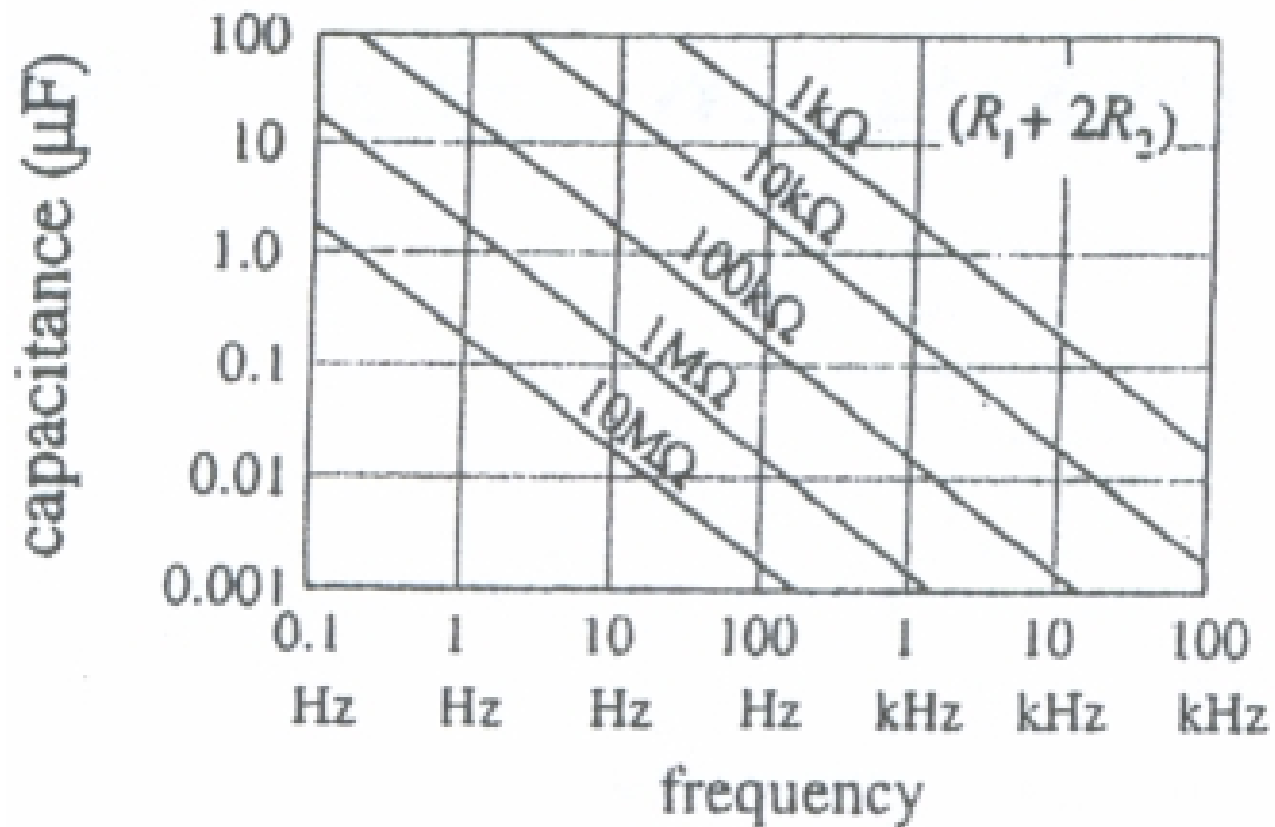

Applications 1

Dark Detector

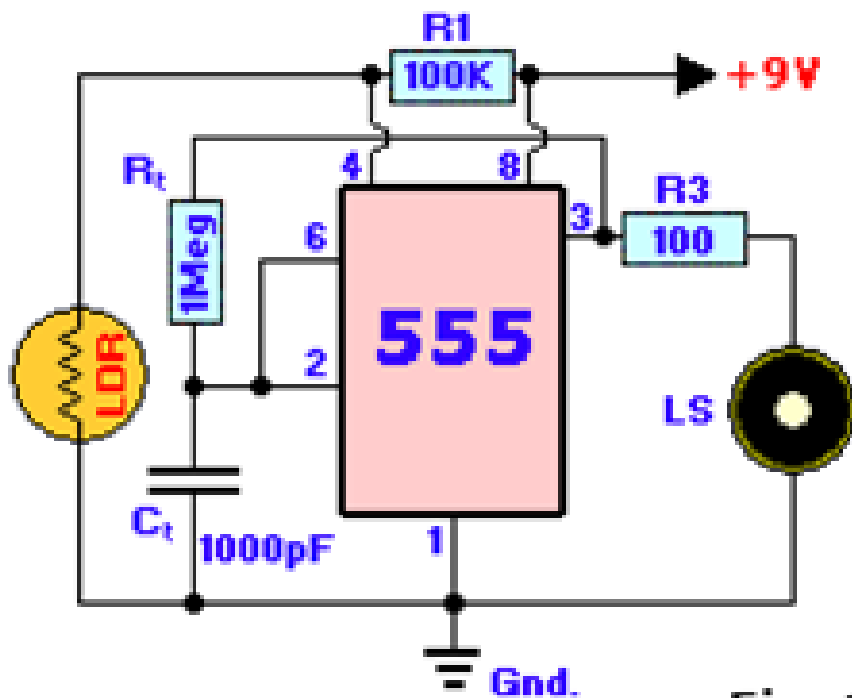


Fig. 1

- It will sound an alarm if it gets too dark all over sudden
- The LDR enables the alarm when light falls below a certain level

Applications 2


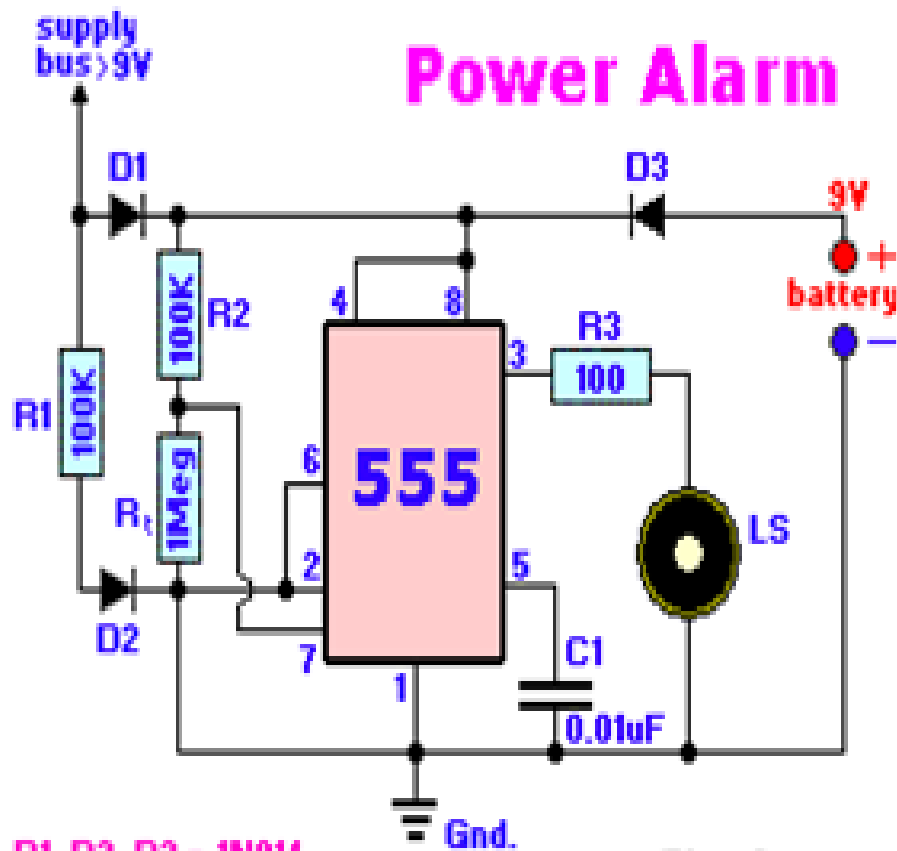


Fig. 2

- This circuit can be used as a audible 'Power-out Alarm'
- When the line voltage fails, the tone will be heard in the speaker


Applications 3

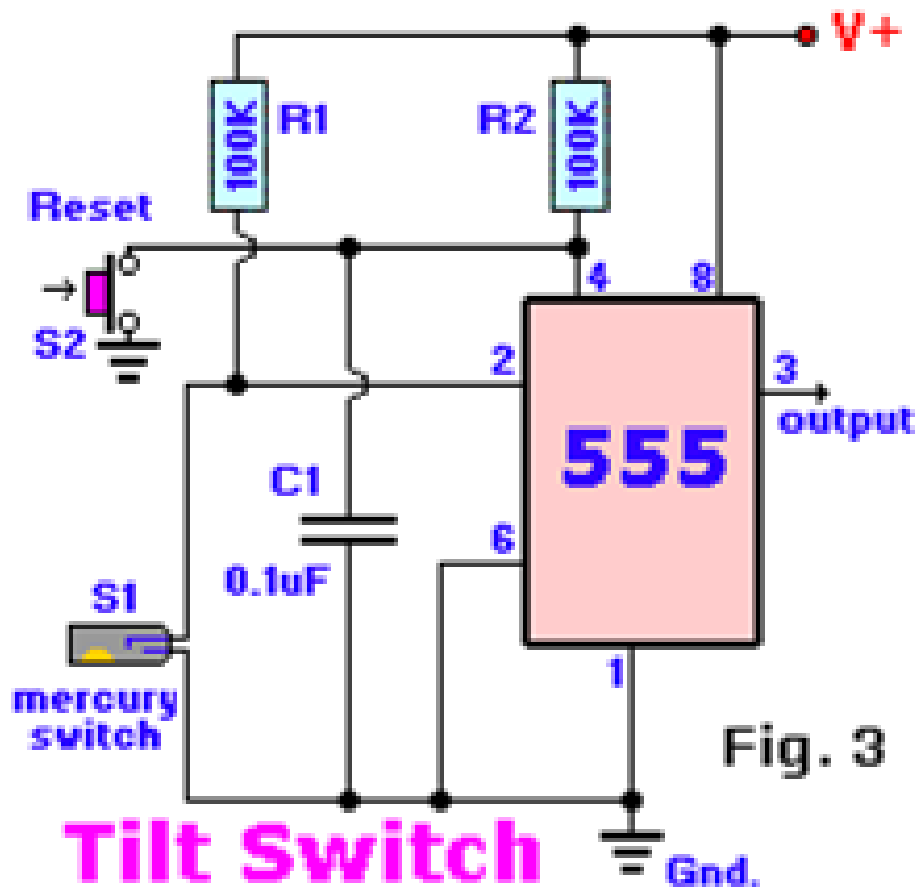

- Actually really a alarm circuit, it shows how to use a 555 timer and a small glass-encapsulated mercury switch to indicate 'tilt'.

Applications 4

Metronome

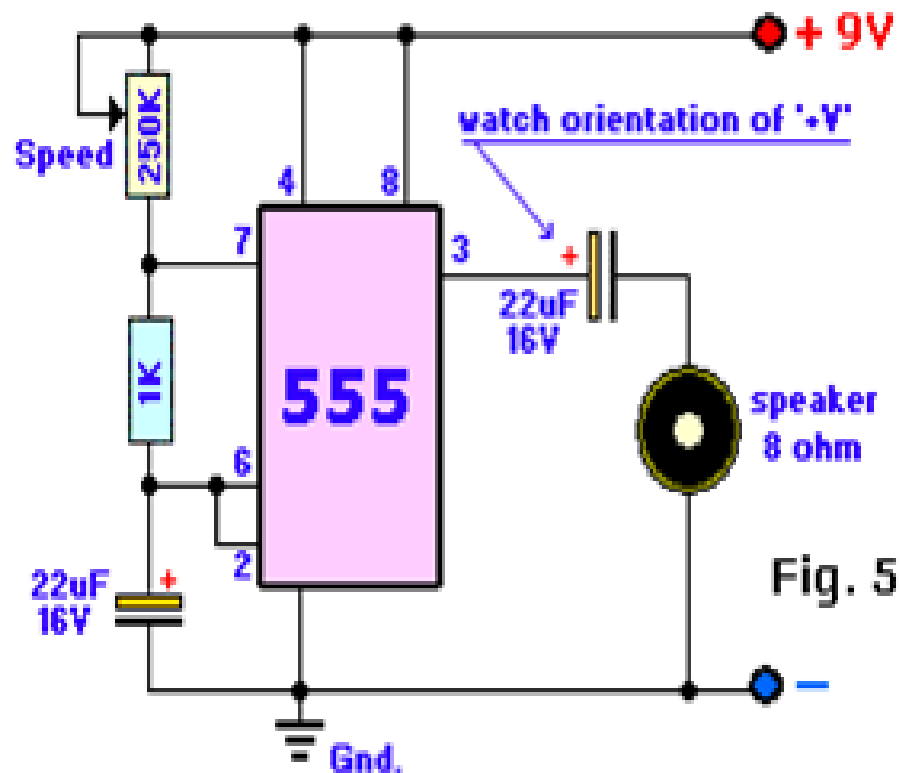


- A Metronome is a device used in the music industry
- It indicates the rhythm by a 'tic-toc' sound which speed can be adjusted with the 250K potentiometer

555 Timer Experiments

Experiments	Chapters
What's micro controller	5
Basic A and D	6
Earth measurements	
Robotics	
StampWorks	17 and 18
Others	

Lecture 10

DS1620

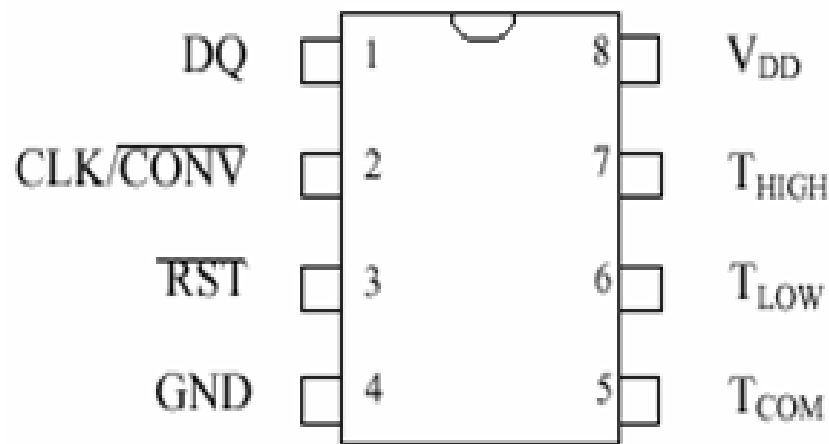


- Digital thermometer
 - Provides 9-bit temperature readings
 - Temperature range from -55°C to 125°C
 - Acts as a thermostat


Detail Description

PIN	SYMBOL	DESCRIPTION
1	DQ	Data Input/Output pin for 3-wire communication port.
2	CLK/ $\overline{\text{CONV}}$	Clock input pin for 3-wire communication port. When the DS1620 is used in a stand-alone application with no 3-wire port, this pin can be used as a convert pin. Temperature conversion will begin on the falling edge of $\overline{\text{CONV}}$.
3	$\overline{\text{RST}}$	Reset input pin for 3-wire communication port.
4	GND	Ground pin.
5	T _{COM}	High/Low Combination Trigger. Goes high when temperature exceeds TH; will reset to low when temperature falls below TL.
6	T _{LOW}	Low Temperature Trigger. Goes high when temperature falls below TL.
7	T _{HIGH}	High Temperature Trigger. Goes high when temperature exceeds TH.
8	V _{DD}	Supply Voltage. 2.7V – 5.5V input power pin.

DS1620 with BS2

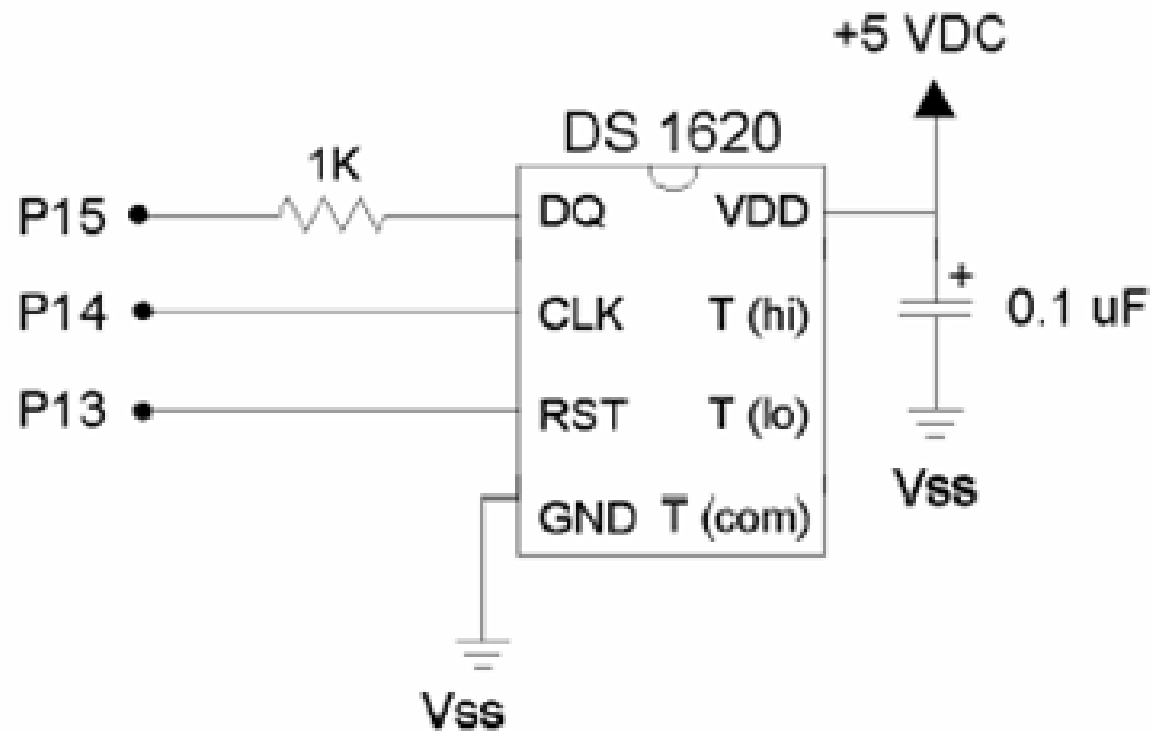

Programming for DS1620 1

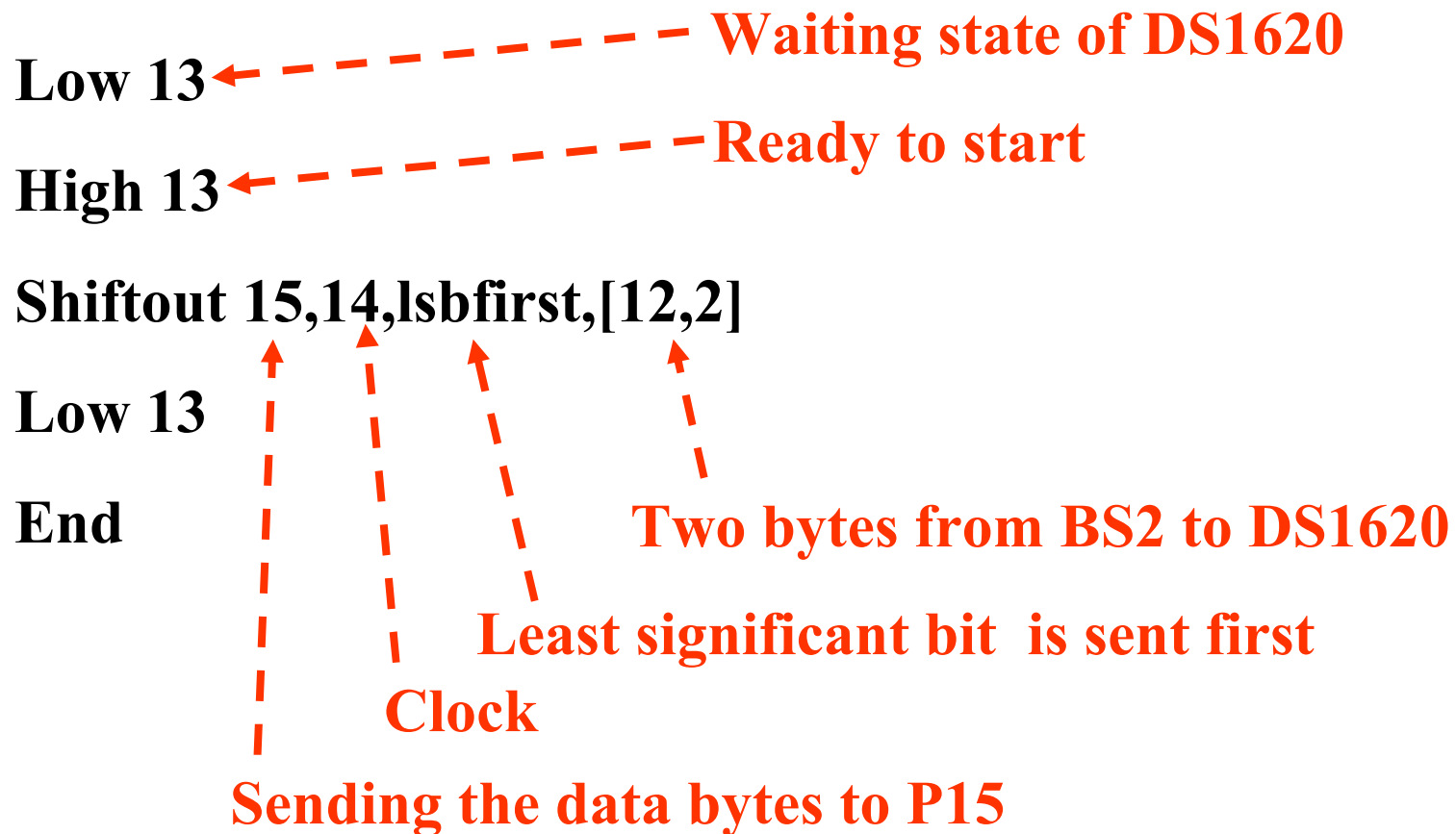

Programming for DS1620 2

high 13 ← - - - - - Ready to start

Shiftout 15,14,lsbfirst,[238] ← - - Start conversion

low 13

Temploop:

high 13

shiftout 15,14,lsbfirst,[170] ← - - Send "get data" command



shiftin 15,14,lsbpre,[x] ← - - - - Get the data

low 13

degC=x/2

Goto Temploop


AD592

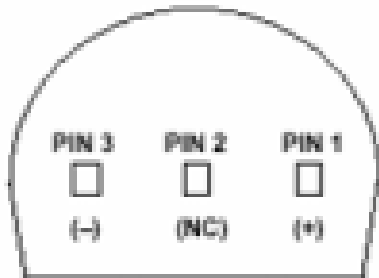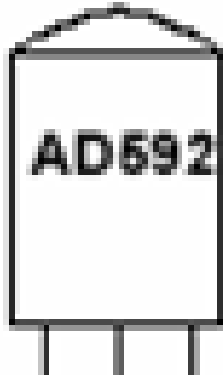

✦ PIN 2 CAN BE EITHER ATTACHED OR UNCONNECTED
BOTTOM VIEW

- Analog temperature sensor
 - Provides an output current proportional to absolute temperature
 - Temperature range from -25°C to 105°C
 - Acts as a thermostat
 - Extended out away from the recording instruments



Temperature Probe with AD592

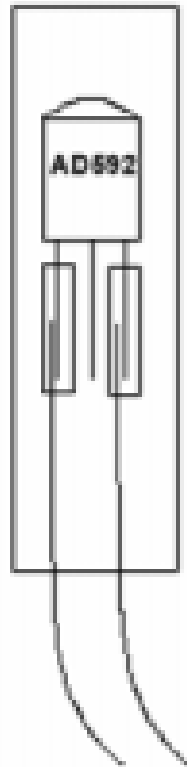

- The part needs to be protected before being inserted into liquid




How to Make Temperature Probe 1

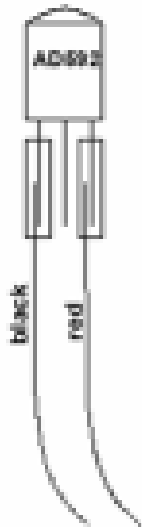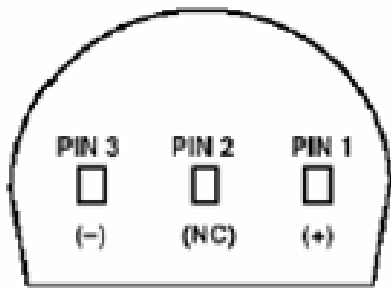


1. Identify the AD 592's (-), NC, and (+) pins from this picture as viewed from the bottom
2. Slip the solder sleeve over the black wire and pin 3 (-)
3. Slip another solder sleeve over the red wire and pin 1 (+)
4. Heat up the connections until the wires are joined

How to Make Temperature Probe 2

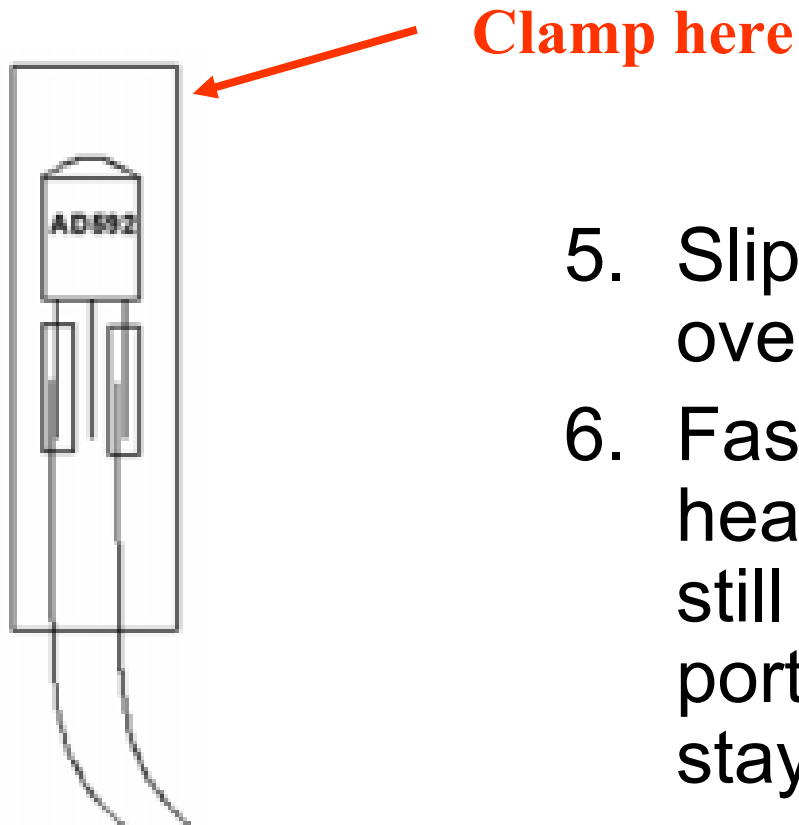


5. Slip the heat shrink tubing over the entire package
6. Fasten the package with a heat gun, and while it's still hot clamp the top portion to ensure that it stays shut

AD592 with BS2

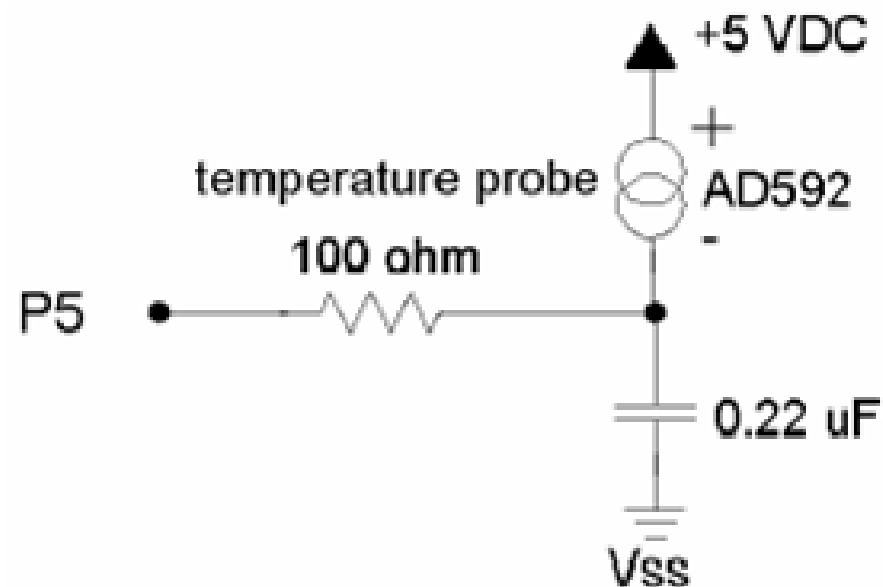

Caution!!

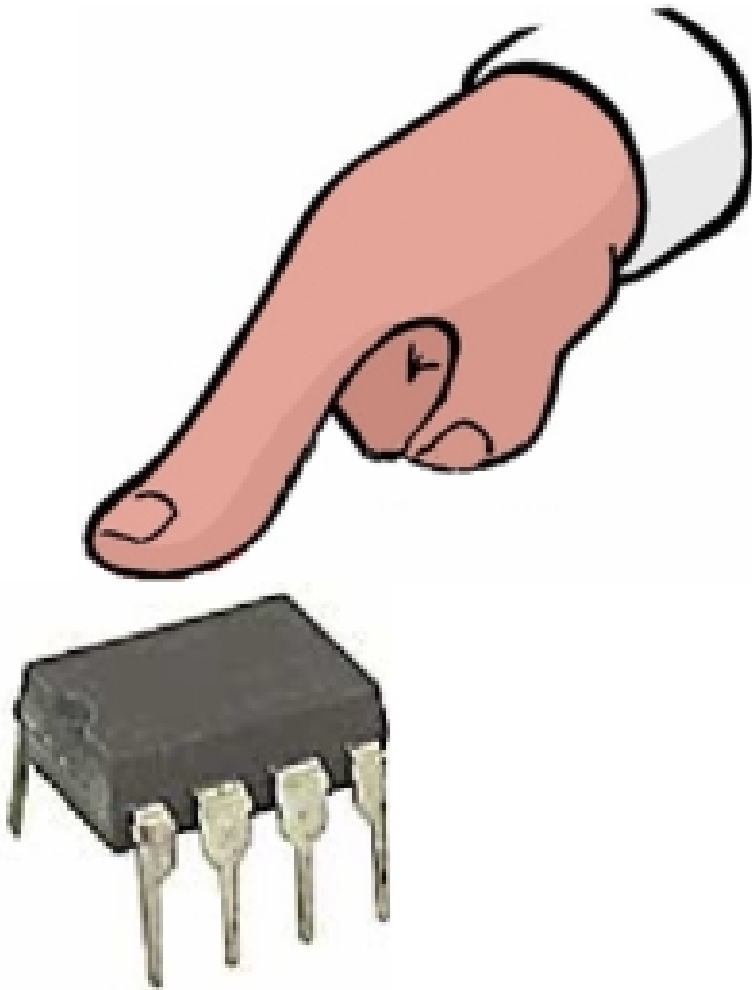

- Be careful when you put your finger on it
- Specially for a big finger

Temperature Sensors Experiments

Experiments	Chapters
What's micro controller	
Basic A and D	
Earth measurements	1, 2, 3*, and 4
Robotics	
StampWorks	28
Others	

***Use 2 wires for Simple Resistance Detector with proper resistor and capacitor**