

8TH GRADE MATHEMATICS:



AIM: USING OHM'S LAW TO SOLVE MATH PROBLEMS

HOME WORK: HANDOUT BY MR. AKOMAH

ENCHANCING STUDENTS SKILLS IN INVERESE OPERATION USING OHMS LAW

Learning Objectives : Students will...

1. Become aware of Ohm's Law, the relationship between current, voltage, and resistance in a series circuit.
2. To solve selected problems using Ohm's Law & Inverse operation and other math concepts.
3. To study Ohm's law and its application in simple series circuits; to determine current voltage and resistance

COGNITIVE DEMANDS ON THE LESSON

LEVEL I: MATHEMATICAL SKILL


LEVEL II: CONCEPTUAL UNDERSTANDING

LEVEL III: PROBLEM SOLVING



PREPARED

BY: MR. A. AKOMAH

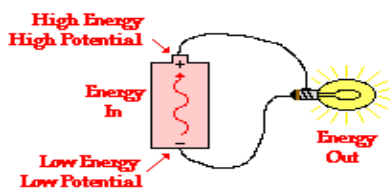

MOTIVATION: HAVE A STUDENT READ THE FOLLOWING:


Ohm's Law shows the relationship between ohms, volts and amps. This lesson will help us comprehend the daily use electricity in our homes.

LESSON INTRODUCTION: HOW THIS MATH CONNECTS:

TEACHER: Explain to students the daily use of mathematics in all aspects of our lives. Draw the schematics of a circuit and explain to students how Electricians use the formulas to install the correct gauge of wire to carry the load.

Materials needed per student:

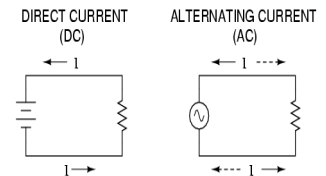- Pencil
- Calculator with $\sqrt{\quad}$ key & memory +/- functions
- Electricity and Ohm's Law Worksheets
- Electricity and Ohm's Law Example Problem handout
- Formulas, Equations, and Laws handout and two Ohm's Law handouts



NOTE: Ohm's Law states that in a simple electrical circuit, the voltage equals the electrical current times the resistance.

$$V = IR$$

where:

- V is the voltage in volts
- I is the current in amperes or amps
- R is the resistance in ohms

Vocabulary: CURRENT, VOLTAGE, RESISTANCE

Current: Indicates the amount of electrons passing through the wire and is measured in amperes or amps for short. { I } is the unit symbol for Amps.

Ohm's Law

$$I = \frac{V}{R}$$

Electric current = Voltage / Resistance

EXPLAIN: Current is what flows in a wire or conductor like water flowing down a pipe.

VOLTAGE: The force that drives electrical charges through a circuit is measured in volts. $V = IR$

RESISTANCE: Determines how much current will flow through a component. Resistors are used to control. $R = \frac{V}{I}$

Teacher used training aids:

- 9 volt battery
- 18" lengths of insulated wire with clips

- 10 ohm 0.25 watt resister
- 220 ohm 0.5 watt resister

Problem #1: GIVE STUDENTS TIME TO ANALYSIS THE PROBLEM (LEVEL III)

A 110 volt wall outlet supplies power to a strobe light with a resistance of 20 ohms. How much current is flowing through the strobe light?

SOLUTION:

$$V = 110 \text{ VOLTS} \quad R = 20 \text{ OHMS} \quad I = ?$$

$$V = IR$$

REPLACE VARIABLE WITH VALUES

$$110 \text{ VOLTS} = I (20)$$

DIVIDE BOTH SIDES BY 20

$$\frac{110 \text{ VOLTS}}{20} = \frac{I(20)}{20}$$

$$5.5 = I$$

ANSWER: $I = 5.5 \text{ Amp}$.

Problem #2

A CD player with a resistance of 50 ohms has a current of 0.2 amps flowing through it. Sketch the circuit diagram and calculate how many volts supply the CD player.

SOLUTION:

$$V = ? \quad R = 50 \text{ ohms} \quad I = 0.2$$

$$V = IR$$

$$V = 50 (0.2)$$

ANSWER: $V = 5 \text{ Volt}$.

Problem #3

A 120-volt power source supplies a lamp with a resistance of 200 ohms. What is the current flow of the circuit?

$$V = 120 \text{ VOLTS} \quad R = 200 \text{ OHMS} \quad I = ?$$

$$V = IR$$

REPLACE VARIABLE WITH VALUES

$$120 \text{ VOLTS} = I (200)$$

DIVIDE BOTH SIDES BY 200

$$\frac{120 \text{ VOLTS}}{200} = \frac{I(200)}{200}$$

$$0.6 = I$$

ANSWER: $I = 0.6 \text{ Amp}$

Problem #4

A source has a current of 0.2Amperes and a resistance $R = 1000 \text{ ohms}$, Find the Voltage.

.Solution:

$$V = IR$$



REPLACE VARIABLE WITH VALUES

$$V = 0.2A (1000 \Omega) = 200V$$

MULTIPLY

$$V = 200V$$

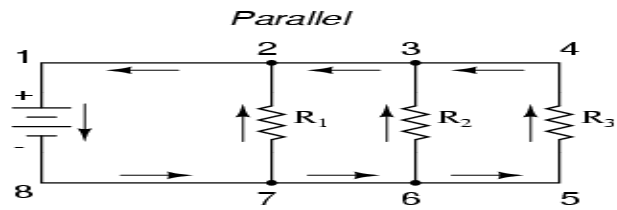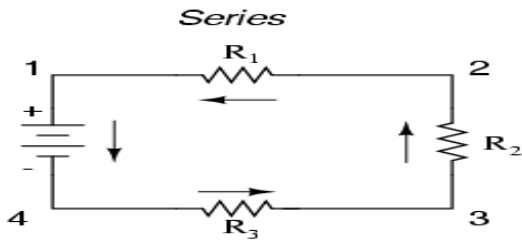
ANOTHER LESSON COMPONENT: DRAW ON BOARD AND EXPLAIN:
EXPLAIN TO STUDENTS: Most home are wired in Series or Parallel Circuit



Resistances in Series

When resistances R_1, R_2, R_3, \dots are connected in series, the total resistance R_s is:


$$R_s = R_1 + R_2 + R_3 + \dots R_n$$

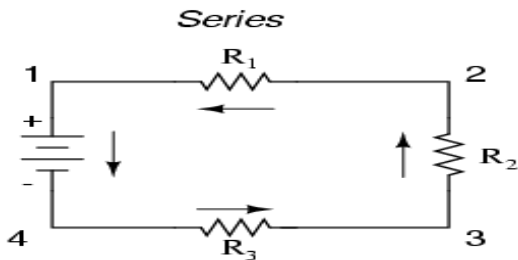


Resistances in Parallel

When resistances R_1, R_2, R_3, \dots are connected in parallel, the total resistance R_p is:
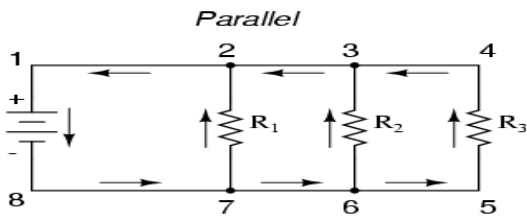
$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots + \frac{1}{R_n}$$



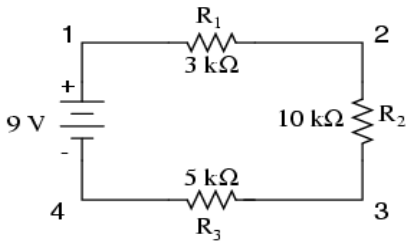EXAMPLE: FIND THE TOTAL RESISTANCE, CURRENT, & VOLTAGE ACROSS EACH RESISTOR



Solution:

$$R_S = R_1 + R_2 + R_3 + \dots R_S$$

$$R_S = 3 + 10 + 5 +$$

$$R_S = 18 \text{ Ohms}$$

$$I_{\text{TOTAL}} = \frac{E_{\text{TOTAL}}}{R_{\text{TOTAL}}} = \frac{9V}{18}$$

$$I_{\text{TOTAL}} = \frac{9V}{18K\Omega} = \frac{9}{18,000} = 500\mu A$$

$$E_{R1} = I(R1)$$

$$E_{R2} = I(R2)$$

$$E_{R3} = I(R3)$$

$$E_{R1} = 500\mu A (3K\Omega)$$

$$E_{R2} = 500\mu A (10K\Omega)$$

$$E_{R3} = 500\mu A (5K\Omega)$$

$$E_{R1} = 500\mu A (3000)$$


$$E_{R2} = 500\mu A (1000\Omega)$$

$$E_{R3} = 500\mu A (5000\Omega)$$

$$E_{R1} = 1.5 \text{ VOLTS}$$

$$E_{R2} = 5 \text{ VOLTS}$$

$$E_{R3} = 500\mu A (5000\Omega)$$

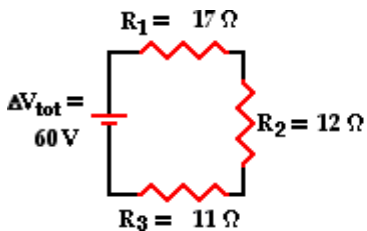

FIND THE TOTAL RESISTOR, TOTAL CURRENT, EACH CURRENT, AND EACH VOLTAGE ACROSS EACH RESISTOR:

SOLUTION: $R_{eq} = R_1 + R_2 + R_3 = 17 \Omega + 12 \Omega + 11 \Omega = 40 \Omega$
 $I_{tot} = \Delta V_{\text{battery}} / R_{eq} = (60 \text{ V}) / (40 \Omega) = 1.5 \text{ amp}$

$$I_{\text{battery}} = I_1 = I_2 = I_3$$

$$\Delta V_1 = I_1 \cdot R_1$$

$$= 1.5 \text{ amp}$$

$$\Delta V_2 = I_2 \cdot R_2$$

$$\Delta V_3 = I_3 \cdot R_3$$

$$\Delta V_1 = (1.5 \text{ A}) \cdot (17 \Omega)$$

$$\Delta V_2 = (1.5 \text{ A}) \cdot (12 \Omega)$$


$$\Delta V_3 = (1.5 \text{ A}) \cdot (11 \Omega)$$

$$\Delta V_1 = 25.5 \text{ V}$$

$$\Delta V_2 = 18 \text{ V}$$

$$\Delta V_3 = 16.5 \text{ V}$$

$$\Delta V_{\text{tot}} = 60 \text{ V}$$

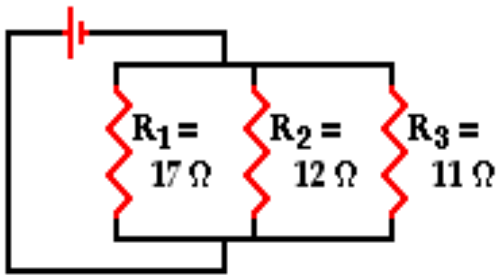

FIND THE TOTAL RESISTOR, TOTAL CURRENT, EACH CURRENT, AND EACH VOLTAGE ACROSS EACH RESISTOR:

SOLUTION

$$1 / R_{\text{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} = \frac{1}{17} + \frac{1}{12} + \frac{1}{11}$$

$$I_{\text{tot}} = \frac{\Delta V_{\text{battery}}}{R_{\text{eq}}} = \frac{60 \text{ V}}{4.29063 \Omega}$$

$$I_{\text{tot}} = 14.0 \text{ amp}$$

$$I_1 = \Delta V_1 / R_1$$

$$\Delta V_2 = \Delta V_2 / R_2$$

$$\Delta V_3 = \Delta V_3 / R_3$$


$$\begin{aligned} \Delta V_{\text{battery}} &= \Delta V_1 \\ &= \Delta V_2 = \Delta V_3 \\ &= 60 \text{ V} \end{aligned}$$

$$I_1 = (60 \text{ V}) / (17 \Omega) \quad I_2 = (60 \text{ V}) / (12 \Omega) \quad I_3 = (60 \text{ V}) / (11 \Omega)$$

$$I_1 = 3.53 \text{ amp}$$

$$I_2 = 5.00 \text{ amp}$$

$$I_3 = 5.45 \text{ amp}$$

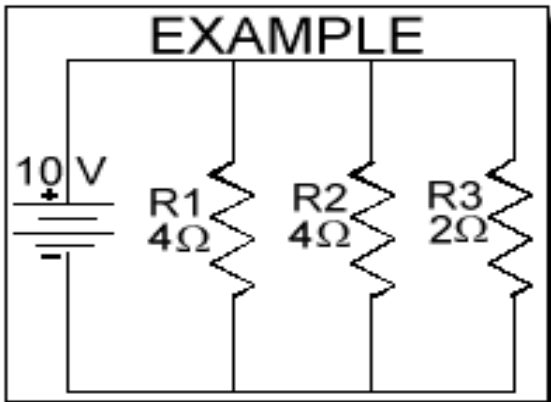

FIND THE TOTAL RESISTANCE OF THE CIRCUIT

SOLUTION:

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$\frac{1}{R_T} = \frac{1}{4} + \frac{1}{4} + \frac{1}{2}$$

$$\frac{1}{R_T} = \frac{1}{4} + \frac{1}{4} + \frac{2}{2}$$

$$\frac{1}{R_T} = \frac{1}{4} + \frac{1}{4} + \frac{2}{2}$$


$$\frac{1}{R_T} = \frac{1}{4} + \frac{1}{4} + \frac{2}{2} = 1 \text{ OHM}$$

$$R_T = 1 \text{ OHM}$$

Extensions

Students will solve problems with circuits dealing with series and parallel circuits.

A series-parallel combination circuit

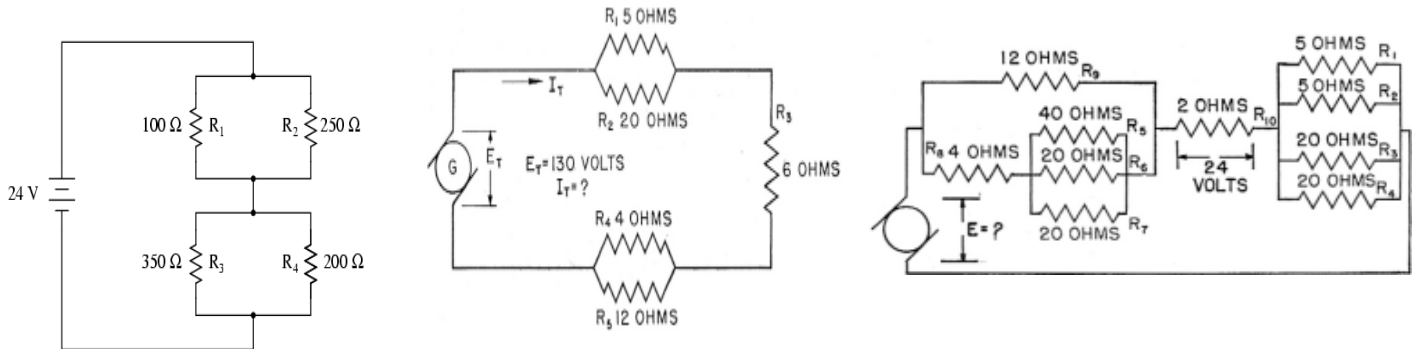


Summary: Ohm's Law is the equation $V = I R$ that shows the relationship between voltage, current and resistance in a simple electrical circuit. It applies both the AC and DC circuits.



$$R_{equivalent} = R_1 + R_2 + R_3 + \dots$$

$$R_{equivalent} = \frac{V}{I} = \frac{V_1 + V_2 + V_3 + \dots}{I} = \frac{V_1}{I_1} + \frac{V_2}{I_2} + \frac{V_3}{I_3} + \dots = R_1 + R_2 + R_3 + \dots$$

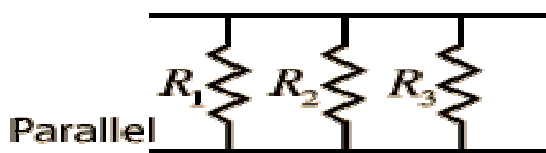Series key idea: The current is the same in each resistor by the current law.



$$\frac{1}{R_{equivalent}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots$$

Parallel:
$$\frac{V}{R_{equivalent}} = I = I_1 + I_2 + I_3 + \dots = \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} + \dots$$

$$\frac{1}{R_{equivalent}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots$$

Parallel key idea: The voltage is the same across each resistor by the voltage law.

HANDOUT:

HOME WORK: BY MR. A. AKOMAH {PLEASE SHOW YOUR STEPS}

1. The unit of electrical pressure is the _____.
2. The unit of electrical current is the _____.
3. The unit of electrical resistance is the _____.
4. The current in a circuit is
 - (a) _____ proportional to the applied voltage.
 - (b) _____ proportional to the resistance.
5. The relation between current, voltage and resistance in a circuit is expressed by the equation
Amperes _____.
6. If a generator supplies 60 volts across a resistor and a current of 10 amperes flows through the circuit, what is the ohmic value of the resistor?
7. A generator is supplying 120 volts to a circuit which comprises two resistances, 6 ohms and 4 ohms, in series. What is the current flowing in the circuit?
8. What voltage must a generator have to produce a current of 6 amperes through resistances of 2 ohms, 3 ohms, and 5 ohms connected in series?
9. Four resistors, of 8 ohms, 6 ohms, 2 ohms and one of unknown resistance, are connected in series. A generator supplies 120 volts across this circuit. The IR-drop across the 6-ohm resistance is 36 volts. (a) What current is flowing in the circuit? (b) What is the total circuit resistance? (c) What ohmic value has the unknown resistor?
10. A generator supplies 100 volts to 3 resistors in series, whose resistances are 2 ohms, 3 ohms and 5 ohms. (a) What current flows in the circuit? (b) What is the current in each resistor?

ANSWERS : TO THE ABOVE

1. volt 2. Ampere 3. Ohm 4. (a) directly (b) inversely
5. volts/ohms 6. 6 ohms 7. 12 amperes 8. 60 volts 9. (a) $I = 6$ amperes
(b) $R_t = 20$ ohms (c) $R_x = 20$ ohms 10. (a) $I = 10$ amperes (b) $I = 10$ amperes

EXAMPLE :

Voltage = 10V
R1 = 4 Ohm
R2 = 4 Ohm
R3 = 2 Ohm

Remember that "Rt" means Total resistance of the circuit.
R1, R2, etc. are Resistor one, Resistor two, etc.

Now we will apply the formula above to this example:

$$\frac{1}{R_t} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

Therefore:

$$\frac{1}{R_t} = \frac{1}{4} + \frac{1}{4} + \frac{1}{2}$$

It is easiest to change the fractions into decimal numbers (example 1 divide by 4 equals .25):

$$\frac{1}{R_t} = .25 + .25 + .5$$
$$\frac{1}{R_t} = 1$$

Now you have to get rid of the 1 on the left side so...

$$R_t = 1/1$$
$$R_t = 1 \text{ Ohm}$$

NOW, Let's try a more complex one:

Voltage = 120 Volts
R1 = 100 Ohms
R2 = 200 Ohms
R3 = 1000 Ohms
R4 = 1 Ohms

$$\frac{1}{R_t} = \frac{1}{100} + \frac{1}{200} + \frac{1}{1000} + \frac{1}{1}$$
$$\frac{1}{R_t} = .01 + .005 + .001 + 1$$
$$\frac{1}{R_t} = 1.016$$
$$R_t = 1/1.016 = .98 \text{ Ohms}$$